



EE201

تصميم منطقي

Logic Design

إعداد وتجميع

ا.م.د/ هانى احمد عطاالله

كلية الهندسة بقنا

قسم الهندسة الكهربائية

العام الجامعى

2025/2024

بيانات الكتاب

الكلية: الحاسبات والمعلومات

الفرقة: المستوى الثانى

التخصص: عام

تاريخ النشر: 2024

عدد الصفحات: 145

اعداد وتجميع : ا.م.د/ هانى احمد عطاالله

الرموز المستخدمة

نص للقراءة والدراسة



أنشطة ومهام



أسئلة للتفكير والتقييم الذاتى



فيديو للمشاهدة



رابط خارجي



تواصل عبر مؤتمر الفيديو



المحتوى

Contents	Page
Introduction	5
Ch1: Introduction to digital design and Binary Numbers	9
Ch1: Binary Codes and Logic Gates	20
Ch2: Boolean Algebra	39
Ch2: Logic Gates and operations	50
Ch3: the map method and Gate Level Minimization	61
Ch3: Nand and Nor Implementation	82
Ch4: Adders	91
Ch4: Multipliers	95
Ch4: Decoders and Encoders	106
Ch4: Multiplexers	113
Ch5: Sequential Circuits -Flip-Flops	119
Ch5: Sequential Circuits -Counters	129
Ch5: Registers and Shift registers	142
Ch5: Serial Addition and Ripple counters	145
Review	142
References	145

الصور والأشكال

الفيديو

Introduction



Digital Design is about designing in digital space so that the created contents can be displayed and seen on a digital device. With the availability of high computing power, designers are able to quickly create designs in digital space prior to actual deployment.

The course is an introduction to digital design technology. It allows you to understand the basics of digital design and helps you develop skills.

In this course the student will be learn the following topics: Binary systems and Boolean algebra- logic gates – simplifying the Boolean circuit-combinational circuits- encryption and decryption - asynchronous sequential circuits and their applications- synchronous sequential circuits and their applications- displacement recorders- counters – memories and types of memories.

The following is a brief summary of the topics that are covered in each chapter.

Chapter 1 presents the various binary systems suitable for representing information in digital systems. The binary number system is explained and binary codes are illustrated. Examples are given for addition and subtraction of signed binary numbers and decimal numbers in binary-coded decimal (BCD) format.

Chapter 2 introduces the basic postulates of Boolean algebra and shows the correlation between Boolean expressions and their corresponding logic diagrams. All Possible logic operations for two variables are investigated, and the most useful logic gates used in the design of digital systems are identified. This chapter also introduces basic CMOS logic gates.

Chapter 3 covers the map method for simplifying Boolean expressions. The map method is also used to simplify digital circuits constructed with AND-OR, NAND, or NOR gates. All other possible two-level gate circuits are considered, and their method of implementation is explained. Verilog HDL is introduced together with simple examples of gate-level models.

Chapter 4 outlines the formal procedures for the analysis and design of combinational circuits. Some basic components used in the design of digital systems, such as adders and code converters, are introduced as design examples. Frequently used digital logic functions such as parallel adders and subtractors, decoders, encoders, and multiplexers are explained, and their use in the design of combinational circuits is illustrated.

Chapter 5 outlines the formal procedures for analyzing and designing clocked (synchronous) sequential circuits. The gate structure of several types of flip-flops is presented together with a discussion on the difference between level and edge triggering.

Chapter 6 deals with various sequential circuit components such as registers, shift registers, and counters. These digital components are the basic building blocks from which more complex digital systems.

Logic Design

Table of Contents

Week 1	Ch1: Introduction to digital design and Binary Numbers
Week 2	Ch1: Binary Codes and Logic Gates
Week 3	Ch2: Boolean Algebra
Week 4	Ch2: Logic Gates and operations
Week 5	Ch3: the map method and Gate Level Minimization
Week 6	Ch3: Nand and Nor Implementation
Week 7	Ch4: Adders
Week 8	Ch4: Multipliers
Week 9	Midterm Exam
Week 10	Ch5: Decoders and Encoders
Week 11	Ch5: Multiplexers
Week 12	Ch6: Sequential Circuits -Flip-Flops
Week 13	Ch6: Sequential Circuits -Counters
Week 14	Ch7: Registers and Shift registers
Week 15	Ch7: Serial Addition and Ripple counters
Week 16	Review


Ch1: Introduction to Digital Design and Binary Numbers

Digital vs. Analog

- **Analog:** Continuous function V of continuous variable t (time, space etc.) : $V(t)$

An **analog*** quantity is one having continuous values.


 
Example: Human voice in air, analog devices.



- **Digital:** Discrete function V_k of discrete sampling variable t_k , with $k = \text{integer}$: $V_k = V(t_k)$

A **digital** quantity is one having a discrete set of values.

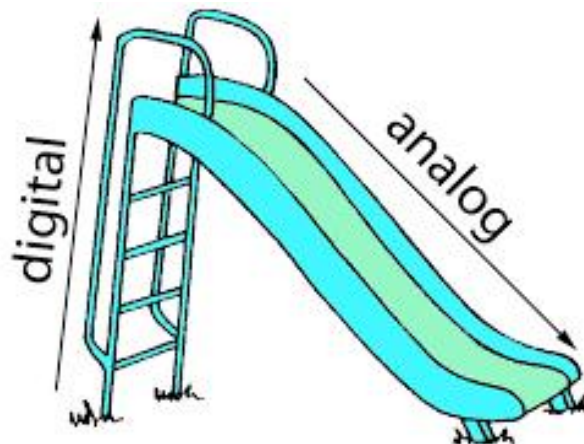 
Example: Computer, CDs, DVDs, digital devices.



Continuous vs. Discrete






Continuous:

 - defined for every instant of time
- denoted by $x(t)$



Discrete:

     - defined at the discrete-instant of time
- denoted by $x(n)$



Digital vs. Analog

- An analog system has continuous range of values
- ☐ A mercury thermometer
- ☐ Vinyl records
- ☐ Human eye




- A digital system has a set of discrete values


- Digital Thermometer
- Compact Disc (CD)
- Digital camera



Analog System: Audio System

 

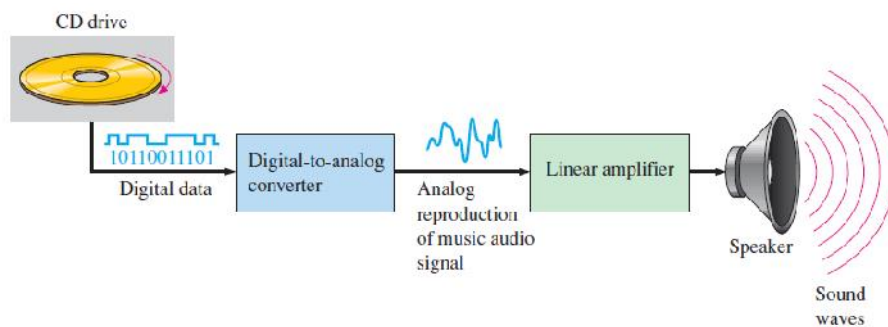System using Digital and Analog Methods: The Compact Disk (CD) Player



Digital Systems and Units

CPU	Digital Watch	Digital Cameras

Benefits of using digital

- Advantages of using Digital:
- Cheap electronic circuits
- Easier to calibrate and adjust
- Resistance to noise: Clearer picture and sound

Data Types and Representation

1- Integers: 35, 125, 5612*1e2

2-Real Numbers, 5.67, 0.05, 52*1e0.5

3-Strings,

a- Names (ali, maha, ...)

b- Dates (12/9/2016)


c- Addresses (Qena, Egypt)

d- Telephone Numbers (0965214264)

e- string: \$, &, %, @, ...

Number Systems : 1- Decimal Code

 Base (Radix) is 10 - symbols (0,1, . . 9) Digits (Base-1)




✓ If we were to write 1936.25 using a power series expansion and **base 10** arithmetic:

$$1 \times 10^3 + 9 \times 10^2 + 3 \times 10^1 + 6 \times 10^0 + 2 \times 10^{-1} + 5 \times 10^{-2}$$

2- Binary Number System

Discrete elements of information are represented with bits called *binary codes*.

 - Base is 2 - symbols (0,1) - Binary Digits (Bits)
- Each position carries a weight (using decimal).



- ✓ If we write 10111.01 using a decimal power series we convert from binary to decimal:

$$1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 + 0 \times 2^{-1} + 1 \times 2^{-2} =$$

$$= 1 \times 16 + 0 \times 8 + 1 \times 4 + 1 \times 2 + 1 \times 1 + 0 \times 0.5 + 1 \times 0.25 = 23.25$$


3- Octal Number system

The octal number system [from Greek: OKTΩ].

- Its base is 8 → eight digits 0, 1, 2, 3, 4, 5, 6, 7

- ✓ $(236.4)_8 = (?)_{10}$
 
$$2 \times 8^2 + 3 \times 8^1 + 6 \times 8^0 + 4 \times 8^{-1} = 158.5$$



4- Hexadecimal Number system

-The hexadecimal number system [from Greek: ΔΕΚΑΕΞΙ].

– Its base is 16 → first 10 digits are borrowed from the decimal system (0 -- 9) and the letters A, B, C, D, E, F are used for the digits 10, 11, 12, 13, 14, 15

$$\checkmark (D63FA)_{16} = (?)_{10}$$

$$13 \times 16^4 + 6 \times 16^3 + 3 \times 16^2 + 15 \times 16^1 + 10 \times 16^0 = 877562$$

Different Systems

Numbers with Different Bases

Decimal (base 10)	Binary (base 2)	Octal (base 8)	Hexadecimal (base 16)
00	0000	00	0
01	0001	01	1
02	0010	02	2
03	0011	03	3
04	0100	04	4
05	0101	05	5
06	0110	06	6
07	0111	07	7
08	1000	10	8
09	1001	11	9
10	1010	12	A
11	1011	13	B
12	1100	14	C
13	1101	15	D
14	1110	16	E
15	1111	17	F

Conversion from Binary to Decimal

Let each bit of a binary number be represented by a variable whose subscript = bit positions, i.e.,

$$(110)_2 = (a_2 a_1 a_0)_2$$

Its decimal equivalent is:

$$(1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0)_{10} = (a_2 \times 2^2 + a_1 \times 2^1 + a_0 \times 2^0)_{10}$$

It is necessary to separate the number into an integer part and a fraction: Repeatedly divide the decimal number by 2.

✓ Find the binary equivalent of 37.

$2 \overline{)37}$	$- 18 + 0.5$	1	←	LSB	↘	LSB Least Significant Bit
$2 \overline{)18}$	$= 9 + 0$	0				
$2 \overline{)9}$	$= 4 + 0.5$	1				
$2 \overline{)4}$	$= 2 + 0$	0				
$2 \overline{)2}$	$= 1 + 0$	0				
$2 \overline{)1}$	$= 0 + 0.5$	1	←	MSB	↙	MSB Most Significant Bit

$$37_{10} = 100101_2$$

□ $53_{10} = \underline{\quad? \quad}_2$ ANS: $53_{10} = 110101_2$

Conversion from decimal fraction to binary:

same method used for integers except multiplication is used instead of division.

✓ Convert $(0.8542)_{10}$ to binary (give answer to 6 digits).

$$\begin{array}{rcll}
 0.8542 \times 2 = & 1 & + & 0.7084 & a_{-1} = 1 & \text{MSB} \\
 0.7084 \times 2 = & 1 & + & 0.4168 & a_{-2} = 1 & \\
 0.4168 \times 2 = & 0 & + & 0.8336 & a_{-3} = 0 & \\
 0.8336 \times 2 = & 1 & + & 0.6672 & a_{-4} = 1 & \\
 0.6672 \times 2 = & 1 & + & 0.3344 & a_{-5} = 1 & \\
 0.3344 \times 2 = & 0 & + & 0.6688 & a_{-6} = 0 & \text{LSB}
 \end{array}$$

$$(0.8542)_{10} = (0.a_{-1}a_{-2}a_{-3}a_{-4}a_{-5}a_{-6})_2 = (0.110110)_2$$


Dr. Hany Ahmed Date: 9/2017

Convert $(0.6875)_{10}$ to binary. First, 0.6875 is multiplied by 2 to give an integer and a fraction. Then the new fraction is multiplied by 2 to give a new integer and a new fraction. The process is continued until the fraction becomes 0 or until the number of digits has sufficient accuracy. The coefficients of the binary number are obtained from the integers as follows:

	Integer		Fraction	Coefficient
$0.6875 \times 2 =$	1	+	0.3750	$a_{-1} = 1$
$0.3750 \times 2 =$	0	+	0.7500	$a_{-2} = 0$
$0.7500 \times 2 =$	1	+	0.5000	$a_{-3} = 1$
$0.5000 \times 2 =$	1	+	0.0000	$a_{-4} = 1$

Dr. Hany Ahmed Date: 9/2017

• Conversion from Decimal to Octal

 

Division	Quotient	Remainder
415/8	51	7
51/8	6	3
6/8	0	6

Octal = 637

Dr. Hany Ahmed Date: 9/2017

• Conversion from Decimal to Octal

Decimal to Octal Conversion

Example: $(175)_{10}$

	Quotient	Remainder	Coefficient
$175 / 8 =$	21	7	$a_0 = 7$
$21 / 8 =$	2	5	$a_1 = 5$
$2 / 8 =$	0	2	$a_2 = 2$

Answer: $(175)_{10} = (a_2 a_1 a_0)_8 = (257)_8$

Example: $(0.3125)_{10}$

	Integer	Fraction	Coefficient
$0.3125 * 8 =$	2	. 5	$a_1 = 2$
$0.5 * 8 =$	4	. 0	$a_2 = 4$

Answer: $(0.3125)_{10} = (0.a_1 a_2 a_3)_8 = (0.24)_8$

Dr. Hany Ahmed Date: 9/2017

Conversion from decimal fraction to Octal:

Convert $(0.513)_{10}$ to octal.

$$0.513 \times 8 = 4.104$$

$$0.104 \times 8 = 0.832$$

$$0.832 \times 8 = 6.656$$

$$0.656 \times 8 = 5.248$$

$$0.248 \times 8 = 1.984$$

$$0.984 \times 8 = 7.872$$

The answer, to seven significant figures, is obtained from the integer part of the products:

$$(0.513)_{10} = (0.406517 \dots)_8$$

Dr. Hany Ahmed Date: 9/2017

Arithmetic operations in Systems

Arithmetic operations in Binary Number System

augend:	101101	minuend:	101101	multiplicand:	1011
addend:	<u>+100111</u>	subtrahend:	<u>-100111</u>	multiplier:	<u>× 101</u>
sum:	1010100	difference:	000110		1011
				partial product:	0000
					<u>1011</u>
				product:	110111

Dr. Hany Ahmed Date: 9/2017

Arithmetic operations in Binary Number System

$$\begin{array}{r}
 11.25 \quad 1011.01 \\
 6.5 \quad \times 110.1 \\
 \hline
 \boxed{101101} \\
 \boxed{0000000} \\
 \boxed{10110100} \\
 \boxed{101101000} \\
 \hline
 73.125 \quad 1001001.001
 \end{array}
 \qquad
 \begin{array}{r}
 10111.01 \\
 + 1110.11 \\
 \hline
 100110.00 \\
 \hline
 23.25 \\
 14.75 \\
 38.00
 \end{array}$$

Dr. Hany Ahmed Date: 9/2017

Arithmetic operations in Octal Number System

Evaluate:

(i) $(162)_8 + (537)_8$

$$\begin{array}{r}
 11 \quad \leftarrow \text{carry} \\
 162 \\
 \hline
 537 \\
 \hline
 721
 \end{array}$$

Therefore, sum = $(721)_8$

Dr. Hany Ahmed Date: 9/2017

Arithmetic operations in Octal Number System

$$(iv) (67.5)_8 + (45.6)_8$$

Solution:


$$\begin{array}{r}
 11 \quad \leftarrow \text{carry} \\
 67.5 \\
 \underline{45.6} \\
 135.3
 \end{array}$$

Therefore, sum = $(135.3)_8$


Binary Digits

Each of the two digits in the **binary** system, 1 and 0, is called a **bit**, which is a contraction of the words *binary digit*. In digital circuits, two different voltage levels are used to represent the two bits. Generally, 1 is represented by the higher voltage, which we will refer to as a HIGH, and a 0 is represented by the lower voltage level, which we will refer to as a LOW. This is called **positive logic** and will be used throughout the book.

HIGH 1 and LOW 0

 

(a) Positive-going pulse

 


(b) Negative-going pulse

Non Ideal Pulse

rise time (t_r),

fall time (t_f)

 The **pulse width (t_w)** is a measure of the duration of the pulse and is often defined as the time interval between the 50% points on the rising and falling edges



8 Nonideal pulse characteristics.

Binary Digits

1 Byte = 8 bits (Bit → 0 or 1)

enough to represent one alphanumeric **character**

1 KB = 2^{10} Bytes = 1024

1024 bytes = 1 KB	KB = Kilobyte
1024 KB = 1 MB	MB = Megabyte
1024 MB = 1 GB	GB = Gigabyte
1024 GB = 1 TB	TB = Terabyte
1024 TB = 1 PB	PB = Petabyte

Systematic multiples

the International System of Units (SI).

[memory standards](#)

**JEDEC
memory
standards**

Symbol	Prefix	SI Meaning	Binary meaning
k	kilo	$10^3 = 1000^1$	$2^{10} = 1024^1$
M	mega	$10^6 = 1000^2$	$2^{20} = 1024^2$
G	giga	$10^9 = 1000^3$	$2^{30} = 1024^3$
T	tera	$10^{12} = 1000^4$	$2^{40} = 1024^4$
P	peta	$10^{15} = 1000^5$	$2^{50} = 1024^5$
E	exa	$10^{18} = 1000^6$	$2^{60} = 1024^6$
Z	zetta	$10^{21} = 1000^7$	$2^{70} = 1024^7$
Y	yotta	$10^{24} = 1000^8$	$2^{80} = 1024^8$

[Joint Electron Device Engineering Council \(JEDEC\)](#)

ASCII Code

An alphanumeric character (e.g. a letter or number such as 'A', 'B' or '7') is stored as 1 byte. For example, to store the letter 'R' uses 1 byte, which is stored by the computer as 8 bits, '01010010'.

ASCII (American Standard Code for Information Interchange) Code

ASCII Code: Character to Binary

0	0011 0000	O	0100 1111	m	0110 1101
1	0011 0001	P	0101 0000	n	0110 1110
2	0011 0010	Q	0101 0001	o	0110 1111
3	0011 0011	R	0101 0010	p	0111 0000
4	0011 0100	S	0101 0011	q	0111 0001
5	0011 0101	T	0101 0100	r	0111 0010
6	0011 0110	U	0101 0101	s	0111 0011
7	0011 0111	V	0101 0110	t	0111 0100
8	0011 1000	W	0101 0111	u	0111 0101
9	0011 1001	X	0101 1000	v	0111 0110
A	0100 0001	Y	0101 1001	w	0111 0111
B	0100 0010	Z	0101 1010	x	0111 1000
C	0100 0011	a	0110 0001	y	0111 1001
D	0100 0100	b	0110 0010	z	0111 1010
E	0100 0101	c	0110 0011	.	0010 1110
F	0100 0110	d	0110 0100	,	0010 0111
G	0100 0111	e	0110 0101	!	0011 1010
H	0100 1000	f	0110 0110	;	0011 1011
I	0100 1001	g	0110 0111	?	0011 1111
J	0100 1010	h	0110 1000	!	0010 0001
K	0100 1011	I	0110 1001	'	0010 1100
L	0100 1100	j	0110 1010	"	0010 0010
M	0100 1101	k	0110 1011	(0010 1000
N	0100 1110	l	0110 1100)	0010 1001
				space	0010 0000

Complements of Numbers

Why? -> to simplify the subtraction operation

There are two types of complements for each base- r system: the radix complement and the diminished radix complement.

The first is referred to as

the r 's complement and the second as the $(r - 1)$'s complement. When the value of the base r is substituted in the name,

the two types are referred to as **the 2's complement** and **1's complement** for binary numbers and the **10's complement** and **9's complement** for decimal numbers.

Complements of Numbers

The $(r - 1)$'s complement.

The 9's complement of 546700 is $999999 - 546700 = 453299$.

The 9's complement of 012398 is $999999 - 012398 = 987601$.

The 1's complement of 1011000 is 0100111.

The 1's complement of 0101101 is 1010010.

Invert the binary digits

Complements of Numbers

The r 's complement.

the 10's complement of 012398 is 987602

and

the 10's complement of 246700 is 753300

The 9's complement + 1

Or the 10's complement of the first digit then the 9's for the reaming digits.

the 2's complement of 1101100 is 0010100

and

the 2's complement of 0110111 is 1001001

The 1's complement + 1

Or keep the first One (not the first digit) from left then Invert all digits (after).

Subtraction with Complements

The subtraction of two n -digit unsigned numbers $M - N$ in base r can be done as follows:

1. Add the minuend M to the r 's complement of the subtrahend N . Mathematically, $M + (r^n - N) = M - N + r^n$.
2. If $M \geq N$, the sum will produce an end carry r^n , which can be discarded; what is left is the result $M - N$.
3. If $M < N$, the sum does not produce an end carry and is equal to $r^n - (N - M)$, which is the r 's complement of $(N - M)$. To obtain the answer in a familiar form, take the r 's complement of the sum and place a negative sign in front.

The following examples illustrate the procedure:

Subtraction with Complements

Given the two binary numbers $X = 1010100$ and $Y = 1000011$, perform the subtraction (a) $X - Y$ and (b) $Y - X$ by using 2's complements.

$$\begin{array}{r}
 \text{(a)} \qquad \qquad X = \quad 1010100 \quad 84 \\
 \qquad \qquad \qquad 2\text{'s complement of } Y = + \quad \underline{0111101} \quad 67 \\
 \qquad \qquad \qquad \text{Sum} = \quad 10010001 \\
 \qquad \qquad \text{Discard end carry } 2^7 = - \quad \underline{10000000} \\
 \qquad \qquad \text{Answer: } X - Y = \quad 0010001 \quad 17
 \end{array}$$

Subtraction with Complements

Given the two binary numbers $X = 1010100$ and $Y = 1000011$, perform the subtraction (a) $X - Y$ and (b) $Y - X$ by using 2's complements.

$$\begin{array}{r}
 \text{(b)} \qquad \qquad Y = \quad 1000011 \\
 \qquad \qquad \qquad 2\text{'s complement of } X = + \quad \underline{0101100} \\
 \qquad \qquad \qquad \text{Sum} = \quad 1101111
 \end{array}$$

There is no end carry. Therefore, the answer is $Y - X = -(2^7 \text{ complement of } 1101111) = -0010001$

Signed Binary Numbers

1- the signed-magnitude


The representation: the sign with a bit placed in the leftmost position of the number. The convention is to make the sign bit 0 for positive and 1 for negative.

For example, the string of bits 01001 can be considered as 9 (unsigned binary) or as +9 (signed binary)


The string of bits 11001 represents the binary equivalent of 25 when considered as an unsigned number and the binary equivalent of -9 when considered as a signed number

referred to as the signed-magnitude

Signed Binary Numbers

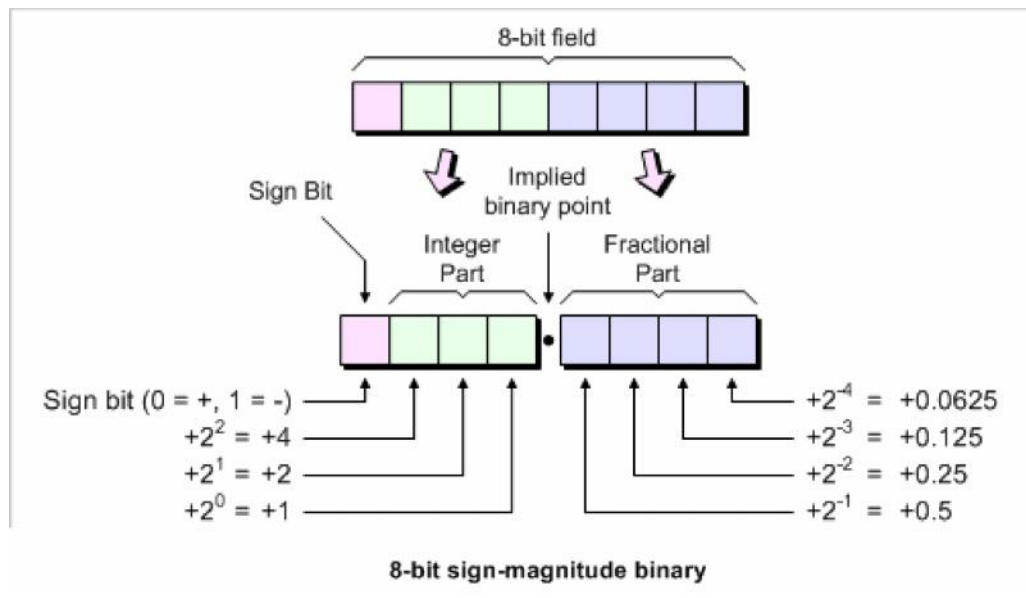

Signed Binary Numbers

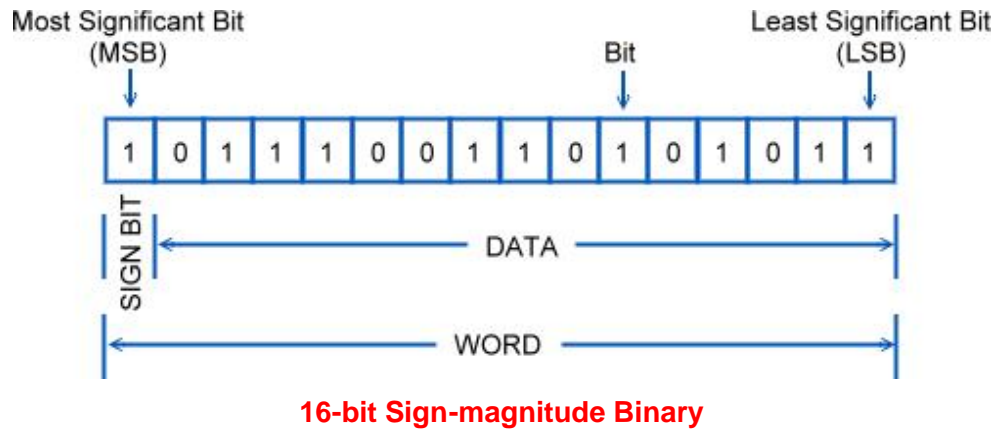

2- the signed-Complement system

The complement will always start with a 1, indicating a negative number. The signed-complement system can use either the 1's or the 2's complement, but the 2's complement is the most common.

there are three different ways to represent -9 with eight bits

signed-magnitude representation: -9	<u>1</u> 0001001
signed-1's-complement representation:	<u>1</u> 1110110
signed-2's-complement representation:	<u>1</u> 1110111

Signed Binary Numbers

Signed Binary Numbers

Decimal	Signed-2's Complement	Signed-1's Complement	Signed Magnitude
+7	0111	0111	0111
+6	0110	0110	0110
+5	0101	0101	0101
+4	0100	0100	0100
+3	0011	0011	0011
+2	0010	0010	0010
+1	0001	0001	0001
+0	0000	0000	0000
-0		1111	1000
-1	1111	1110	1001
-2	1110	1101	1010
-3	1101	1100	1011
-4	1100	1011	1100
-5	1011	1010	1101
-6	1010	1001	1110
-7	1001	1000	1111
-8	1000	—	—

Arithmetic Addition

+ 6	00000110	Discard Carry	- 6	11111010
+13	00001101		+13	00001101
+19	00010011		+ 7	00000111
+ 6	00000110		- 6	11111010
-13	11110011		-13	11110011
- 7	11111001		-19	11101101

Arithmetic Subtraction

Take the 2's complement of the subtrahend (including the sign bit) and add it to the minuend (including the sign bit). A carry out of the sign-bit position is discarded.

$$(\pm A) - (+B) = (\pm A) + (-B);$$

$$(\pm A) - (-B) = (\pm A) + (+B).$$

consider the subtraction $(-6) - (-13) = +7$.

written as $(11111010 - 11110011)$.

The subtraction is changed to addition by taking the 2's complement of the subtrahend (-13) , giving $(+13)$.

$11111010 + 00001101 = 100000111$. Removing the end carry, we obtain the correct answer: $00000111 (+7)$.

Why Signed Binary Numbers

It is worth noting that binary numbers in the signed-complement system are added and subtracted by the same basic addition and subtraction rules as unsigned numbers.

Therefore, **computers need only one common hardware circuit to handle both types of arithmetic**. This consideration has resulted in the signed-complement system being used in virtually all arithmetic units of computer systems.

Binary Coded Decimal-BCD

each decimal digit is represented by its corresponding **four-bit** binary value

Decimal digit	BCD			
	8	4	2	1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

the binary combinations 1010 through 1111 are not used and have no meaning in BCD.

$$(185)_{10} = (0001\ 1000\ 0101)_{\text{BCD}} = (10111001)_2$$

an advantage in the use of decimal numbers, because computer input and output data are generated by people who use the decimal system.

Digital Design

BCD Addition

$$\begin{array}{r}
 4 \quad 0100 \\
 +5 \quad +0101 \\
 \hline
 9 \quad 1001
 \end{array}
 \quad
 \begin{array}{r}
 4 \quad 0100 \\
 +8 \quad +1000 \\
 \hline
 12 \quad 1100 \\
 +0110 \\
 \hline
 10010
 \end{array}
 \quad
 \begin{array}{r}
 8 \quad 1000 \\
 +9 \quad 1001 \\
 \hline
 17 \quad 10001 \\
 +0110 \\
 \hline
 10111
 \end{array}$$

BCD Addition

BCD	1	1		
	0001	1000	0100	184
	+0101	0111	0110	+576
Binary sum	0111	10000	1010	
Add 6	_____	0110	0110	_____
BCD sum	0111	0110	0000	760

Dr. Hany Ahmed Date: 2017

Different Binary Codes

Decimal Digit	BCD 8421	2421	Excess-3	8, 4, -2, -1
0	0000	0000	0011	0000
1	0001	0001	0100	0111
2	0010	0010	0101	0110
3	0011	0011	0110	0101
4	0100	0100	0111	0100
5	0101	1011	1000	1011
6	0110	1100	1001	1010
7	0111	1101	1010	1001
8	1000	1110	1011	1000
9	1001	1111	1100	1111
Unused bit combinations	1010	0101	0000	0001
	1011	0110	0001	0010
	1100	0111	0010	0011
	1101	1000	1101	1100
	1110	1001	1110	1101
	1111	1010	1111	1110

Dr. Hany Ahmed Date: 2017

Gray Code

The **reflected binary code (RBC)**

advantage of the Gray code over the straight binary number sequence is that **only one bit** in the code group **changes** in going from one number to the next.

Decimal	Binary	Gray	Gray as decimal
0	000	000	0
1	001	001	1
2	010	011	3
3	011	010	2
4	100	110	6
5	101	111	7
6	110	101	5
7	111	100	4

Dr. Hany Ahmed Date: 2017


Gray Code

The **reflected binary code (RBC)**


Gray Code	Decimal Equivalent
0000	0
0001	1
0011	2
0010	3
0110	4
0111	5
0101	6
0100	7
1100	8
1101	9
1111	10
1110	11
1010	12
1011	13
1001	14
1000	15

Dr. Hany Ahmed Date: 2017

Binary to Gray Code Conversion


 


 - MSB does not change as a result of conversion
- Start with MSB of binary number and add it to neighboring binary bit to get the next Gray code bit
- Repeat for subsequent Gray coded bits



Dr. Hany Ahmed Date: 2017

Gray Code to Binary Conversion

  

Dr. Hany Ahmed Date: 2017

ASCII Character Code

American Standard Code for Information Interchange (ASCII)

$b_4b_3b_2b_1$	$b_7b_6b_5$							
	000	001	010	011	100	101	110	111
0000	NUL	DLF	SP	0	@	P	~	p
0001	SOH	DC1	!	1	A	Q	a	q
0010	STX	DC2	"	2	B	R	b	r
0011	ETX	DC3	#	3	C	S	c	s
0100	EOF	DC4	\$	4	D	T	d	t
0101	ENO	NAK	%	5	E	U	e	u
0110	ACK	SYN	&	6	F	V	f	v
0111	BEL	ETB	^	7	G	W	g	w
1000	BS	CAN	(8	H	X	h	x
1001	HT	FM)	9	I	Y	i	y
1010	LF	SUB	*	:	J	Z	j	z
1011	VT	ESC	+	;	K	[k	{
1100	FF	FS	:	<	L	\	l	
1101	CR	GS	-	=	M]	m	}
1110	SO	RS	.	>	N	^	n	~
1111	SI	US	/	?	O	_	o	DEL

Dr. Hany Ahmed Date: 2017

Error-Detecting Code

A *parity bit* is an extra bit included with a message to make the total number of 1's either even or odd.

Even Parity Check →

1- No. of One's Even → 0

2- No. of One's Odd → 1

	With even parity	With odd parity
ASCII A = 1000001	01000001	11000001
ASCII T = 1010100	11010100	01010100

Odd Parity Check →

1- No. of One's Even → 1

2- No. of One's Odd → 0

The parity bit is helpful in detecting errors during the transmission of information

Dr. Hany Ahmed Date: 2017

BINARY STORAGE AND REGISTERS

Registers

A *register* is a group of binary cells. A register with n cells can store any discrete quantity of information that contains n bits.


A register with 16 cells can be in one of 2^{16} possible states

Register Transfer

is a basic operation that consists of a transfer of binary information from one set of registers into another set of registers.


Dr. Hany Ahmed Date: 2017

Register Transfer

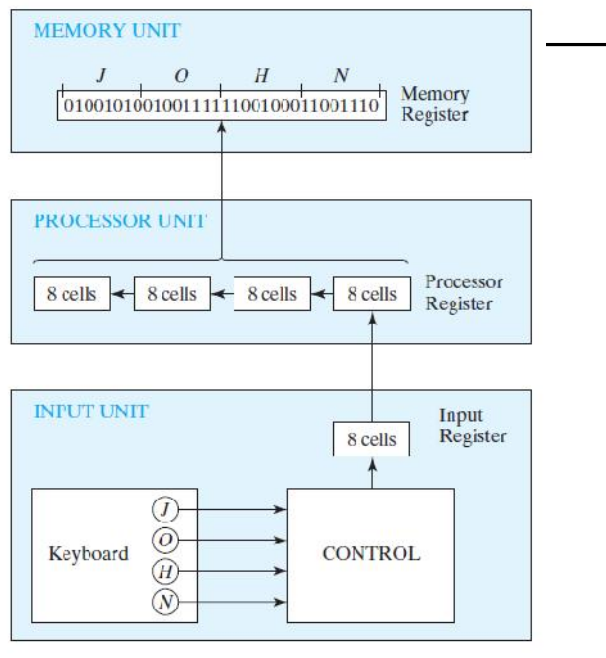


Dr. Hany Ahmed Date: 2017

Register Transfer: Serial I/O

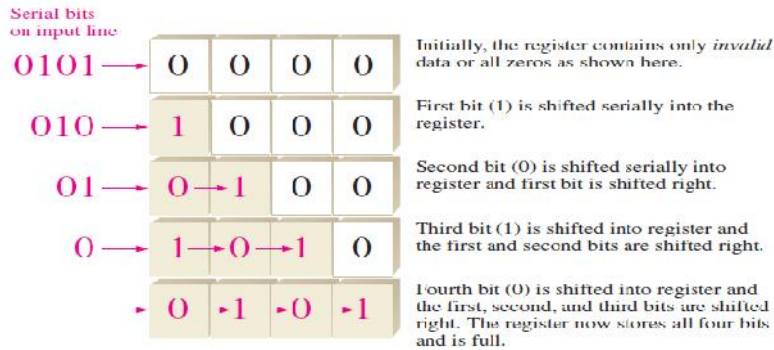

Register Transfer: Parallel I/O

 

Dr. Hany Ahmed Date: 2017

BINARY LOGIC

Binary logic consists of binary variables and a set of logical operations. The variables are designated by letters of the alphabet, such as *A*, *B*, *C*, *x*, *y*, *z*, etc., with each variable having two and only two distinct possible values: 1 and 0. There are three basic logical operations:

AND, OR, and NOT.

Truth Tables of Logical Operations

AND			OR			NOT	
<i>x</i>	<i>y</i>	<i>x · y</i>	<i>x</i>	<i>y</i>	<i>x + y</i>	<i>x</i>	<i>x'</i>
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1		
1	1	1	1	1	1		

Dr. Hany Ahmed Date: 2017


Logic Gates





(a) Two-input AND gate



(b) Two-input OR gate

 

(c) NOT gate or inverter

  

(b) Four-input OR gate



(a) Three-input AND gate

Dr. Hany Ahmed Date: 2017


Logic Gates





(a) Two-input AND gate



(b) Two-input OR gate

 


(c) NOT gate or inverter

  


Dr. Hany Ahmed Date: 2017

Transistor Transistor Logic (TTL)

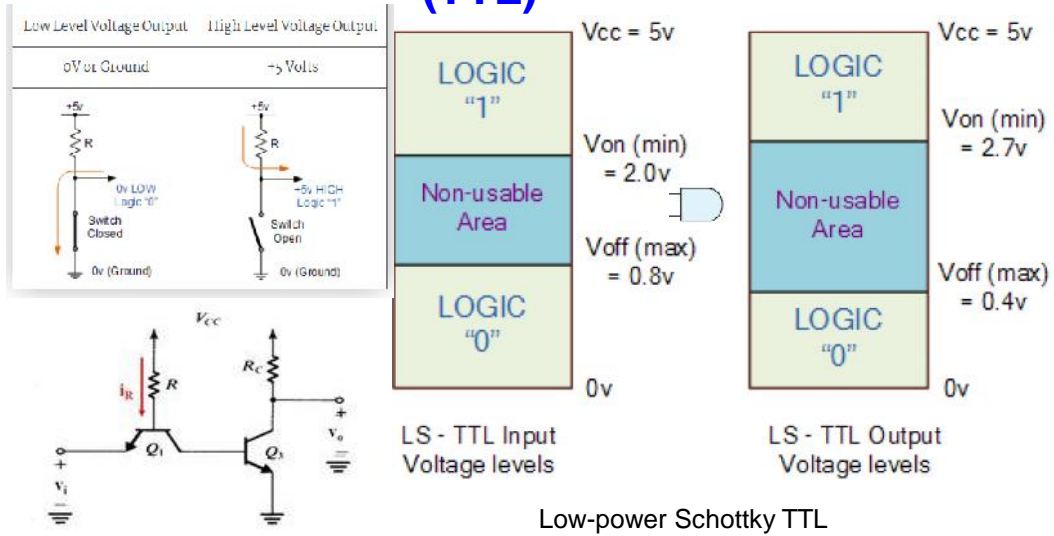

Dr. Hany Ahmed Date: 2017

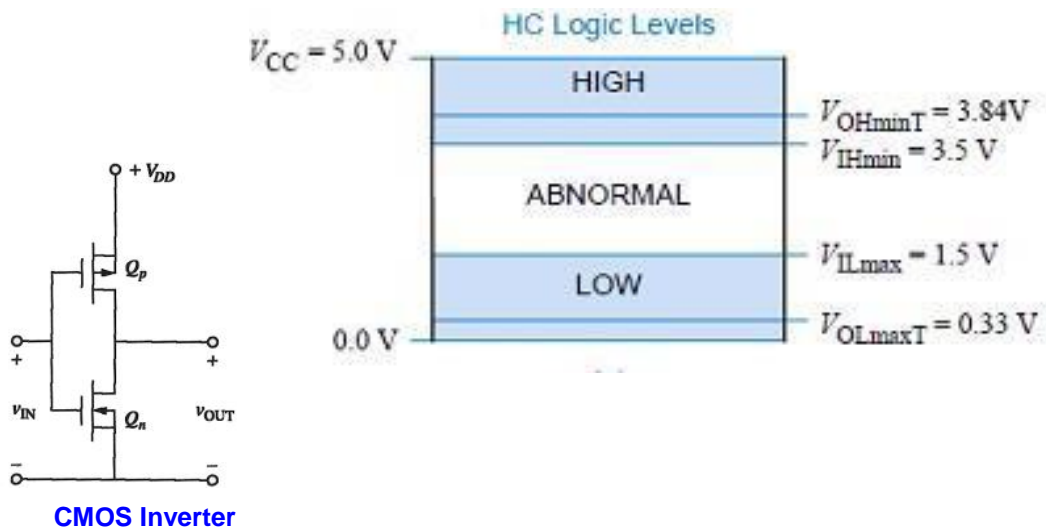Complementary metal-oxide-semiconductor (CMOS)



Dr. Hany Ahmed Date: 2017

Boolean Algebra

1. (a) The structure is closed with respect to the operator $+$.
 (b) The structure is closed with respect to the operator \cdot .
2. (a) The element 0 is an identity element with respect to $+$; that is, $x + 0 = 0 + x = x$.
 (b) The element 1 is an identity element with respect to \cdot ; that is, $x \cdot 1 = 1 \cdot x = x$.
3. (a) The structure is commutative with respect to $+$; that is, $x + y = y + x$.
 (b) The structure is commutative with respect to \cdot ; that is, $x \cdot y = y \cdot x$.
4. (a) The operator \cdot is distributive over $+$; that is, $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$.
 (b) The operator $+$ is distributive over \cdot ; that is, $x + (y \cdot z) = (x + y) \cdot (x + z)$.
5. For every element $x \in B$, there exists an element $x' \in B$ (called the *complement* of x) such that (a) $x + x' = 1$ and (b) $x \cdot x' = 0$.
6. There exist at least two elements $x, y \in B$ such that $x \neq y$.

Dr. Hany Ahmed Date: 2017

Boolean Algebra

Identity

$$0 + x = x \qquad 1 \cdot x = x$$

Commutation

$$x \cdot y = y \cdot x \qquad x + y = y + x$$

Distribution

$$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$$

$$x + (y \cdot z) = (x + y) \cdot (x + z)$$

Complement

$$x + x' = 1 \qquad x \cdot x' = 0$$

Dr. Hany Ahmed Date: 2017

Boolean Algebra

x	y	z	$y + z$	$x \cdot (y + z)$	$x \cdot y$	$x \cdot z$	$(x \cdot y) + (x \cdot z)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

Dr. Hany Ahmed Date: 2017

Basic Theorems

Duality

Postulates and Theorems of Boolean Algebra

Postulate 2	(a) $x + 0 = x$	(b) $x \cdot 1 = x$
Postulate 5	(a) $x + x' = 1$	(b) $x \cdot x' = 0$
Theorem 1	(a) $x + x = x$	(b) $x \cdot x = x$
Theorem 2	(a) $x + 1 = 1$	(b) $x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Postulate 3, commutative	(a) $x + y = y + x$	(b) $xy = yx$
Theorem 4, associative	(a) $x + (y + z) = (x + y) + z$	(b) $x(yz) = (xy)z$
Postulate 4, distributive	(a) $x(y + z) = xy + xz$	(b) $x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a) $(x + y)' = x'y'$	(b) $(xy)' = x' + y'$
Theorem 6, absorption	(a) $x + xy = x$	(b) $x(x + y) = x$

Dr. Hany Ahmed Date: 2017

Basic Theorems

THEOREM 1(a): $x + x = x$.

Statement	Justification
$x + x = (x + x) \cdot 1$	postulate 2(b)
$= (x + x)(x + x')$	5(a)
$= x + xx'$	4(b)
$= x + 0$	5(b)
$= x$	2(a)

Dr. Hany Ahmed Date: 2017

Basic Theorems

THEOREM 6(a): $x + xy = x$.

Statement	Justification
$x + xy = x \cdot 1 + xy$	postulate 2(b)
$= x(1 + y)$	4(a)
$= x(y + 1)$	3(a)
$= x \cdot 1$	2(a)
$= x$	2(b)

Dr. Hany Ahmed Date: 2017

Basic Theorems

DeMorgan's theorem

$$(x + y)' = x'y'$$

Using Duality

De Morgan's Theorem

$$\overline{x \cdot y} = \bar{x} + \bar{y} \Rightarrow x \cdot y = \overline{\bar{x} + \bar{y}}$$

$$\overline{x + y} = \bar{x} \cdot \bar{y} \Rightarrow x + y = \overline{\bar{x} \cdot \bar{y}}$$

x	y	x + y	(x + y)'
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0


x'	y'	x'y'
1	1	1
1	0	0
0	1	0
0	0	0

Dr. Hany Ahmed Date: 2017

Boolean Function

$$F_1 = x + y'z$$

x	y	z	F ₁
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 


Dr. Hany Ahmed Date: 2017

Simplifications of Function

$$F_2 = x'y'z + x'yz + xy'$$

$$= x'z(y' + y) + xy' = x'z + xy'$$

 (a) $F_2 = x'y'z + x'yz + xy'$ (b) $F_2 = xy' + x'z$

Dr. Hany Ahmed Date: 2017

Simplifications of Function

1. $x(x' + y) = xx' + xy = 0 + xy = xy$.
2. $x + x'y = (x + x')(x + y) = 1(x + y) = x + y$.
3. $(x + y)(x + y') = x + xy + xy' + yy' = x(1 + y + y') = x$.
4. $xy + x'z + yz = xy + x'z + yz(x + x')$
 $= xy + x'z + xyz + x'yz$
 $= xy(1 + z) + x'z(1 + y)$
 $= xy + x'z$.
5. $(x + y)(x' + z)(y + z) = (x + y)(x' + z)$, by duality from function 4.

Dr. Hany Ahmed Date: 2017

Complement of a Function

The complement of a function F is F'

$$\begin{aligned}
 (A + B + C)' &= (A + x)' && \text{let } B + C = x \\
 &= A'x' && \text{by theorem 5(a) (DeMorgan)} \\
 &= A'(B + C)' && \text{substitute } B + C = x \\
 &= A'(B'C') && \text{by theorem 5(a) (DeMorgan)} \\
 &= A'B'C' && \text{by theorem 4(b) (associative)}
 \end{aligned}$$

Dr. Hany Ahmed Date: 2017

Complement of a Function

These theorems can be generalized as follows:

$$\begin{aligned}
 (A + B + C + D + \dots + F)' &= A'B'C'D' \dots F' \\
 (ABCD \dots F)' &= A' + B' + C' + D' + \dots + F'
 \end{aligned}$$

Find the complement of the functions $F_1 = x'yz' + x'y'z$

$$\begin{aligned}
 F_1' &= (x'yz' + x'y'z)' = (x'yz')'(x'y'z)' \\
 &= (x + y' + z)(x + y + z')
 \end{aligned}$$

Dr. Hany Ahmed Date: 2017

Canonical and Standard Forms

Minterms and Maxterms

A Boolean function can be expressed algebraically from a given truth table by forming a minterm for each combination of the variables that produces a 1 in the function and then taking the OR of all those terms.

Minterms or Standard Products
Function \rightarrow (Sum of Product)

Maxterms or Standard Sums
Function \rightarrow (Product of Sums)

Dr. Hany Ahmed Date: 2017

Canonical and Standard Forms

Minterms and Maxterms

Minterms and Maxterms for Three Binary Variables

x	y	z	Minterms		Maxterms	
			Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7

Hint: Minterms are the complements of the Maxterms or vice versa

Dr. Hany Ahmed Date: 2017

Canonical and Standard Forms

Minterms or Standard Products

For example

$$f_1 = x'y'z + xy'z' + xyz$$

$$f_2 = x'yz + xy'z + xyz' + xyz$$

Functions of Three Variables

x	y	z	Function f_1	Function f_2
0	0	0	0	m_0
0	0	1	1	m_1
0	1	0	0	m_2
0	1	1	0	m_3
1	0	0	1	m_4
1	0	1	0	m_5
1	1	0	0	m_6
1	1	1	1	m_7

$$f_1 = m_1 + m_4 + m_7$$

$$f_2 = m_3 + m_5 + m_6 + m_7$$

Dr. Hany Ahmed Date: 2017

Canonical and Standard Forms

Maxterms or Standard Sums

For example

$$f_1' = x'y'z' + x'yz' + x'yz + xy'z + xyz'$$

The complement of f_1 is read as

$$f_1 = (x + y + z)(x + y' + z)(x' + y + z')(x' + y' + z)$$

Maxterms				
x	y	z	Term	Designation
0	0	0	$x + y + z$	M_0
0	0	1	$x + y + z'$	M_1
0	1	0	$x + y' + z$	M_2
0	1	1	$x + y' + z'$	M_3
1	0	0	$x' + y + z$	M_4
1	0	1	$x' + y + z'$	M_5
1	1	0	$x' + y' + z$	M_6
1	1	1	$x' + y' + z'$	M_7

$$f_1 = M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6$$

Dr. Hany Ahmed Date: 2017

Canonical and Standard Forms

Boolean functions expressed as a sum of minterms or product of maxterms are said to be in *canonical form*.

The **minterms** whose sum defines the Boolean function are those which give the **1's** of the function in a truth table

Express the Boolean function $F = A + B'C$ as a sum of minterms. The function has three variables: A , B , and C . The first term A is missing two variables; therefore,

$$A = A(B + B') = AB + AB'$$

Dr. Hany Ahmed Date: 2017

Example

Express the Boolean function $F = A + B'C$ as a sum of minterms.

The function has three variables: A , B , and C . The first term A is missing two variables; therefore,

$$A = A(B + B') = AB + AB'$$

This function is still missing one variable, so

$$\begin{aligned} A &= AB(C + C') + AB'(C + C') \\ &= ABC + ABC' + AB'C + AB'C' \end{aligned}$$

Dr. Hany Ahmed Date: 2017

The second term BC is missing one variable; hence,

$$B'C = B'C(A + A') = AB'C + A'B'C$$

Combining all terms, we have But $AB'C$ appears twice ($x + x = x$)

$$F = A + B'C$$

$$= ABC + ABC' + AB'C + AB'C' + A'B'C$$

$$F = A'B'C + AB'C + AB'C + ABC' + ABC$$

$$= m_1 + m_4 + m_5 + m_6 + m_7$$

$$F(A, B, C) = \Sigma(1, 4, 5, 6, 7)$$

The summation symbol stands for the ORing of terms

Dr. Hany Ahmed Date: 2017

Another solution

An alternative procedure for deriving the minterms of a Boolean function is to obtain the truth table of the function directly from the algebraic expression and then read the minterms from the truth table.

Truth Table for $F = A + B'C$

A	B	C	F	
0	0	0	0	m_0
0	0	1	1	m_1
0	1	0	0	m_2
0	1	1	0	m_3
1	0	0	1	m_4
1	0	1	1	m_5
1	1	0	1	m_6
1	1	1	1	m_7

$$F(A, B, C) = \Sigma(1, 4, 5, 6, 7)$$

Dr. Hany Ahmed Date: 2017

Example : Maxterms

Express the Boolean function $F = xy + x'z$ as a product of maxterms

$$\begin{aligned} F &= xy + x'z = (xy + x')(xy + z) \\ &= (x + x')(y + x')(x + z)(y + z) \\ &= (x' + y)(x + z)(y + z) \end{aligned}$$

The function has three variables: x , y , and z . Each OR term is missing one variable; therefore,

$$\begin{aligned} x' + y &= x' + y + zz' = (x' + y + z)(x' + y + z') \\ x + z &= x + z + yy' = (x + y + z)(x + y' + z) \\ y + z &= y + z + xx' = (x + y + z)(x' + y + z) \end{aligned}$$

Dr. Hany Ahmed Date: 2017

Example : Maxterms

Express the Boolean function $F = xy + x'z$ as a product of maxterms

$$\begin{aligned} F &= (x + y + z)(x + y' + z)(x' + y + z)(x' + y + z') \\ &= M_0 M_2 M_4 M_5 \end{aligned}$$

$$F(x, y, z) = \Pi(0, 2, 4, 5)$$

The product symbol denotes the ANDing of maxterms

The **maxterms** whose product defines the Boolean function are those which give the **0's** of the function in a truth table

Dr. Hany Ahmed Date: 2017

Example : Maxterms

Express the Boolean function $F = xy + x'z$ as a product of maxterms

Hint. An alternative procedure for deriving the maxterms of a Boolean function is to obtain the truth table of the function directly from the algebraic expression and then read the maxterms from the truth table.

Truth Table for $F = xy + x'z$

x	y	z		F
0	0	0	M_0	0
0	0	1	M_1	1
0	1	0	M_2	0
0	1	1	M_3	1
1	0	0	M_4	0
1	0	1	M_5	0
1	1	0	M_6	1
1	1	1	M_7	1

$$F(x, y, z) = \Pi(0, 2, 4, 5)$$

Dr. Hany Ahmed Date: 2017

Conversion between Canonical Forms

$$F(A, B, C) = \Sigma(1, 4, 5, 6, 7)$$

This function has a complement that can be expressed as

$$F'(A, B, C) = \Sigma(0, 2, 3) = m_0 + m_2 + m_3$$

Now, if we take the complement of F by DeMorgan's theorem, we obtain F in a different form:

$$F = (m_0 + m_2 + m_3)' = m_0' \cdot m_2' \cdot m_3' = M_0 M_2 M_3 = \Pi(0, 2, 3)$$

$$m_j' = M_j$$

the maxterm with subscript j is a complement of the minterm with the same subscript j and vice versa.

Dr. Hany Ahmed Date: 2017

Minterms and Maxterms of Function F

$$F = xy + x'z$$

Truth Table for $F = xy + x'z$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Diagram showing connections from the F column to Minterms and Maxterms:

- Minterms: 1, 3, 6, 7
- Maxterms: 0, 2, 4, 5


$$F(x, y, z) = \Pi(0, 2, 4, 5)$$

$$F(x, y, z) = \Sigma(1, 3, 6, 7)$$


Dr. Hany Ahmed Date: 2017

Minterms and Maxterms of Functions

$$F_1 = y' + xy + x'yz'$$

 

$$F_2 = x(y' + z)(x' + y + z')$$

 

Dr. Hany Ahmed Date: 2017

Boolean Algebra and Logic Gates

2.7 Other Logic Operations

Truth Tables for the 16 Functions of Two Binary Variables

x	y	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇	F ₈	F ₉	F ₁₀	F ₁₁	F ₁₂	F ₁₃	F ₁₄	F ₁₅
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

Dr. Hany Ahmed Date: 2016


2.7 Other Logic Operations

Boolean Expressions for the 16 Functions of Two Variables


Boolean Functions	Operator Symbol	Name	Comments
$F_0 = 0$		Null	Binary constant 0
$F_1 = xy$	$x \cdot y$	AND	x and y
$F_2 = xy'$	x/y	Inhibition	x, but not y
$F_3 = x$		Transfer	x
$F_4 = x'y$	y/x	Inhibition	y, but not x
$F_5 = y$		Transfer	y
$F_6 = xy' + x'y$	$x \oplus y$	Exclusive-OR	x or y, but not both
$F_7 = x + y$	$x \uparrow y$	OR	x or y
$F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + x'y'$	$(x \oplus y)'$	Equivalence	x equals y
$F_{10} = y'$	y'	Complement	Not y
$F_{11} = x + y'$	$x \supset y$	Implication	If y, then x
$F_{12} = x'$	x'	Complement	Not x
$F_{13} = x' + y$	$x \supset y$	Implication	If x, then y
$F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND
$F_{15} = 1$		Identity	Binary constant 1

Dr. Hany Ahmed Date: 2016

Logic Gates

 

x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

 


x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

Dr. Hany Ahmed Date: 2016

Logic Gates



x	y	F
0	0	0
0	1	1
1	0	1
1	1	0

 

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1

Dr. Hany Ahmed Date: 2016

Logic Gates

The NAND and NOR operators are not associative

$$(x \downarrow y) \downarrow z = [(x + y)' + z]' = (x + y)z' = xz' + yz'$$


$$x \downarrow (y \downarrow z) = [x + (y + z)']' = x'(y + z) = x'y + x'z$$

$$x \downarrow y \downarrow z = (x + y + z)'$$

$$x \uparrow y \uparrow z = (xyz)'$$

Dr. Hany Ahmed Date: 2016

Logic Gates

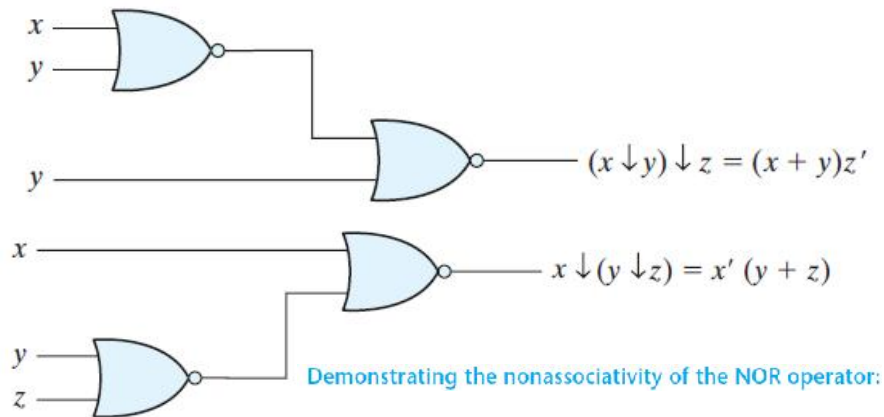


$$(x \downarrow y) \downarrow z \neq x \downarrow (y \downarrow z)$$


The exclusive-OR and equivalence gates are both commutative and associative and can be extended to more than two inputs.

Dr. Hany Ahmed Date: 2016


Logic Gates

 


(a) 3-input NOR gate

 

(b) 3-input NAND gate

 

(a) Using 2-input gates

 

(b) 3-input gate


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(c) Truth table

Signal assignment and logic polarity

x	y	z
L	L	L
L	H	L
H	L	L
H	H	H

(a) Truth table with H and L

 

(b) Gate block diagram



(a) Positive logic

a positive logic system




(b) Negative logic

a negative logic system.

Signal assignment and logic polarity

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1


(c) Truth table for positive logic

 

(d) Positive logic AND gate

x	y	z
1	1	1
1	0	1
0	1	1
0	0	0

(e) Truth table for negative logic

 

(f) Negative logic OR gate

Dr. Hany Ahmed Date: 2016

An integrated circuit (IC)

Small-scale integration (SSI) devices



Up to 10 gates in a single package

Medium-scale integration (MSI)



complexity of approximately 10 to 1,000 gates in a single package

Large-scale integration (LSI) devices



contain thousands of gates in a single package

Very large-scale integration (VLSI) devices



contain millions of gates within a single package.

Dr. Hany Ahmed Date: 2016

Logic Families

Many different logic families of digital integrated circuits

TTL transistor–transistor logic;

ECL emitter–coupled logic; high-speed operation

MOS metal–oxide semiconductor; high component density

CMOS complementary metal–oxide semiconductor.
low power consumption



Low power consumption is essential for VLSI design

Dr. Hany Ahmed Date: 2016

Basic Definitions

Fan-out specifies the number of standard loads that the output of a typical gate can drive without impairing its normal operation.

  Fan-in is the number of inputs available in a gate.




Dr. Hany Ahmed Date: 2016

Basic Definitions


Power dissipation is the power consumed by the gate that must be available from the power supply.

 Propagation delay is the average transition delay time for a signal to propagate from input to output.



Dr. Hany Ahmed Date: 2016


Basic Definitions

 

propagation delay
$$t_p = (t_{pHL} + t_{pLH}) / 2$$

Dr. Hany Ahmed Date: 2016


Propagation delay

 

Dr. Hany Ahmed Date: 2016

Noise margin

 Noise margin is the maximum external noise voltage added to an input signal that does not cause an undesirable change in the circuit output.



$$NM_{II} \equiv V_{OII} - V_{III}$$

$$NM_{IL} \equiv V_{IIL} - V_{OIL}$$

noise margin high


noise margin low

Dr. Hany Ahmed Date: 2016

Standard Load and Waveform

A standard load is usually defined as the amount of current needed by an input of another similar gate in the same family.

Waveform Characteristics

 

duty cycle, which is the ratio of the pulse width (t_w) to the period (T).

$$\text{Duty cycle} = \left(\frac{t_w}{T} \right) 100\%$$

Dr. Hany Ahmed Date: 2016

computer-aided design (CAD)

The designer can choose between

- 1- application-specific integrated circuit (ASIC),
- 2- field-programmable gate array (FPGA),

With each of these devices comes a set of CAD tools that provide the necessary software to facilitate the hardware fabrication of the unit.

An important development in the design of digital systems is the use of a **hardware description language (HDL)**.

- 1- HDLs—Verilog
- 2- VHDL (VHSIC Hardware Description Language)

Very High Speed Integrated Circuit

have been approved as standards by the Institute of Electronics and Electrical Engineers (IEEE) and are in use by design teams worldwide

Dr. Hany Ahmed Date: 2016

Minimization of Logic Functions

We have chips with millions of gates

- Why care about minimizing a function?
- What do a few gates matter?

Basic logic functions replicated thousands of times

- Saving one gate for a memory cell pays off

What is the criterion for “minimization”

Should we minimize

- Number of product terms?
- Number of logic operations?
- Number of variables (literals)?
- Number of wires?
- ...?

systematic approach to minimize expression


→ **Karnaugh maps (K-maps)**

For implementation: minimize number of gates

Dr. Hany Ahmed Date: 2016

Karnaugh Maps

 - Karnaugh maps (K-maps) are *graphical* representations of Boolean functions.
- One *map cell* corresponds to a row in the truth table.
- Also, one map cell corresponds to a **minterm** or a maxterm in the boolean expression
- Multiple-cell areas of the map correspond to standard terms.




Dr. Hany Ahmed Date: 2016

Karnaugh Maps

NOTE: ordering of variables is **IMPORTANT** for $f(x,y)$, x is the row, y is the column. Cell 0 represents $x'y'$; Cell 1 represents $x'y$; etc.

 If a **minterm** is present in the function, then a **1** is placed in the corresponding cell.



Dr. Hany Ahmed Date: 2016

Boolean Function in Karnaugh Map


1s and 0s represent function in Karnaugh map

–1 represent *On-set* ($F=1$), 0 represents *Off-set* ($F=0$)

–Similar to truth table


–0s are typically not shown

Example: And & OR Gates

 


(b) $x + y$

x	y	f
0	0	0
0	1	0
1	0	0
1	1	1

 

(a) xy

x	y	f
0	0	0
0	1	1
1	0	1
1	1	1

 


(b) $x + y$

Dr. Hany Ahmed Date: 2016

Boolean Function in Karnaugh Map

$$F = x' + y'$$

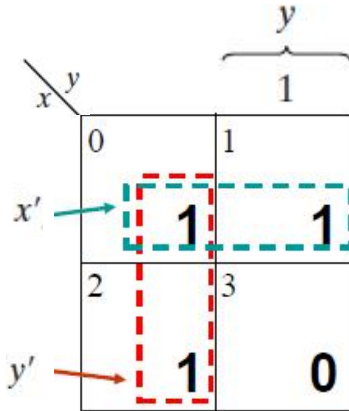

Any two adjacent cells in the map differ by **ONLY** one variable, which appears complemented in one cell and uncomplemented in the other.


• **Example:** $m_0 (=x'y')$ is adjacent to $m_1 (=x'y)$ this means that $x'y' + x'y = x'(y'+y) = x'$

• **Also** $m_0 (=x'y')$ is adjacent to $m_2 (=xy')$ $x'y' + xy' = y'(x'+x) = y'$

Three-Variable K-Map

- Karnaugh map with 3 variables:
 - Two variables on one side, one on the other
 - Note Gray code sequence (single variable change) facilitates grouping of 1-entries into logic blocks
 - Note that the minterms are not arranged in a binary sequence, but similar to **the Gray code**.
 - For simplifying Boolean functions, we must recognize the basic property possessed by adjacent squares.

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

 


Three-Variable K-Map

To clarify this concept, consider the sum of two adjacent squares such as m_5 and m_7 :

$$m_5 + m_7 = xy'z + xyz = xz(y' + y) = xz$$

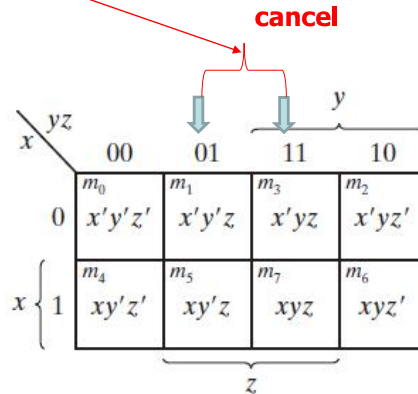
Here, the two squares differ by the variable y , which can be removed when the sum of the two minterms is formed. Thus, any two minterms in adjacent squares (vertically or horizontally, but not diagonally, adjacent) that are ORed together will cause a removal of the dissimilar variable.



Neighboring minterms can be combined:

Three-Variable K-Map

 - Note: variable ordering is (x,y,z); yz specifies column, x specifies row.
- Each cell is adjacent to *three* other cells (left or right or top or bottom or edge wrap)




Three-Variable K-Map

Simplify the Boolean function

$$F(x, y, z) = \Sigma(2, 3, 4, 5)$$
 
$$F(x, y, z) = \Sigma(2, 3, 4, 5) = x'yz' + x'yz + xy'z' + xy'z$$




Three-Variable K-Map

For the Boolean function

$$F = A'C + A'B + AB'C + BC$$


- (a) Express this function as a sum of minterms.
- (b) Find the minimal sum-of-products expression.

$$F(A, B, C) = \Sigma(1, 2, 3, 5, 7)$$

 


Three-Variable K-Map

 
$$\text{Out} = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C$$





$$\text{Out} = \bar{A}\bar{B}$$

 
 
$$\text{Out} = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$



$$\text{Out} = C$$

  


$$\text{Out} = \bar{C}$$


$$\text{Out} = \bar{C}$$

Three-Variable K-Map


Why Minimization?

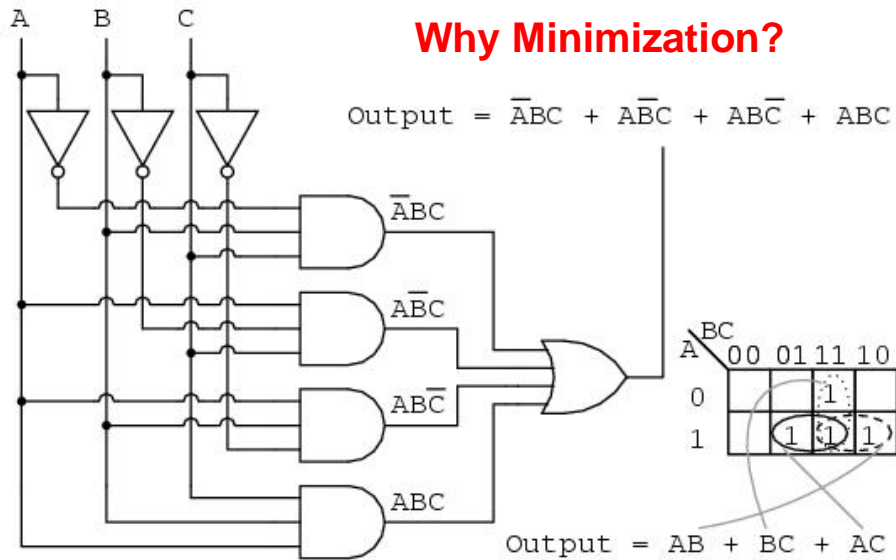

Three-Variable K-Map

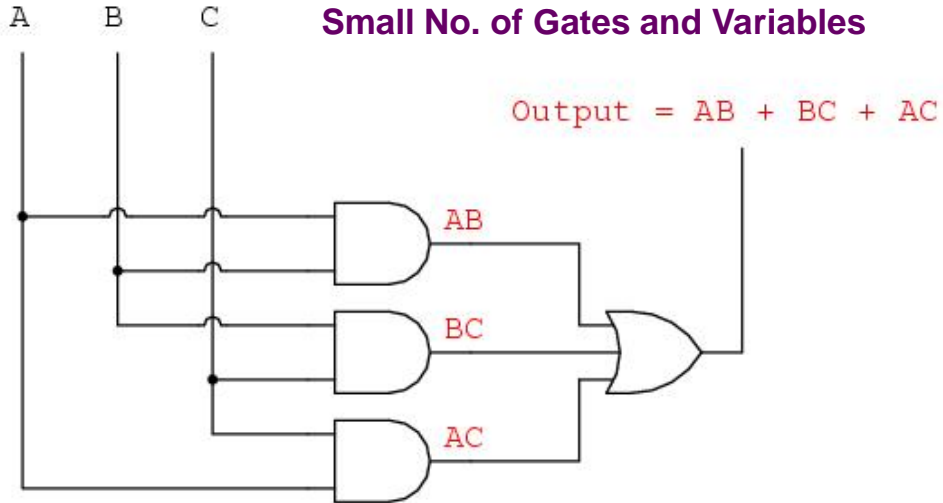


Four-Variable K-Map

 

Four-Variable K-Map


Simplify the Boolean function
 
$$F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$



Dr. Hany Ahmed Date: 2016

Four-Variable K-Map

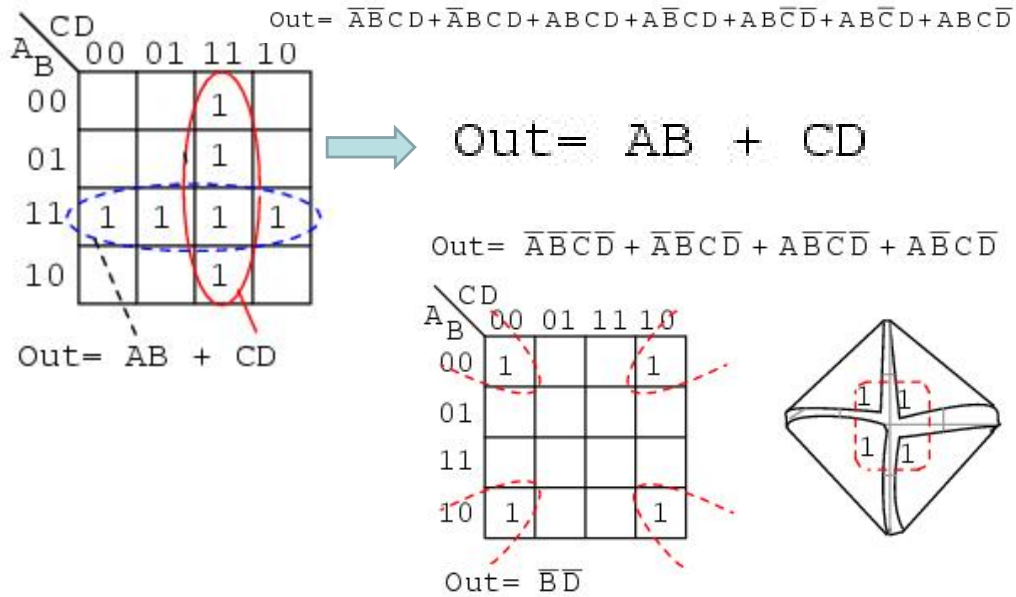

Dr. Hany Ahmed Date: 2016

Four-Variable K-Map

$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}BC\overline{D} + \overline{A}BCD$$

	CD	00	01	11	10
A/B	00	1	1	1	1
	01				
	11				
	10	1	1	1	1

Out = \overline{B}

$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + B\overline{C}\overline{D} + B\overline{C}D + A\overline{B}\overline{C}\overline{D} + A\overline{B}CD$$

	CD	00	01	11	10
A/B	00	1	1	1	1
	01	1			1
	11	1			1
	10	1	1	1	1

	CD	00	01	11	10
A/B	00	1	1	1	1
	01	1			1
	11	1			1
	10	1	1	1	1

Out = $\overline{B} + \overline{D}$

Four-Variable K-Map

$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}BC\overline{D} + \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}CD + AB\overline{C}\overline{D} + ABCD$$


	CD	00	01	11	10
A/B	00	1	1	1	
	01	1	1	1	
	11	1	1	1	
	10				

	CD	00	01	11	10
A/B	00	1	1	1	
	01	1	1	1	
	11	1	1	1	
	10				

	CD	00	01	11	10
A/B	00	1	1	1	
	01	1	1	1	
	11	1	1	1	
	10				

Out = $\overline{A}\overline{C} + \overline{A}D + B\overline{C} + BD$

Four-Variable K-Map

 

Simplification by Boolean Algebra


Out = $\bar{C} + ABCD$

Applying rule $A + \bar{A}B = A + B$ to the $\bar{C} + ABCD$ term

Out = $\bar{C} + ABD$

Dr. Hany Ahmed Date: 2016


Four-Variable K-Map

 

Dr. Hany Ahmed Date: 2016

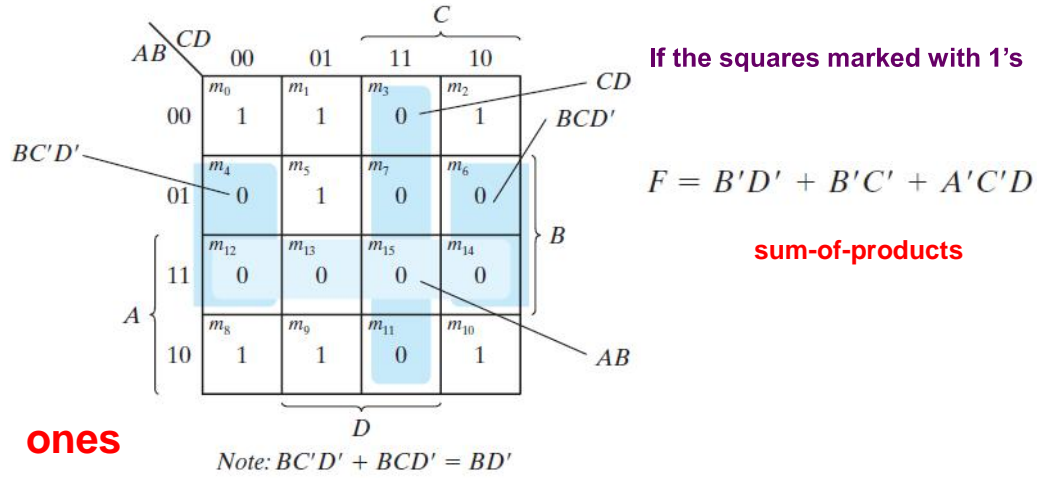Example 3.7


Simplify the following Boolean function into (a) sum-of-products form and (b) product-of-sums form: $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$



Dr. Hany Ahmed Date: 2016

 Example 3.7

Simplify the following Boolean function into (a) sum-of-products form and (b) product-of-sums form:



Dr. Hany Ahmed Date: 2016

Example 3.7

Simplify the following Boolean function into (a) sum-of-products form and (b) product-of-sums form: $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$

		CD		C	
		00	01	11	10
AB	00	m_0 1	m_1 1	m_3 0	m_2 1
	01	m_4 0	m_5 1	m_7 0	m_6 0
A	11	m_{12} 0	m_{13} 0	m_{15} 0	m_{14} 0
	10	m_8 1	m_9 1	m_{11} 0	m_{10} 1
		D			

Zeros

Note: $BC'D' + BCD' = BD'$

If the squares marked with 0's $F' = AB + CD + BD'$


Applying DeMorgan's theorem $F = (A' + B')(C' + D')(B' + D)$

product-of-sums form

Dr. Hany Ahmed Date: 2016

 Example 3.7

Simplify the following Boolean function into (a) sum-of-products form and (b) product-of-sums form:




product-of-sums

Dr. Hany Ahmed Date: 2016

Don't-Care Conditions

Don't Care Cells in the Karnaugh Map >>>>>> **x or ***

 Don't cares in a Karnaugh map, or truth table, may be either 1s or 0s,




Dr. Hany Ahmed Date: 2016

Don't-Care Conditions

Simplify the Boolean function $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$

 which has the don't-care conditions $d(w, x, y, z) = \Sigma(0, 2, 5)$



Dr. Hany Ahmed Date: 2016

Don't-Care Conditions

$$F(w, x, y, z) = yz + w'x' = \Sigma(0, 1, 2, 3, 7, 11, 15)$$

$$F(w, x, y, z) = yz + w'z = \Sigma(1, 3, 5, 7, 11, 15)$$

It is also possible to obtain a simplified product-of-sums expression for the function. In this case, the only way to **combine the 0's** is to include don't-care minterms 0 and 2 with the 0's to give a simplified complemented function:

$$F' = z' + wy'$$



$$F(w, x, y, z) = z(w' + y) = \Sigma(1, 3, 5, 7, 11, 15)$$

Dr. Hany Ahmed Date: 2016


Tri-State-Buffers

Tri-state-buffer


is actually a "variable resistor"

  

 The resistance of the yellow substance can change depending of the value of the control signal



Works like:

 

Works like:



Dr. Hany Ahmed Date: 2016

Digital Design CH 3 Nand and Nor Implementation

Nand and Nor Implementation


- Digital circuit are frequently constructed with **NAND or NOR** gates rather than AND and OR gates.
- NAND and NOR gates are **easier to fabricate with electronic components** and are the basic gates used in all **IC digital logic families**.

NAND Circuits

FAIRCHILD
SEMICONDUCTOR

October 1967
Revised May 2002

MM74C00 • MM74C02 • MM74C04
Quad 2-Input NAND Gate •
Quad 2-Input NOR Gate •
Hex Inverter



General Description
The MM74C00, MM74C02, and MM74C04 logic gates employ complementary MOS (CMOS) to achieve wide power supply operating range, low power consumption, high noise immunity and symmetric controlled rise and fall times. With features such as this the 74C logic family is close to ideal for use in digital systems. Function and pin out compatibility with series 74 devices minimizes design time for those designers already familiar with the standard 74 logic family.
All inputs are protected from damage due to static discharge by diode clamps to V_{CC} and GND.


Features

- Wide supply voltage range: 3V to 15V
- Guaranteed noise margin: 1V
- High noise immunity: $0.4C V_{CC}$ (typ.)
- Low power consumption: 10 nW/package (typ.)
- Low power: TTL compatibility.
Fan out of 2 driving 74L.

Dr. Hany Ahmed Date: 2016

Digital Design


Logic operations with NAND gates

 

Dr. Hany Ahmed Date: 2016

Logic operations with NAND gates


NAND Circuits

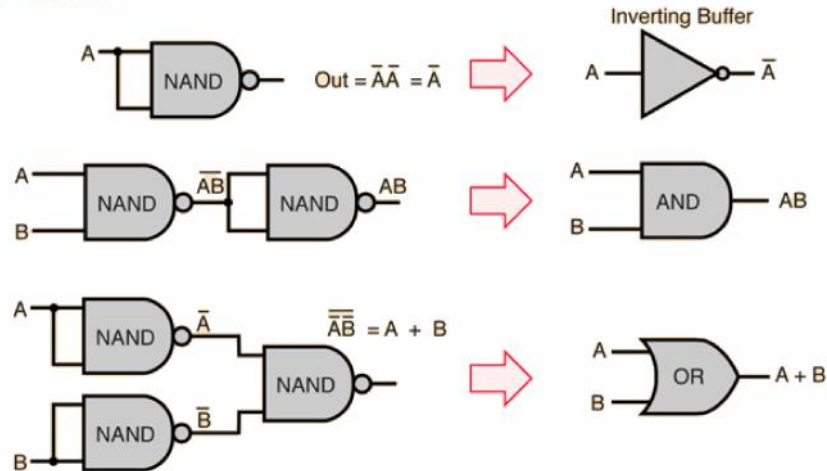

Dr. Hany Ahmed Date: 2016

Logic operations with NAND gates

 Two graphic symbols for a three-input NAND gate




The implementation of Boolean functions with NAND gates requires that the functions be in sum-of-products form.

Dr. Hany Ahmed Date: 2016


Two-Level Implementation

Example Implement


$$F = AB + CD$$

 

(a)

 

(b)

 


(c)

Dr. Hany Ahmed Date: 2016

Logic operations with NAND gates

Implement the following Boolean function with NAND gates:

$$F(x, y, z) = (1, 2, 3, 4, 5, 7)$$

 

$$F = xy' + x'y + z$$

$$F = xy' + x'y + z$$



(a)

Dr. Hany Ahmed Date: 2016

Logic operations with NAND gates

Implement the following Boolean function with NAND gates:


$$F = xy' + x'y + z$$

  


Dr. Hany Ahmed Date: 2016

Multilevel NAND Circuits

$$F = A(CD + B) + BC'$$

 


(a) AND-OR gates

 

(b) NAND gates


Dr. Hany Ahmed Date: 2016

Nor Implementation

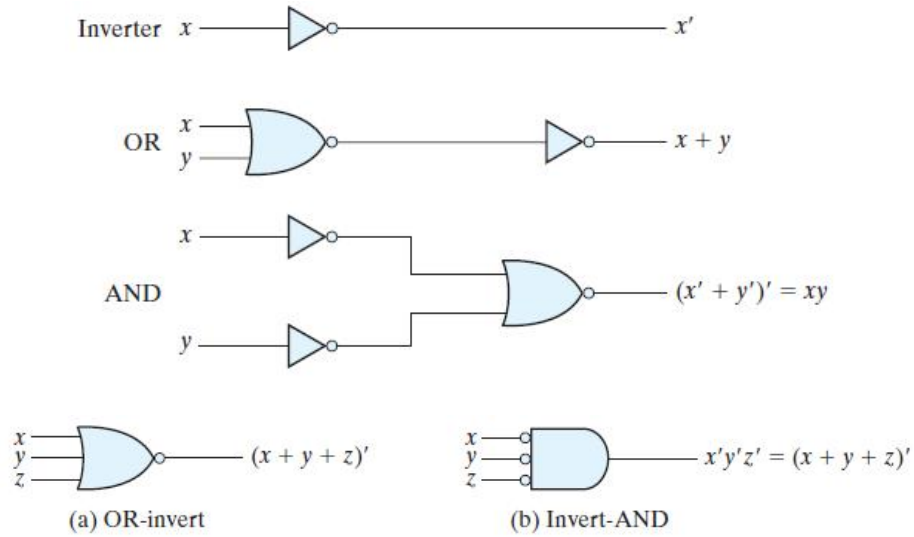

Dr. Hany Ahmed Date: 2016


Nand and Nor Implementation

 

Nand and Nor Implementation

NOR Circuits

Implementing $F = (A + B)(C + D)E$

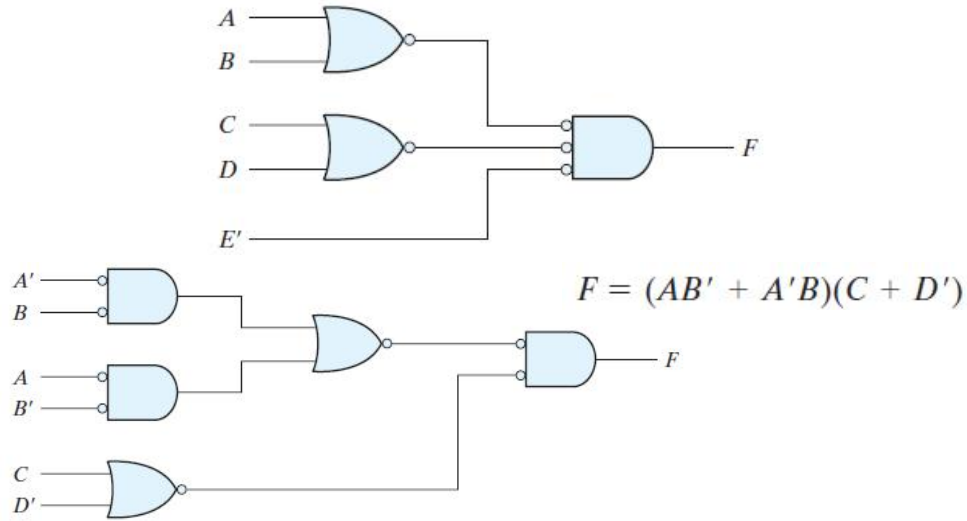

Other Two Level Implementation

AND-OR

OR-AND

NAND-NAND


NOR-NOR

NOR-OR

NAND-AND

OR-NAND


AND-NOR

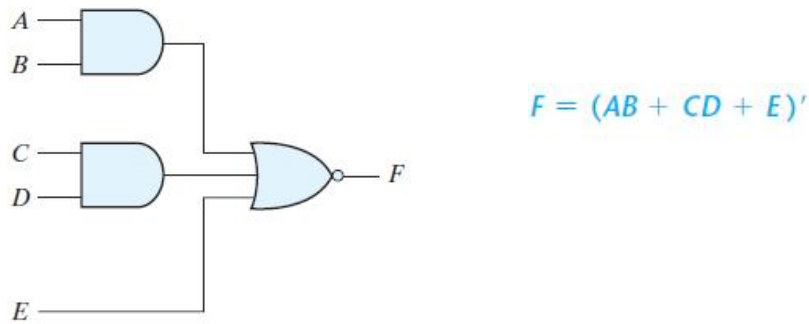


(a) AND-NOR

Other Two Level Implementation

$$F = (AB + CD + E)'$$

 


(b) AND-NOR

 


(c) NAND-AND

Other Two Level Implementation


$$F = [(A + B)(C + D)E]'$$

 

(a) OR-NAND

 


(b) OR-NAND

 

(c) NOR-OR

Nand and Nor Implementation

 Example $F' = x'y + xy' + z$
 $F = (x'y + xy' + z)'$



Dr. Hany Ahmed Date: 2016

The exclusive-OR (XOR)

$$x \oplus y = xy' + x'y$$

The following identities apply to the exclusive-OR operation:

$$x \oplus 0 = x$$

$$x \oplus 1 = x'$$

$$x \oplus x = 0$$

$$x \oplus x' = 1$$

$$x \oplus y' = x' \oplus y = (x \oplus y)'$$

the exclusive-OR operations both commutative and associative;


$$A \oplus B = B \oplus A$$

and


$$(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$$

Dr. Hany Ahmed Date: 2016

The exclusive-OR (XOR)

 

(a) Exclusive-OR with AND-OR-NOT gates

 

(b) Exclusive-OR with NAND gates


Dr. Hany Ahmed Date: 2016

Odd Function

$$\begin{aligned}
 A \oplus B \oplus C &= (AB' + A'B)C' + (AB + A'B')C \\
 &= AB'C' + A'BC' + ABC + A'B'C \\
 &= \Sigma(1, 2, 4, 7)
 \end{aligned}$$

		B			
		00	01	11	10
A	0	m_0	m_1 1	m_3	m_2 1
	1	m_4 1	m_5	m_7 1	m_6
		C			

 (a) Odd function $F = A \oplus B \oplus C$




(a) 3-input odd function


Dr. Hany Ahmed Date: 2016

Odd Function
 
$$\begin{aligned}
 A \oplus B \oplus C \oplus D &= (AB' + A'B) \oplus (CD' + C'D) \\
 &= (AB' + A'B)(CD + C'D') + (AB + A'B')(CD' + C'D) \\
 &= \Sigma(1, 2, 4, 7, 8, 11, 13, 14)
 \end{aligned}$$



 (a) Odd function $F = A \oplus B \oplus C \oplus D$



(b) Even function $F = (A \oplus B \oplus C \oplus D)'$


Dr. Hany Ahmed Date: 2016

Parity Generation and Checking

Even-Parity-Generator Truth Table

Three-Bit Message			Parity Bit
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$P = x \oplus y \oplus z$$

 

(a) 3-bit even parity generator

Even Parity Check →

1- No. of One's Even → 0


2- No. of One's Odd → 1

Dr. Hany Ahmed Date: 2016

CH 4 combinational circuit:

Logic circuits can be classified as either

 1- Combinational Logic Circuits
 — the output(s) depend only on the input(s) at any specific time and not on any previous input(s).



An example of the two concepts is a television remote control. You can enter a number and the output (a particular television channel) depends only on the number entered. It does not matter what channels been viewed previously. So the relationship between the input (a number) and the output is combinational.


2- Sequential Logic Circuits — the output(s) depend both on previous and current input(s).

The remote control also has inputs for stepping either up or down one channel. When using this input method, the channel selected depends on what channel has been previously selected and the sequence of up/down button pushes. The channel up/down buttons illustrate a sequential input/output relationship.

CH 4 combinational circuit: Code Conversion BCD to Excess-3

Truth Table for Code Conversion Example


Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

 

CH 4 combinational circuit: Code Conversion BCD to Excess-3

Truth Table for Code Conversion Example

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

 


Dr. Hany Ahmed Date: 2016

CH 4 combinational circuit: Code Conversion BCD to Excess-3

Truth Table for Code Conversion Example

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

 


Dr. Hany Ahmed Date: 2016

CH 4 combinational circuit: Code Conversion BCD to Excess-3

Truth Table for Code Conversion Example

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

 

Dr. Hany Ahmed Date: 2016

Code Conversion BCD to Excess-3


$$z = D'$$

$$y = CD + C'D' = CD + (C + D)'$$

$$x = B'C + B'D + BC'D' = B'(C + D) + BC'D'$$

$$= B'(C + D) + B(C + D)'$$


$$w = A + BC + BD = A + B(C + D)$$

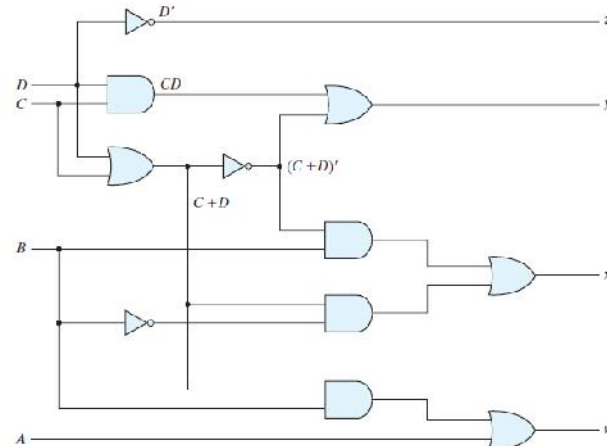

Dr. Hany Ahmed Date: 2016

CH 4 combinational circuit:



Half Adder (2 bit)

 

x_i	y_i	Carry _{i+1}	Sum _i
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Half Adder


x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

  

Dr. Hany Ahmed Date: 2016



CH 4 combinational circuit:

Full Adder (3 bit)

 

Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

  

$$S = x'y'z + x'yz' + xy'z' + xyz$$


$$C = xy + xz + yz$$

Dr. Hany Ahmed Date: 2016

CH 4 combinational circuit: Full Adder (3 bit)

$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy + xz + yz$$

 


Dr. Hany Ahmed Date: 2016

CH 4 combinational circuit: Full Adder (3 bit)

$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy + xz + yz$$

 

$$S = z \oplus (x \oplus y)$$

$$= z'(xy' + x'y) + z(xy' + x'y)'$$

$$= z'(xy' + x'y) + z(xy + x'y')$$

$$= xy'z' + x'yz' + xyz + x'y'z$$

$$Carry_{i+1} = x_i \cdot y_i + Carry_i \cdot x'_i \cdot y_i + Carry_i \cdot x_i \cdot y'_i$$


$$= x_i \cdot y_i + Carry_i \cdot (x'_i \cdot y_i + x_i \cdot y'_i)$$

$$= x_i \cdot y_i + Carry_i \cdot (x_i \oplus y_i)$$

Dr. Hany Ahmed Date: 2016

CH 4 combinational circuit: Full Adder (3 bit)

$$S = z \oplus (x \oplus y)$$

 

Dr. Hany Ahmed Date: 2016

TASKs

1- Learning MULTISIM 14 Software.



2- Implementing the Half and Full Adders
using Multisim.


Dr. Hany Ahmed Date: 2016

1- Adders**Half Adder**


- 2 Inputs (A & B)
- 2 Outputs (Sum & C_{out})
- Used for LSB only

 **Full Adder**

- 3 Inputs (A, B, C_{in})
- 2 Outputs (Sum & C_{out})
- Used for all other bits




Dr. Hany Ahmed Date: 2016

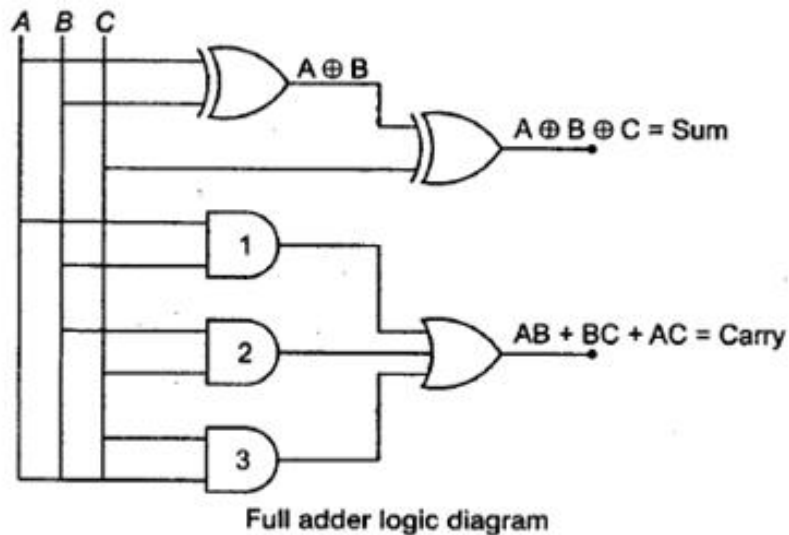Full Adder Circuit

Dr. Hany Ahmed Date: 2016


Full Adder Circuit

- Full adder logic diagram

 

Dr. Hany Ahmed Date: 2016

 Implementation of Full Adder with Two Half Adders




Full Adder

$$S = (A \oplus B) \oplus C_{in}$$

$$C_{out} = AB + (A \oplus B)C_{in}$$

Dr. Hany Ahmed Date: 2016

 Implementation of Full Adder with Two Half Adders




Dr. Hany Ahmed Date: 2016

Four-bit Adder

To demonstrate with a specific example, consider the two binary numbers $A = 1011$ and $B = 0011$. Their sum $S = 1110$ is formed with the four-bit adder as follows:

0	1	1	0	C_i	$A = 1011$	C_3	C_2	C_1	C_0
1	0	1	1	A_i	$B = 0011$	A_3	A_2	A_1	A_0
0	0	1	1	B_i		B_3	B_2	B_1	B_0
1	1	1	0	S_i		S_3	S_2	S_1	S_0
0	0	1	1	C_{i+1}		C_4			0

 

Dr. Hany Ahmed Date: 2016

Subtraction with Complements

The subtraction of two n -digit unsigned numbers $M - N$ in base r can be done as follows:

1. Add the minuend M to the r 's complement of the subtrahend N . Mathematically, $M + (r^n - N) = M - N + r^n$.
2. If $M \geq N$, the sum will produce an end carry r^n , which can be discarded; what is left is the result $M - N$.
3. If $M < N$, the sum does not produce an end carry and is equal to $r^n - (N - M)$, which is the r 's complement of $(N - M)$. To obtain the answer in a familiar form, take the r 's complement of the sum and place a negative sign in front.

The following examples illustrate the procedure:

Dr. Hany Ahmed Date: 2016

Subtraction with Complements

Given the two binary numbers $X = 1010100$ and $Y = 1000011$, perform the subtraction (a) $X - Y$ and (b) $Y - X$ by using 2's complements.

$$\begin{array}{r}
 \text{(a)} \quad X = \quad 1010100 \quad 84 \\
 \quad \quad 2\text{'s complement of } Y = + \quad \underline{0111101} \quad 67 \\
 \quad \quad \quad \quad \quad \text{Sum} = \quad 10010001 \\
 \quad \quad \quad \quad \quad \text{Discard end carry } 2^7 = - \quad \underline{10000000} \\
 \quad \quad \quad \quad \quad \text{Answer: } X - Y = \quad 0010001 \quad 17
 \end{array}$$

Dr. Hany Ahmed Date: 2016

Subtraction with Complements


Given the two binary numbers $X = 1010100$ and $Y = 1000011$, perform the subtraction
(a) $X - Y$ and **(b)** $Y - X$ by using 2's complements.

$$\begin{array}{r}
 \text{(b)} \qquad \qquad \qquad Y = \quad 1000011 \\
 \qquad \qquad \qquad \qquad \qquad \quad 2\text{'s complement of } X = + \quad \underline{0101100} \\
 \qquad \qquad \qquad \qquad \qquad \quad \text{Sum} = \quad 1101111
 \end{array}$$

There is no end carry. Therefore, the answer is $Y - X = -(2^7 \text{ complement of } 1101111) = -0010001$

Dr. Hany Ahmed Date: 2016

Four-bit Adder-Subtractor

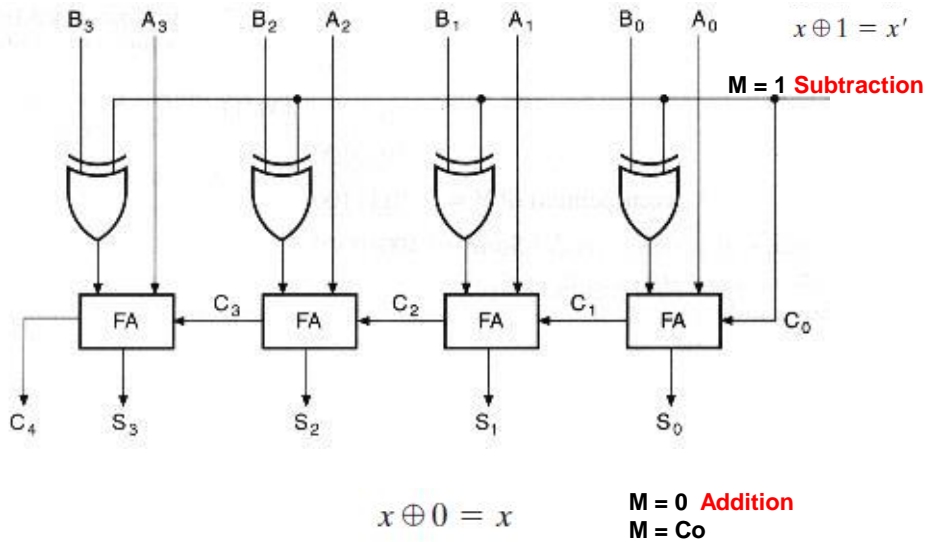

Dr. Hany Ahmed Date: 2016

Unsigned Numbers

C4 End Carry	Case Addition	Case Subtraction
0	Correct (N) bits	The answer is negative and the 2's complement (N) bits
1	Overflow (N+1) bits	Discard the End Carry (N) bits

Dr. Hany Ahmed Date: 2016

Signed Binary Numbers

1- the signed-magnitude

The representation: the sign with a bit placed in the leftmost position of the number. The convention is to make the sign bit 0 for positive and 1 for negative.

For example,
the string of bits 01001 can be considered as 9 (unsigned binary) or
as +9 (signed binary)

The string of bits 11001 represents the binary equivalent of 25 when considered as an unsigned number and the binary equivalent of -9 when considered as a signed number

referred to as the signed-magnitude

Dr. Hany Ahmed Date: 2016

2- the signed-Complement system

The complement will always start with a 1, indicating a negative number. The signed-complement system can use either the 1's or the 2's complement, but the 2's complement is the most common.


there are three different ways to represent -9 with eight bits

signed-magnitude representation: -9	<u>1</u> 0001001
signed-1's-complement representation:	<u>1</u> 1110110
signed-2's-complement representation:	<u>1</u> 1110111
signed-magnitude representation: +9	0 <u>0</u> 001001

The representation: the sign with a bit placed in the leftmost position of the number. The convention is to make the sign bit 0 for positive and 1 for negative.


Dr. Hany Ahmed Date: 2016

 Four-bit adder-subtractor with overflow detection



Dr. Hany Ahmed Date: 2016


Two-bit by two-bit binary multiplier

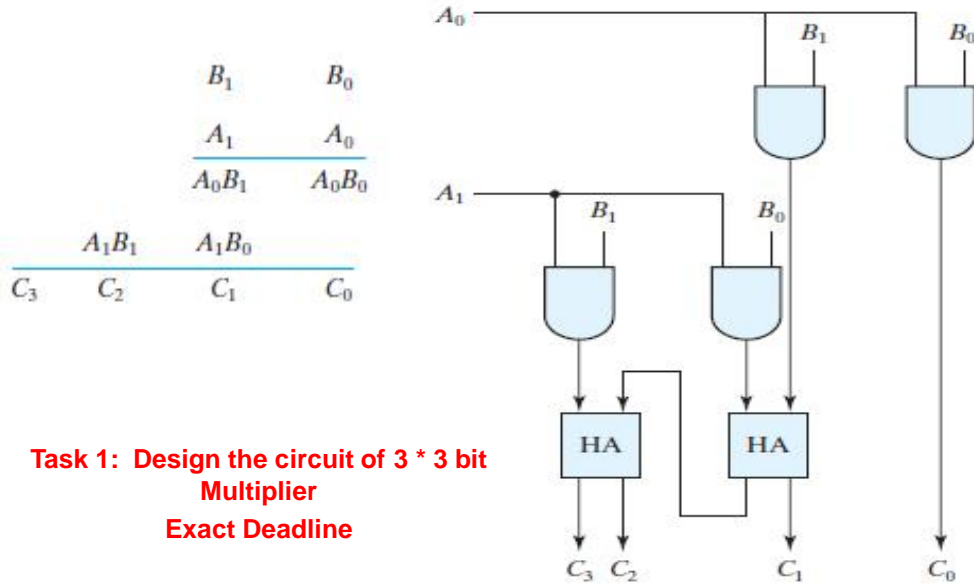

Dr. Hany Ahmed Date: 2016

Magnitude Comparator

 magnitude comparator is a combinational circuit that compares two numbers A and B and determines their relative magnitudes. The outcome of the comparison is specified by three binary variables that indicate whether $A > B$, $A = B$, or $A < B$.



Dr. Hany Ahmed Date: 2016

Single Bit Magnitude Comparator

A comparator used to compare two bits, i.e., two numbers each of single bit is called a single bit comparator. It consists of two inputs for allowing two single bit numbers and three outputs to generate less than, equal and greater than comparison outputs.

A_0	B_0	L	E	G
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0



The truth table for the single bit comparator is given below. When $A_0 B_0 = 00$ & 11 , both inputs are equal, therefore $A=B$ output will be high. When $A_0 B_0 = 01$, B is more than A and hence AB is active.

Dr. Hany Ahmed Date: 2016

Single Bit Magnitude Comparator

A_0	B_0	L	E	G
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0


$$A_0 < B_0: L = \overline{A_0} B_0$$

$$A_0 = B_0: E = \overline{A_0} \overline{B_0} + A_0 B_0$$

$$A_0 > B_0: G = A_0 \overline{B_0}$$

By using these Boolean expressions, we can implement a logic circuit for this comparator using two AND gates, one NOT gate and one **Ex-NOR gate** as shown

 It is to be noted that E can be realized as $\overline{L + G}$.



Dr. Hany Ahmed Date: 2016

Magnitude 4 Bit Comparator

magnitude comparator is a combinational circuit that compares two numbers A and B and determines their relative magnitudes. The outcome of the comparison is specified by three binary variables that indicate whether $A > B$, $A = B$, or $A < B$.

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

can be expressed logically with an exclusive-NOR function as

$$x_i = A_i B_i + A_i' B_i' \quad \text{for } i = 0, 1, 2, 3$$

where $x_i = 1$ only if the pair of bits in position i are equal (i.e., if both are 1 or both are 0).

Dr. Hany Ahmed Date: 2016

Magnitude 4 Bit Comparator

E: Equal

$$(A = B) = x_3 x_2 x_1 x_0$$

G: Greater


$$(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$$

L: Less Than

$$(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$$

Dr. Hany Ahmed Date: 2016

Magnitude 4 Bit Comparator

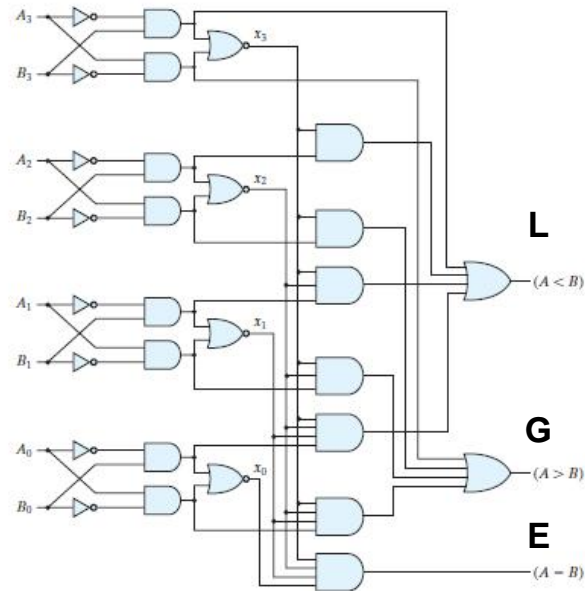

Dr. Hany Ahmed Date: 2016



TASK 2

Design Magnitude comparator: 2-Bit Comparator

TASK 3

Design BCD to 7 segment

TASKs

1- Learning MULTISIM 14 Software.




2- Implementing the BCD to 7 segment and multipliers.

Dr. Hany Ahmed Date: 2016

7 Segment Display and Decoders

BCD to Seven Segment

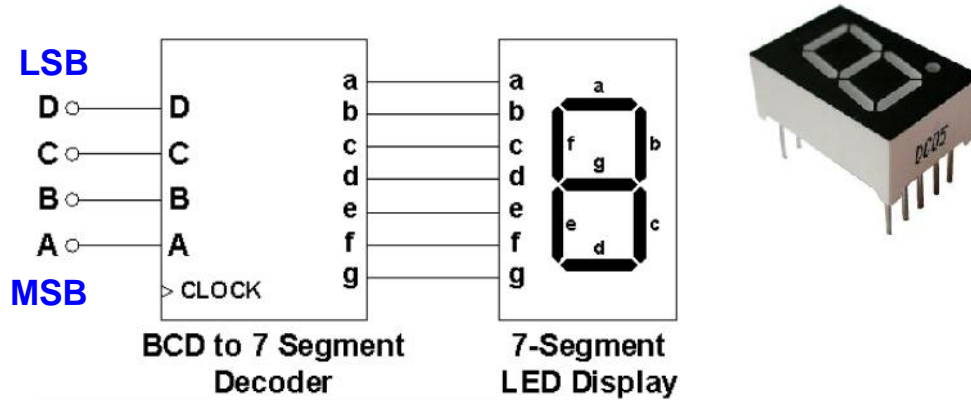

Dr. Hany Ahmed Date: 2016

BCD to Seven Segment


 


Figure 3 BCD-to-Seven segment decoder

 

Dr. Hany Ahmed Date: 2016

BCD to Seven Segment

 


FIGURE 3: Seven segment display format showing arrangement of segments.


 


FIGURE 4 : Display of decimal digits with a 7-segment device.

Dr. Hany Ahmed Date: 2016

Decimal Digit	Input lines				Output lines							Display pattern
	A	B	C	D	a	b	c	d	e	f	g	
0	0	0	0	0	1	1	1	1	1	1	0	
1	0	0	0	1	0	1	1	0	0	0	0	
2	0	0	1	0	1	1	0	1	1	0	1	
3	0	0	1	1	1	1	1	1	0	0	1	
4	0	1	0	0	0	1	1	0	0	1	1	
5	0	1	0	1	1	0	1	1	0	1	1	
6	0	1	1	0	1	0	1	1	1	1	1	
7	0	1	1	1	1	1	1	0	0	0	0	
8	1	0	0	0	1	1	1	1	1	1	1	
9	1	0	0	1	1	1	1	1	0	1	1	

 


Dr. Hany Ahmed Date: 2016



Table 2.4.2


Decimal	BCD Inputs				7 Segment Outputs						
	D	C	B	A	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
10	X	X	X	X	0	0	0	0	0	0	0
11	X	X	X	X	0	0	0	0	0	0	0
12	X	X	X	X	0	0	0	0	0	0	0
13	X	X	X	X	0	0	0	0	0	0	0
14	X	X	X	X	0	0	0	0	0	0	0
15	X	X	X	X	0	0	0	0	0	0	0

 

Dr. Hany Ahmed Date: 2016




BCD to Seven Segment

 

Dr. Hany Ahmed Date: 2016

BCD to Seven Segment

 TASK 3
Design BCD to 7
segment
Exact Deadline




Dr. Hany Ahmed Date: 2016

Decoders

A *decoder* is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines.

Example 3 * 8 Decoder

 Examples
 2*4
 3*8
 4*16
 5 * 32
 Decoder



Dr. Hany Ahmed Date: 2016


Decoders

Truth Table of a Three-to-Eight-Line Decoder

Inputs			Outputs							
<i>x</i>	<i>y</i>	<i>z</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃	<i>D</i> ₄	<i>D</i> ₅	<i>D</i> ₆	<i>D</i> ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


Dr. Hany Ahmed Date: 2016

Decoders

 


Dr. Hany Ahmed Date: 2016

2* 4 Decoder with Enable Active High

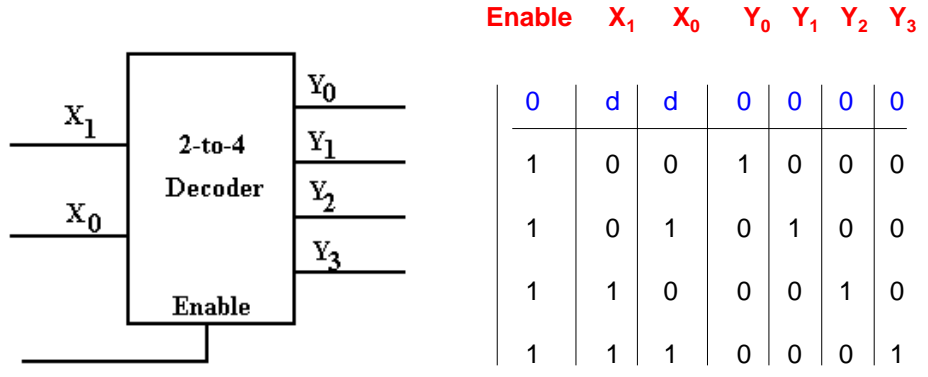

Dr. Hany Ahmed Date: 2016

2* 4 Decoder with Enable Active Low

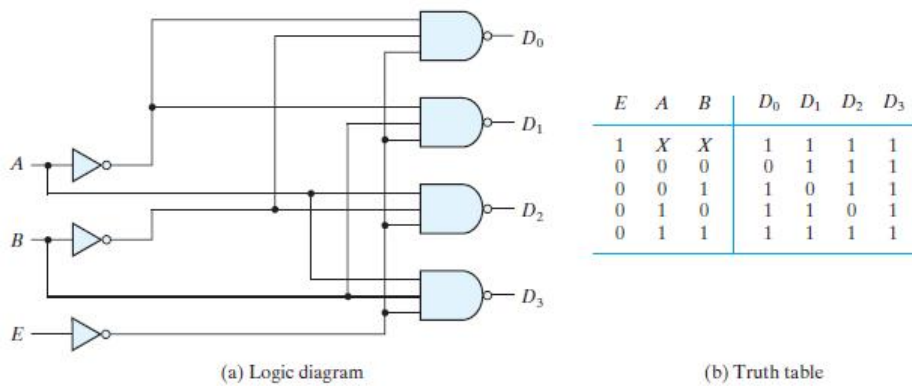


(a) Logic diagram

(b) Truth table

4x16 decoder constructed with two 3x8 decoders

Dr. Hany Ahmed Date: 2016


4*16 Decoders by using 3*8

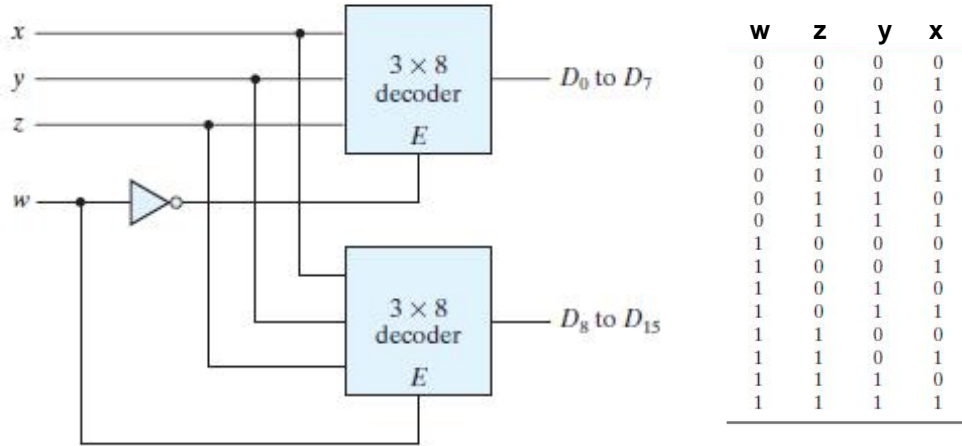

4 × 16 decoder constructed with two 3 × 8 decoders

Dr. Hany Ahmed Date: 2016

 Implementation of a full adder with a decoder



Implementation of a full adder with a decoder

Dr. Hany Ahmed Date: 2016



CH 4 : Combinational Circuit

Encoders, Multiplexers, and Three State Gates.


Dr. Hany Ahmed Date: 2017



Decoders Applications



 Need to activate only one product:
-1: activated (product released)
-0: not activated
•Only **one slot** can be activated at a time.
Machine It could be modeled as follows




Dr. Hany Ahmed Date: 2017



Encoders

An encoder is a digital circuit that performs the inverse operation of a decoder. An encoder has 2^n (or fewer) input lines and n output lines.

 The output lines generate the binary equivalent of the input line whose value is 1.



Dr. Hany Ahmed Date: 2017



8 * 3 Encoder

Truth Table of an Octal-to-Binary Encoder

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$z = D_1 + D_3 + D_5 + D_7$$


$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

Dr. Hany Ahmed Date: 2017



8 * 3 Encoder

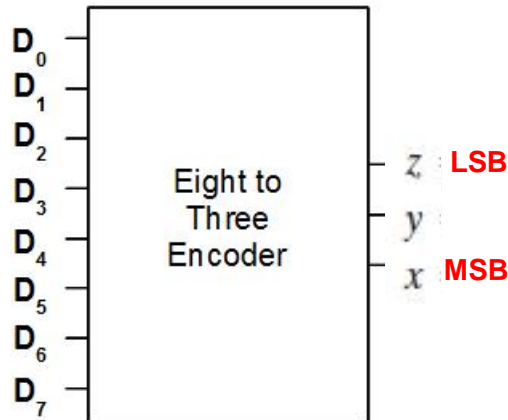

$$z = D_1 + D_3 + D_5 + D_7$$


$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

Dr. Hany Ahmed Date: 2017



8 * 3 Encoder

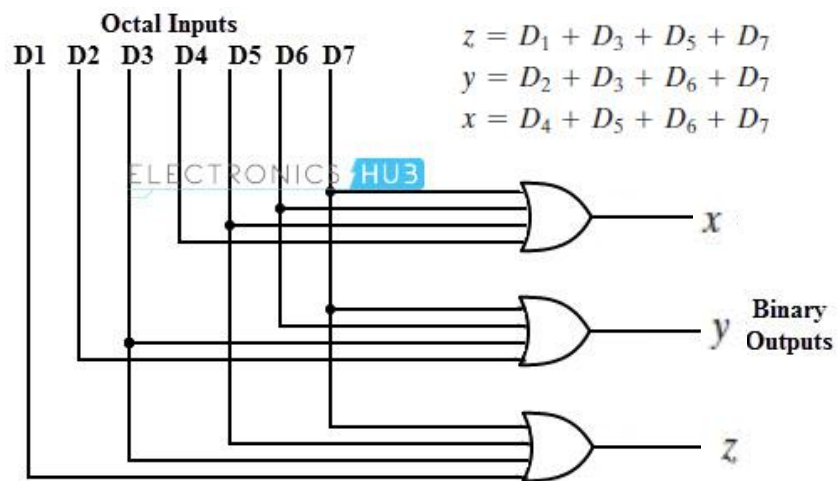


Dr. Hany Ahmed Date: 2017




Multiplexers

Making Connections

 - Direct point-to-point connections between gates
- Wires we've seen so far
- Route one of many inputs to a single output --- multiplexer
- Route a single input to one of many outputs --- demultiplexer



Multiplexer

 

Demultiplexer



Multiplexers


A multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line. The selection of a particular input line is controlled by a set of selection lines. Normally, there are 2^n input lines and n selection lines whose bit combinations determine which input is selected.

• Multiplexers: general concept


- 2^n data inputs, n control inputs (called "selects"), 1 output
- Used to connect 2^n points to a single point
- Control signal pattern forms binary index of input connected to output



2*1 Multiplexer

 

s	I ₁	I ₀	y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


 


$$Y = S' I_0 + S I_1$$

Dr. Hany Ahmed Date: 2017



4*1 Multiplexer

  

S ₁	S ₀	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃


Dr. Hany Ahmed Date: 2017



Boolean Function Implementation

$$F(x, y, z) = \Sigma(1, 2, 6, 7)$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

Dr. Hany Ahmed Date: 2017




Boolean Function Implementation

$$F(x, y, z) = \Sigma(1, 2, 6, 7)$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(a) Truth table

 

(b) Multiplexer implementation


Dr. Hany Ahmed Date: 2017



Boolean Function Implementation

$$F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$$


A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

 


Dr. Hany Ahmed Date: 2017



Three-State Gates

 

Multiplexers with three-state gates

 

(a) 2-to-1-line mux

Dr. Hany Ahmed Date: 2017



Introduction

Sequential Logic Circuit

•A circuit with memory, whose outputs depend on the current input and the sequence of past outputs, is called a sequential circuit.

•The behaviour of such a circuit may be described by a state table that specifies its output and next state as functions of its current state and input.


It consists of a combinational circuit to which storage elements are connected to form a feedback path. The storage elements are devices capable of storing binary information.

Dr. Hany Ahmed Date: 2016



Introduction

sequential circuit

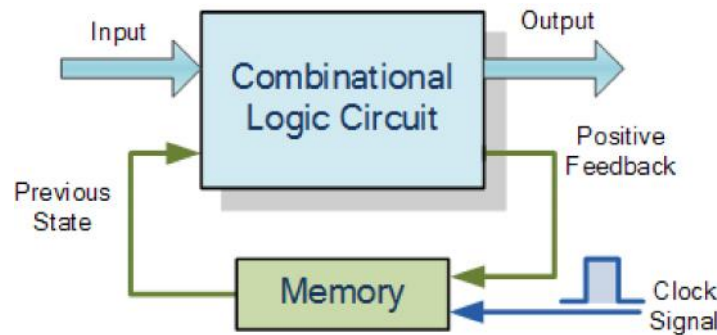

Sequential Logic Circuit

Dr. Hany Ahmed Date: 2016



Sequential Logic Circuit

Types of Sequential Circuits

- Two types of sequential circuits:
 - Synchronous**: The behavior of the circuit depends on the input signal at discrete instances of time (*also called clocked*)
 - Asynchronous**: The behavior of the circuit depends on the input signals at any instance of time and the order of the inputs change
- A combinational circuit with feedback

Dr. Hany Ahmed Date: 2016



Storage elements

Storage elements

•What's required from storage element?

- Store data (hold)
- Accept writing a new data (write)
- Read the stored data




Dr. Hany Ahmed Date: 2016



Storage elements

•Types of storage (memory) elements

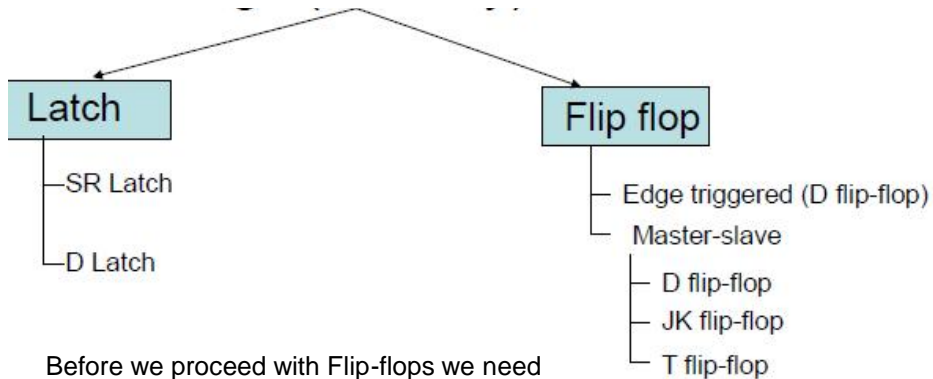

Before we proceed with Flip-flops we need to define, What's the meaning of "Clock"?

Dr. Hany Ahmed Date: 2016



The Term Clock

Clock

•In electronics, a **clock signal** is a particular type of signal that oscillates between a high and a low state and is utilized to coordinate actions of circuits. A clock signal is produced by a clock generator.


•Although more complex arrangements are used, the most common clock signal is in the form of a square wave with a 50% duty cycle, usually with a fixed, constant frequency. Circuits using the clock signal for synchronization may become active at either the rising edge, falling edge of the clock Cycle.



Dr. Hany Ahmed Date: 2016



Clock

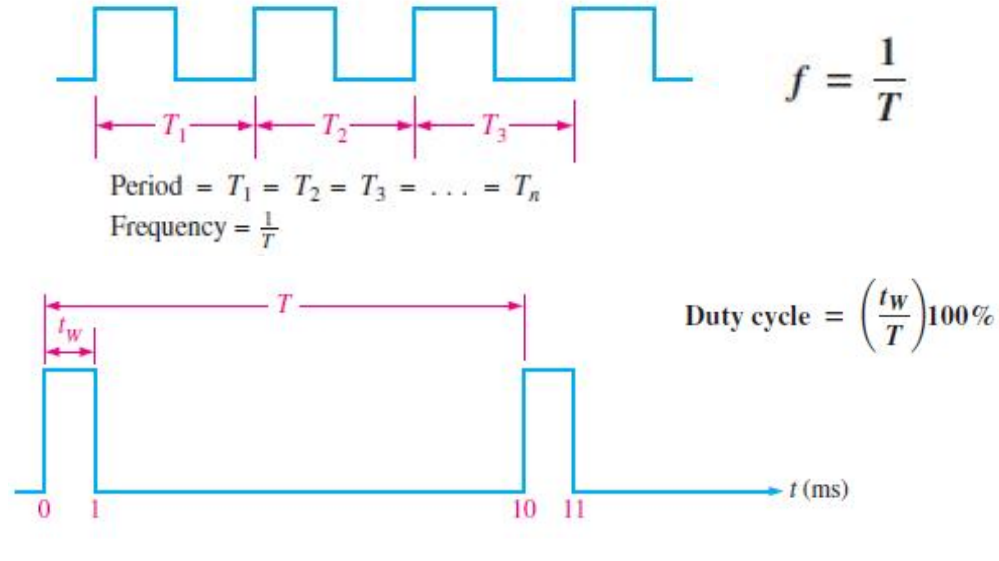


Dr. Hany Ahmed Date: 2016



clock pulses

What's the clock pulses?

-Definition of clock-pulse transition :

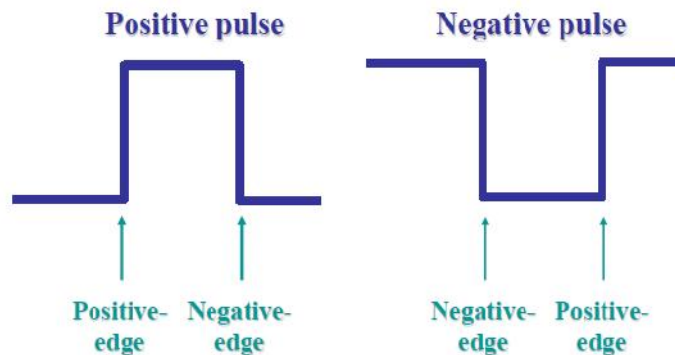


Dr. Hany Ahmed Date: 2016



Timing Diagrams

 A **timing diagram** is a graph of digital waveforms showing the actual time relationship of two or more waveforms and how each waveform changes in relation to the others



Dr. Hany Ahmed Date: 2016




Basic memory element

Storage elements

•What's the Basic idea for the memory cell?

 - Basic memory element consists of two cascaded inverters and the output of the last inverter is fed back to the input of the first inverter.
- Q and Q' are the outputs of the memory element.
- This memory element will always store one bit.
- This cell called **LATCH**




Dr. Hany Ahmed Date: 2016



Basic memory element

 How to write in this cell a new value? We need a special technique to write a new value into the memory.



Dr. Hany Ahmed Date: 2016



Storage Elements: SR latches

Storage elements that operate with signal levels (rather than signal transitions) are referred to as latches ; those controlled by a clock transition are flip-flops .

Dr. Hany Ahmed Date: 2016




D Latch


Storage Elements: D latches

Clk	D	Q(t + 1)
0	x	Q(t)
1	0	0
1	1	1

(b) Characteristic table

 

(c) Graphical symbol

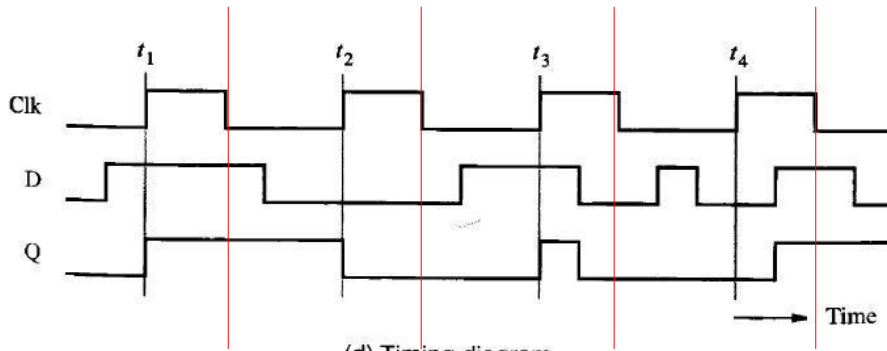


(d) Timing diagram


Dr. Hany Ahmed Date: 2016



Storage Elements: latches

 

Graphic symbols for latches

 


Dr. Hany Ahmed Date: 2016



4-bit Data Latch

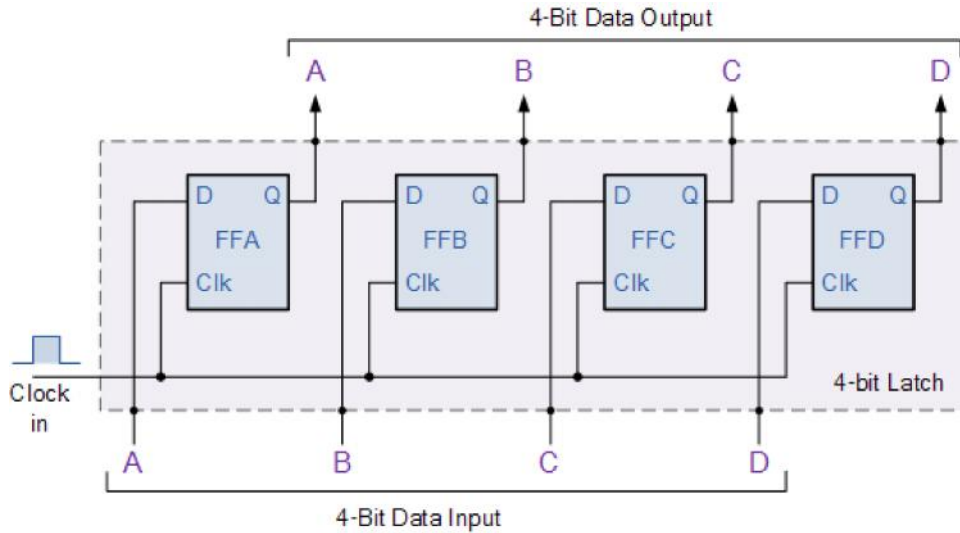
A data latch can be used as a device to hold or remember the data present on its data input, thereby acting a bit like a single bit memory device and IC's



Dr. Hany Ahmed Date: 2016



JK Flip-Flops

 

Flip-Flop Characteristic Tables



JK Flip-Flop			
J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

Dr. Hany Ahmed Date: 2016



JK Flip-Flops

Other Flip-Flops

 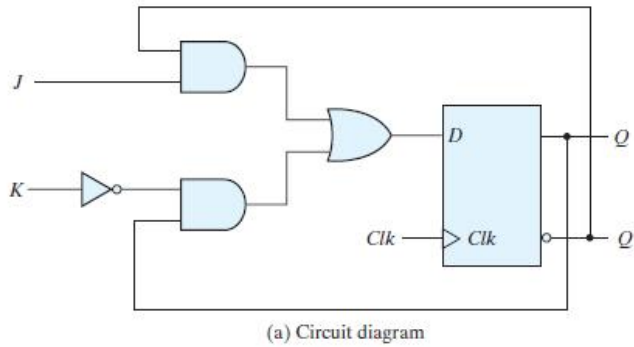


$$D = JQ' + K'Q$$

Dr. Hany Ahmed Date: 2016



T Flip-Flops

 


T Flip-Flop		
T	Q(t + 1)	
0	Q(t)	No change
1	Q'(t)	Complement


Dr. Hany Ahmed Date: 2016



T Flip-Flops

 

(b) From D flip-flop

 


(a) From JK flip-flop

$$D = T \oplus Q = TQ' + T'Q$$

Dr. Hany Ahmed Date: 2016



D Flip-Flop with SYN Reset

 

(b) Graphic symbol

<i>R</i>	<i>Clk</i>	<i>D</i>	<i>Q</i>	<i>Q'</i>
0	X	X	0	1
0	↑	0	0	1
0	↑	1	1	0

(b) Function table

Dr. Hany Ahmed Date: 2016



Digital Design

CH 5 : Synchronous Sequential Logic Circuits

Registers and Counters

Dr. Hany Ahmed Date: 2017



How could you describe combinational circuit?

- Truth table

- Logic function between input and output

- $F = A+B \Rightarrow$ if $A= 1$ and $B= 0$ $F= 1$

- if $A =0$ and $B=0$ $F=0$ (not depends on the pervious value of F)

How could you describe a sequential circuit?

- The sequential circuit output is now function in the inputs and past outputs • So, we need a tool to help us describe the behavior of the circuit.

Finite State Machine (FSM)

Dr. Hany Ahmed Date: 2017



Finite State Machine (FSM)

- **Finite State Machine** is a tool to model the desired behavior of a sequential system.
- The designer has to develop a finite state model of the system behavior and then designs a circuit that implements this model
- A FSM consists of several **states**. **Inputs** into the machine are combined with the **current state** of the machine to **determine** the **new state or next state** of the machine.
- Depending on the state of the machine, **outputs are generated** based on either the state or the state and inputs of the machine

How to describe FSM?

- **State equation** (transition equation) input variables, present states, next states equation
- **State table** input variables, present states □ next states, truth table
- **State diagram**

Dr. Hany Ahmed Date: 2017



Finite State Machine (FSM)

State tables

- Similar to the truth table
- **Doesn't contain the system clock** when specifying its transitions (it is implicit that transitions occur only when allowed by clock)
- Unless different stated, all the transitions are occurring on the **positive edge** of the clock


Present State	Inputs	Next State	Outputs




Finite State Machine (FSM)

State diagram

 - Graphical representation of the state table
- Each state is represented by a circle **vertex**
- Each row of the state table is represented as a directed **arc** from present state vertex to the next state vertex
- In this diagram, the outputs are associated with the states



Counters

 

Counters are sequential circuits which "count" through a specific state sequence. They can count up, count down, or count through other fixed sequences.



Counters

A *counter* is a sequential circuit that goes through a predetermined sequence of states upon the application of clock pulses.

Counters are categorized as:

Synchronous Counter:

All FFs receive the common clock pulse, and the change of state is determined from the present state.

Ripple Counters: Asynchronous

The FF output transition serves as a source for triggering other FFs.
No common clock.



Counters

Counters are a specific type of sequential circuit

The state serves as the “output” (Moore)

A counter that follows the binary number sequence is called a
binary counter

n-bit binary counter: n flip-flops, count in binary from 0 to 2^n-1

Counters are available in two types:

Synchronous Counters

Ripple Counters

Synchronous Counters:

A common clock signal is connected to the C input of each flip-flop



Synchronous Binary Counters

Synchronous Counters

Clock is directly connected to the flip-flop clock inputs
Logic is used to implement the desired state sequencing

The design procedure for a binary counter is the same as any other synchronous sequential circuit.

Most efficient implementations usually use D- FFs or T-FFs or JK-FFs. We will examine T and D flip-flop designs.



Synchronous Binary Counters


Synchronous Binary Up Counter Using D flip flop

The output value increases by one on each clock cycle
After the largest value, the output “wraps around” back to 0

Using two bits, we’d get something like this:

Present State		Next State	
A	B	A	B
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

State tables

 

State diagram




Synchronous Binary Counters

Synchronous Binary Up Counter Using D flip flop

Present State		Next State	
A	B	A	B
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

DA **DB**

 

A	B	
	0	1
0	$A'B'$ ⁰	1 $A'B$ ¹
1	1 AB' ²	AB ³

$$D1 = A'B + AB'$$


A	B	
	0	1
0	1 $A'B'$ ⁰	$A'B$ ¹
1	1 AB' ²	AB ³

$$D0 = B'$$



Synchronous Binary Counters

 Synchronous Binary Up Counter Using D flip flop



$$D1 = A'B + AB'$$

$$D0 = B'$$




Design of Counters

Design Counter Using T flip-flop that counts from 0-1-2-3-4-5-6-7

1- State diagram of three-bit binary counter

 Using T-type FFs, design a 3-bits binary counter that can count in binary from 0 to 7 with step 1



T-FF excitation table

Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0




Synchronous Binary Counters

State Table for Three-Bit Counter


Present State			Next State			Flip-Flop Inputs		
A ₂	A ₁	A ₀	A ₂	A ₁	A ₀	T _{A2}	T _{A1}	T _{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1



Synchronous Binary Counters

 

Synchronous Binary Counters

 



Summary


Counters serve many purposes in sequential logic design

There are lots of variations on the basic counter

Some can increment or decrement

An enable signal can be added

 The counter's value may be explicitly set



There are also several ways to make counters

You can follow the sequential design principles to build counters
from scratch

You could also modify or combine existing counter devices

Exercise

**Design Counter using T flip flops that counts from
0-3-7-4-5-1-6-2**



Registers

A common sequential device: Registers

They're a good example of sequential analysis and design

They are also frequently used in building larger sequential circuits

Registers hold larger quantities of data than individual flip-flops

Registers are central to the design of modern **processors**

There are many different kinds of registers

We'll show some applications of
these special registers





What good are registers?

Flip-flops are limited because they can store only one bit

We had to use two flip-flops for our two-bit counter examples

Most computers work with integers and single-precision floating-point numbers that are 32-bits long

A **register** is an extension of a flip-flop that can store multiple bits

Registers are commonly used as temporary storage in a processor


They are faster and more convenient than main **memory**

More registers can help speed up complex calculations



4-bit Data Latch

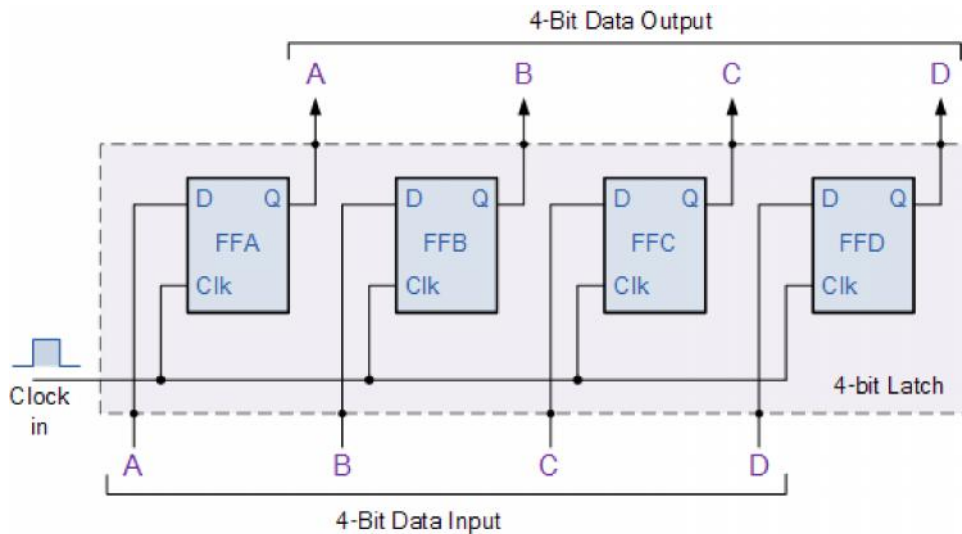A data latch can be used as a device to hold or remember the data present on its data input, thereby acting a bit like a single bit memory device and IC's






A Basic Register (Parallel in/out)

Basic registers are easy to build. We can store multiple bits just by putting a bunch of flip-flops together!

A 4-bit register is given below

This register uses D flip-flops, so it's easy to store data without worrying about flip-flop input equations

 
All the flip-flops share a common **CLK** and **CLR** signal



A Basic Register (Serial in/out)

Shift Registers move data laterally within the register toward its MSB or LSB position

 In the simplest case, the shift register is simply a set of D flip-flops connected in a row like this:



Data input, In, is called a *serial input* or the *shift right input*.


Data output, Out, is often called the *serial output*.

The vector (A, B, C, Out) is called the *parallel output*.



Shift Register

 A **shift register** “shifts” its output once every clock cycle.



SI is an input that supplies a new bit to shift “into” the register

For example, if on some positive clock edge we have:

$$SI = 1$$

$$Q_0-Q_3 = 0110$$


then the next state will be:

$$Q_0-Q_3 = 1011$$

The current Q_3 (0 in this example) will be lost on the next cycle



Shift direction

 

Present Q_0-Q_3	SI	Next Q_0-Q_3
ABCD	X	XABC

The circuit and example make it look like the register shifts “right.”

Present Q_3-Q_0	SI	Next Q_3-Q_0
DCBA	X	CBAX

But it really depends on your interpretation of the bits. If you consider Q_3 to be the most significant bit instead, then the register is shifting in the *opposite* direction!



Serial data transfer

One application of shift registers is converting between “serial data” and “parallel data”

Computers typically work with multiple-bit quantities

ASCII text characters are 8 bits long

Integers, single-precision floating-point numbers, and screen pixels are up to 32 bits long

But sometimes it’s necessary to send or receive data **serially**, or one bit at a time. Some examples include:

Input devices such as keyboards and mice

Output devices like printers

Any serial port, USB or Firewire device transfers data serially

Recent switch from Parallel ATA to Serial ATA in hard drives



Receiving serial data

To *receive* serial data using a shift register:

The serial device is connected to the register’s SI input


The shift register outputs Q3-Q0 are connected to the computer

The serial device transmits one bit of data per clock cycle

These bits go into the SI input of the shift register

After four clock cycles, the shift register will hold a four-bit word

 The computer then reads all four bits at once from the Q3-Q0 outputs.





Sending data serially

To *send* data serially with a shift register, you do the opposite:

The CPU is connected to the register's D inputs


The shift output (Q3 in this case) is connected to the serial device

The computer first stores a four-bit word in the register, in one cycle

The serial device can then read the shift output

One bit appears on Q3 on each clock cycle

 After four cycles, the entire four-bit word will have been sent



Registers summary

A register is a special state machine that stores multiple bits of data

Several variations are possible:

Parallel loading to store data into the register

Shifting the register contents either left or right

Counters are considered a type of register too!

One application of shift registers is converting between serial and parallel data

Most programs need more storage space than registers provide

We'll introduce RAM to address this problem

Registers are a central part of modern processors

TASKs - Implementing the registers and Counters.

Best Wishes

Sheet (1)

1- Convert the following numbers with the indicated bases to decimal:

(a) $(4310)_5$ (b) $(198)_{12}$ (c) $(435)_8$ (d) $(345)_6$

2- Express the following numbers in decimal:

(a) $(10110.0101)_2$ (b) $(16.5)_{16}$ (c) $(26.24)_8$
 (d) $(DADA.B)_{16}$ (e) $(1010.1101)_2$

3- What is the largest binary number that can be expressed with 16 bits?
 What are the equivalent decimal and hexadecimal numbers?

4- Determine the base of the numbers in each case for the following operations to be correct:

(a) $14/2 = 5$ (b) $54/4 = 13$ (c) $24 + 17 = 40$.

5- The solutions to the quadratic equation $x^2 - 11x + 22 = 0$ are $x = 3$ and $x = 6$.
 What is the base of the numbers?

6- (a) Find the 16's complement of C3DF. (b) Convert C3DF to binary.
 (c) Find the 2's complement of the result in (b).
 (d) Convert the answer in (c) to hexadecimal and compare with the answer in (a).


7- Perform subtraction on the given unsigned binary numbers using the 2's complement of the subtrahend. Where the result should be negative, find its 2's complement and affix a minus sign.

(a) $10011 - 10010$ (b) $100010 - 100110$
 (c) $1001 - 110101$ (d) $101000 - 10101$

8- Represent the unsigned decimal numbers 791 and 658 in BCD, and then show the steps necessary to form their sum.

9- The state of a 12-bit register is 100010010111. What is its content if it represents
 (a) Three decimal digits in BCD?
 (b) Three decimal digits in the excess-3 code?
 (c) Three decimal digits in the 84-2-1 code?
 (d) A binary number?

 10- Express the switching electrical circuit below in binary logic form?



Sheet (2)

1- Simplify the following Boolean expressions:

(a)* $ABC + A'B + ABC'$

(c)* $(x + y)'(x' + y')$

(e)* $(BC' + A'D)(AB' + CD')$

(b)* $x'yz + xz$

(d)* $xy + x(wz + wz')$

(f) $(a' + c')(a + b' + c')$

2- Find the complement of $F = wx + yz$; then show that $FF' = 0$ and $F + F' = 1$.

3- Find the complement of the following expressions:

(a)* $xy' + x'y$

(c) $z + z'(v'w + xy)$

(b) $(a + c)(a + b')(a' + b + c')$

4- Given the Boolean functions F1 and F2, show that (a) The Boolean function $E = F1 + F2$ contains the sum of the minterms of F1 and F2. (b) The Boolean function $G = F1F2$ contains only the minterms that are common to F1 and F2.

5- Implement the Boolean function

$$F = xy + x'y' + y'z$$

(a) With AND, OR, and inverter gates.

(c) With AND and inverter gates.

(e) With NOR and inverter gates.

(b) With OR and inverter gates

(d) With NAND and inverter gates.

6- For the Boolean function $F = xy'z + x'y'z + w'xy + wx'y + wxy$

(a) Obtain the truth table of F. (b) Draw the logic diagram, using the original Boolean expression. (c) Use Boolean algebra to simplify the function to a minimum number of literals. (d) Obtain the truth table of the function from the simplified expression and show that it is the same as the one in part (a).

(e) Draw the logic diagram from the simplified expression, and compare the total number of gates with the diagram of part (b).

7- Obtain the truth table of the following functions, and express each function in sum-of-minterms and product-of-maxterms form:

(a)* $(b + cd)(c + bd)$

(c) $(c' + d)(b + c')$

(b) $(cd + b'c + bd')(b + d)$

(d) $bd' + acd' + ab'c + a'c'$

Sheet (2)

8- Express the following function as a sum of minterms and as a product of maxterms:

$$F(A, B, C, D) = B'D + A'D + BD$$

9- Express the complement of the following functions in sum-of-minterms form:

(a) $F(A, B, C, D) = \sum(2, 4, 7, 10, 12, 14)$

(b) $F(x, y, z) = \prod(3, 5, 7)$

10- Determine whether the following Boolean equation is true or false.

$$x'y' + x'z + x'z' = x'z' + y'z' + x'z$$

11- Convert each of the following expressions into sum of products and product of sums:

(a) $(u + xw)(x + u'v)$

(b) $x' + x(x + y')(y + z')$

12- Write the following Boolean expressions in sum of products form:

$$(b + d)(a' + b' + c)$$

13- Write the following Boolean expression in product of sums form:

$$a'b + a'c' + abc$$

14- Show that the dual of the exclusive-OR is equal to its complement.

15- Show that the simplest form of

$$XYZ' + XY'Z + X'YZ + XYZ$$

is

$$XY + XZ + YZ$$

Sheet (3)

1- Simplify the following Boolean expressions:

(a)* $F(x, y, z) = \Sigma(0, 1, 5, 7)$

(b)* $F(x, y, z) = \Sigma(1, 2, 3, 6, 7)$

(c) $F(x, y, z) = \Sigma(2, 3, 4, 5)$

(d) $F(x, y, z) = \Sigma(1, 2, 3, 5, 6, 7)$

(e) $F(x, y, z) = \Sigma(0, 2, 4, 6)$

(f) $F(x, y, z) = \Sigma(3, 4, 5, 6, 7)$

2- Simplify the following Boolean expressions, using three-variable maps:

(a)* $xy + x'y'z' + x'yz'$

(b)* $x'y' + yz + x'yz'$

(c)* $F(x, y, z) = x'y + yz' + y'z'$

(d) $F(x, y, z) = x'yz + xy'z' + xy'z$

3- Simplify the following Boolean functions, using Karnaugh maps:

(a)* $F(x, y, z) = \Sigma(2, 3, 6, 7)$

(b)* $F(A, B, C, D) = \Sigma(4, 6, 7, 15)$

(c)* $F(A, B, C, D) = \Sigma(3, 7, 11, 13, 14, 15)$

(d)* $F(w, x, y, z) = \Sigma(2, 3, 12, 13, 14, 15)$

(e) $F(w, x, y, z) = \Sigma(11, 12, 13, 14, 15)$

(f) $F(w, x, y, z) = \Sigma(8, 10, 12, 13, 14)$

4- Simplify the following Boolean expressions, using four-variable maps:

(a)* $A'B'C'D' + AC'D' + B'CD' + A'BCD + BC'D$

(b)* $x'z + w'xy' + w(x'y + xy')$

(c) $A'B'C'D + AB'D + A'BC' + ABCD + AB'C$

(d) $A'B'C'D' + BC'D + A'C'D + A'BCD + ACD'$

5- Find all the prime implicants for the following Boolean functions, and determine which are essential:

(a)* $F(w, x, y, z) = \Sigma(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$

(b)* $F(A, B, C, D) = \Sigma(0, 2, 3, 5, 7, 8, 10, 11, 14, 15)$

(c) $F(A, B, C, D) = \Sigma(2, 3, 4, 5, 6, 7, 9, 11, 12, 13)$

(d) $F(w, x, y, z) = \Sigma(1, 3, 6, 7, 8, 9, 12, 13, 14, 15)$

(e) $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$

(f) $F(w, x, y, z) = \Sigma(0, 1, 2, 5, 7, 8, 10, 15)$

Sheet (3)

6- Convert the following Boolean function from a sum-of-products form to a simplified product-of-sums form.

$$F(x, y, z) = \Sigma(0, 1, 2, 5, 8, 10, 13)$$

7- Simplify the following Boolean functions:

(a)* $F(A, B, C, D) = \Pi(1, 3, 5, 7, 13, 15)$

(b) $F(A, B, C, D) = \Pi(1, 3, 6, 9, 11, 12, 14)$

8- Simplify the following expressions to (1) sum-of-products and (2) products-of-sums:

(a)* $x'z' + y'z' + yz' + xy$

(b) $ACD' + C'D + AB' + ABCD$

(c) $(A' + B + D')(A' + B' + C')(A' + B' + C)(B' + C + D')$

(d) $BCD' + ABC' + ACD$

9- Simplify the following Boolean function F, together with the don't-care conditions d, and then express the simplified function in sum-of-minterms form:

(a) $F(x, y, z) = \Sigma(0, 1, 4, 5, 6)$

$d(x, y, z) = \Sigma(2, 3, 7)$

(b)* $F(A, B, C, D) = \Sigma(0, 6, 8, 13, 14)$

$d(A, B, C, D) = \Sigma(2, 4, 10)$

(c) $F(A, B, C, D) = \Sigma(5, 6, 7, 12, 14, 15,)$

$d(A, B, C, D) = \Sigma(3, 9, 11, 15)$

(d) $F(A, B, C, D) = \Sigma(4, 12, 7, 2, 10,)$

$d(A, B, C, D) = \Sigma(0, 6, 8)$

10- Simplify the following functions, and implement them with two-level NAND gate circuits:

(a) $F(A, B, C, D) = AC'D' + A'C + ABC + AB'C + A'C'D'$

(b) $F(A, B, C, D) = A'B'C'D + CD + AC'D$

(c) $F(A, B, C) = (A' + C' + D')(A' + C')(C' + D')$

(d) $F(A, B, C, D) = A' + B + D' + B'C$

Sheet (3)

11- Draw a logic diagram using only two-input NOR gates to implement the following function:

$$F(A, B, C, D) = (A \oplus B)'(C \oplus D)$$

12- Simplify the following functions, and implement them with two-level NOR gate circuits

(a)* $F = wx' + y'z' + w'yz'$

(b) $F(w, x, y, z) = \Sigma(0, 3, 12, 15)$

13- Draw the multiple-level NOR circuit for the following expression:

$$CD(B + C)A + (BC' + DE')$$

14- Draw the multiple-level NAND circuit for the following expression

$$w(x + y + z) + xyz$$

15- Implements the following Boolean function F, using the two-level forms of logic (a) NANDAND, (b) AND-NOR, (c) OR-NAND, and (d) NOR-OR:

$$F(A, B, C, D) = \Sigma(0, 4, 8, 9, 10, 11, 12, 14)$$

16- Derive the circuits for a three-bit parity generator and four-bit parity checker using an odd parity bit.

Best Wishes

References



Main Reference:

1. M. Morris Mano, " **Digital Design**," 5th edition.
2. Thomas Floyd, " **Digital Fundamentals**," 10th edition.
3. Hany Ahmed, " **Lecture Notes: Logic Design** ", 2024