



**EE101**

الكترونياات

إعداد وتجميع

ا.م.د/ هانى احمد عطاالله

كلية الهندسة بقنا

قسم الهندسة الكهربائية

العام الجامعى

2025/2024

## بيانات الكتاب

---

الكلية: الحاسبات والمعلومات

الفرقة: المستوى الاول

التخصص: عام

تاريخ النشر: 2024

عدد الصفحات: 194

اعداد وتجميع : ا.م.د/ هانى احمد عطاالله

## الرموز المستخدمة

---

نص للقراءة والدراسة



أنشطة ومهام



أسئلة للتفكير والتقييم الذاتي



فيديو للمشاهدة



رابط خارجي



تواصل عبر مؤتمر الفيديو



## المحتوى

---

Content	Page
<b>Introduction</b>	5
<b>Ch1: Introduction and Fundamentals of Electric Circuits</b>	7
<b>Ch2: Basic Laws of Electric Circuits</b>	25
<b>Ch3: Methods of Analysis of Electric Circuits</b>	44
<b>Ch4: Circuit Theorems</b>	65
<b>Ch5: Operational Amplifier</b>	84
<b>Ch6: Capacitors and Inductors</b>	98
<b>Ch7: Bipolar Junction Transistor (BJT) and Field Effect Transistor (FET) - BJT and FET Applications (Amplifiers)</b>	117
<b>Ch8: AC circuits</b>	156
<b>Ch9: Diodes Circuits and Applications</b>	173
<b>Review</b>	193
<b>References</b>	194

الصور والاشكال

---

الفيديو

---



# Introduction

Electric circuit theory and electromagnetic theory are the two fundamental theories upon which all branches of electrical engineering are built. Many branches of electrical engineering, such as power, electric machines, control, electronics, communications, and instrumentation, are based on electric circuit theory. Therefore, the basic electric circuit theory course is the most important course for a computer science student, and always an excellent starting point for electronics education. Circuit theory is also valuable to students specializing in other branches of the physical sciences because circuits are a good model for the study of energy systems in general, and because of the applied mathematics, physics, and topology involved.

The course is an introduction to Electric circuit theory and electronics as well digital design technology. It allows you to understand the basics of circuit theory and electronics and helps you develop skills.

In this course the student will be learn the following topics: Basic Concepts of DC circuits [ Basic Laws of DC circuits - Methods of Analysis of circuits - Circuit Theorems - Operational Amplifiers - Capacitors and Inductors - Bipolar Junction Transistor (BJT) and Field Effect Transistor (FET) - BJT and FET Applications (Amplifiers) [ AC circuits - Diodes Circuits and Applications [ logic circuits.

The following is a brief summary of the topics that are covered in each chapter.

**Chapter 1** presents the Basic Concepts of DC circuit's for example Charge, Current, Voltage, Power and Energy.

**Chapter 2** introduces the basic Laws of DC circuits.

**Chapter 3** covers the Methods of Analysis of circuits.

**Chapter 4** Explains the Circuit Theorems.

**Chapter 5** outlines the Operational Amplifiers and their applications.

**Chapter 6** defines the Capacitors and Inductors.

**Chapter 7** explains the Bipolar Junction Transistor (BJT) and Field Effect Transistor (FET) - BJT and FET Applications (Amplifiers) [ logic circuits.

**Chapter 8** presents the fundamentals of AC circuits.

**Chapter 9** explains the fundamentals Diodes Circuits and Applications.



---

**EE 101**  
**Electronics**



**1<sup>st</sup> Semester 2021**

**1<sup>st</sup> Year Computers and Information**

**Dr. Eng. Hany Ahmed**

---

Dr. Hany Ahmed Atallah



**Fundamentals of Electric Circuits**

**Chapter 1**  
**Basic Concepts**

Dr. Hany Ahmed Atallah



## Basic Concepts - Chapter 1

**1.1 Systems of Units.**

**1.2 Electric Charge.**

**1.3 Current.**

**1.4 Voltage.**

**1.5 Power, Energy and Efficiency .**

**1.6 Circuit Elements.**

**1.7 Applications**


Dr. Hany Ahmed Atallah
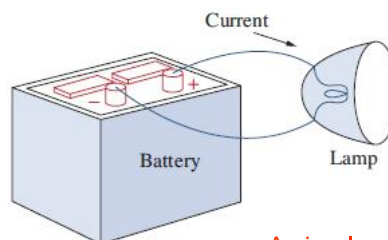
## Introduction



**Electric circuit theory** and **electromagnetic theory** are the two fundamental Theories for all branches of electrical engineering.

An **electric circuit** is an interconnection of electrical elements.




A simple electric circuit

Dr. Hany Ahmed Atallah

## Introduction



A complicated electric circuit

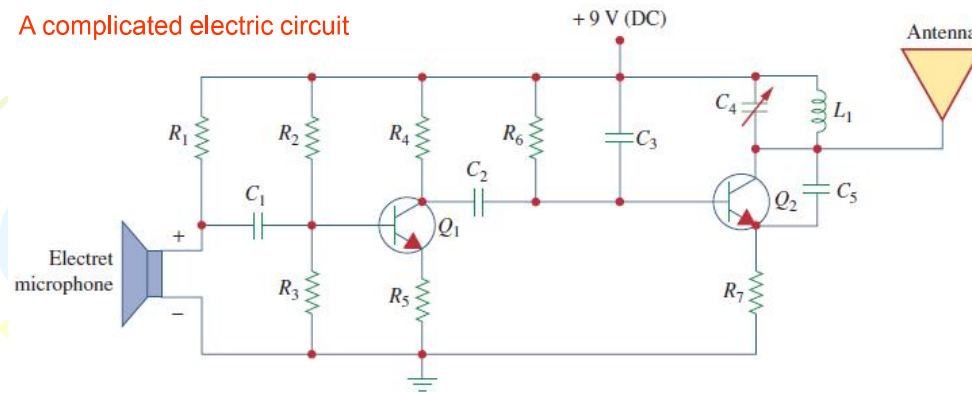

Electric circuit of a radio transmitter.

Dr. Hany Ahmed Atallah

## System of Units (1)



### Basic Units

Quantity	Basic unit	Symbol
Length	meter	m
Mass	kilogram	Kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	kelvin	K
Luminous intensity	candela	cd
Charge	coulomb	C

Dr. Hany Ahmed Atallah

## System of Units (2)



The derived units commonly used in electric circuit theory

Quantity	Unit	Symbol	Factor	Prefix	Symbol
electric charge	coulomb	C	$10^9$	giga	G
electric potential	volt	V	$10^6$	mega	M
resistance	ohm	$\Omega$	$10^3$	kilo	k
conductance	siemens	S	$10^{-2}$	centi	c
inductance	henry	H	$10^{-3}$	milli	m
capacitance	farad	F	$10^{-6}$	micro	$\mu$
frequency	hertz	Hz	$10^{-9}$	nano	n
force	newton	N	$10^{-12}$	pico	p
energy, work	joule	J			
power	watt	W			
magnetic flux	weber	Wb			
magnetic flux density	tesla	T			


Decimal multiples and submultiples of SI units

Dr. Hany Ahmed Atallah
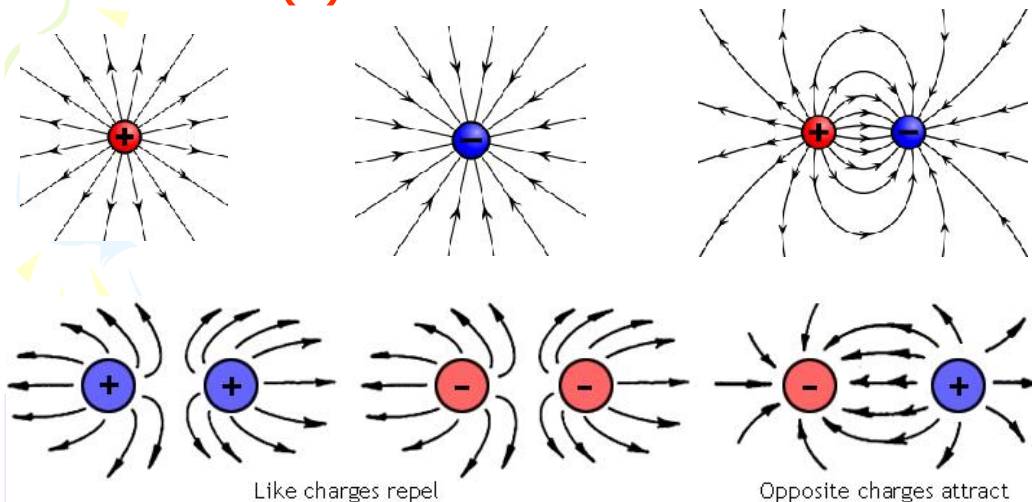
## Electric Charges



- Charge** is an electrical property of the atomic particles of which matter consists, measured in **coulombs (C)**.




Dr. Hany Ahmed Atallah

## Electric and Magnetic Field




The Magnetic Field Lines

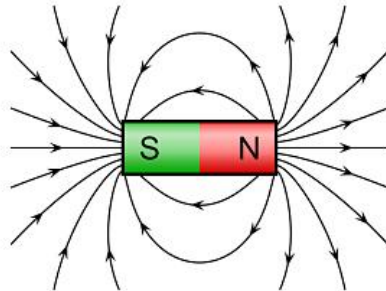

Bar Magnet

The Electric Field Lines

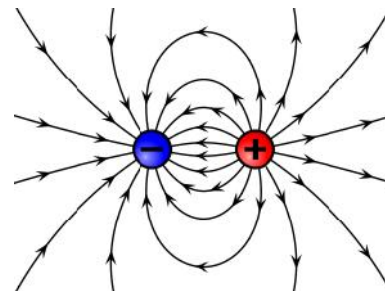



Point Charge

Dr. Hany Ahmed Atallah
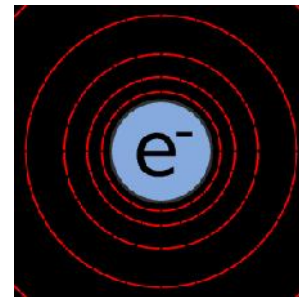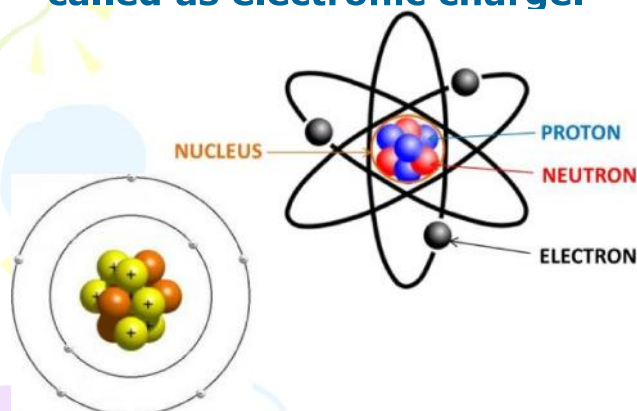
## Electric Charges



- The charge **e** on one **electron** is negative and equal in magnitude to  $1.602 \times 10^{-19}$  C which is called as electronic charge.



- The charges that occur in nature are **integral multiples** of the electronic charge.

Dr. Hany Ahmed Atallah

## Electric Potential: Point Charges



**A volt** represents the amount of work per unit charge (1C) required to move a charge between two positions in an electric field

$$V_{ab} = dw/dq$$


For a point charge the absolute potential of any position in its electric field can be calculated using the equation

$$V_{\text{abs}} = kQ/r$$

Coulomb constant  $K = 9 \times 10^9$

$$k_e = \frac{1}{4\pi\epsilon_0} = \frac{c^2 \mu_0}{4\pi} = c^2 \cdot 10^{-7} \text{ H} \cdot \text{m}^{-1}$$
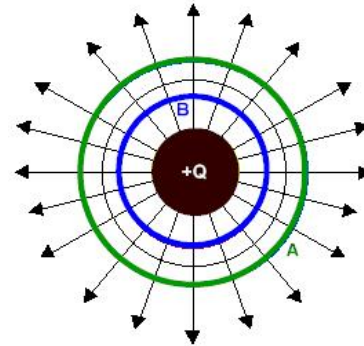
$$= 8.987\ 551\ 787\ 368\ 176\ 4 \times 10^9 \text{ N} \cdot \text{m}^2 \cdot \text{C}^{-2}$$



Dr. Hany Ahmed Atallah

## Work (Energy)



### Work (joule)


If it takes 1 joule of work to move 1 coulomb of charge between two positions in an electric field, then those positions have a potential difference of 1 volt

$$(1 \text{ joule} = 1 \text{ coulomb} \times 1 \text{ volt})$$

work is required by an external agent to move a +1 C charge from surface A to surface B

$$W_{\text{external}} = q\Delta V$$
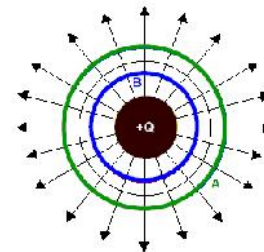
$$W_{\text{external}} = q(V_{\text{final}} - V_{\text{original}})$$



Dr. Hany Ahmed Atallah



## Electric Potential Energy



EPE represents a charge's electric potential energy which is calculated as **the magnitude of the charge times the absolute potential of its position in the electric field** produced by the central charge.

$$\text{EPE} = qV_{\text{abs}} = kqQ/r$$


Dr. Hany Ahmed Atallah

## Current (1)



- **Electric current is the time rate of change of charge, measured in amperes (A).**

$$i \triangleq \frac{dq}{dt}$$

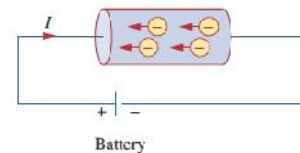

- **Electric current  $i = dq/dt$ . The unit of ampere can be derived as  $1 \text{ A} = 1 \text{ C/s}$ .**

The charge transferred between time  $t_0$  and  $t$  is obtained by

$$Q \triangleq \int_{t_0}^t i dt$$




Andre-Marie Ampere (1775–1836)

Dr. Hany Ahmed Atallah
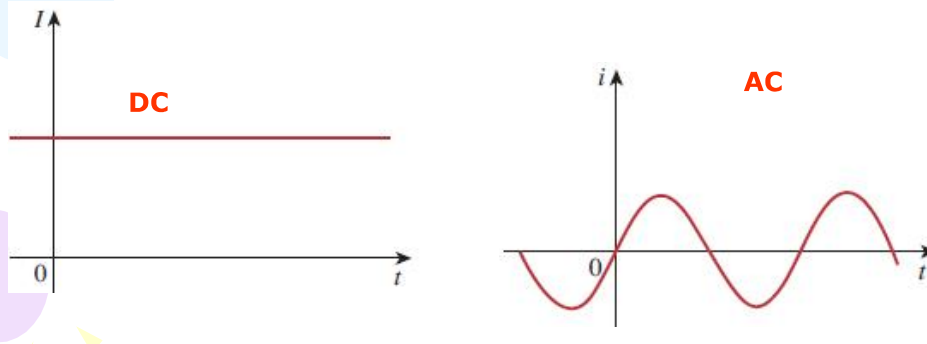
## Current (2)



- A **direct current (dc)** is a current that remains constant with time.
- An **alternating current (ac)** is a current that varies sinusoidally with time. (reverse direction)




Dr. Hany Ahmed Atallah

## Current (3)



- The direction of current flow

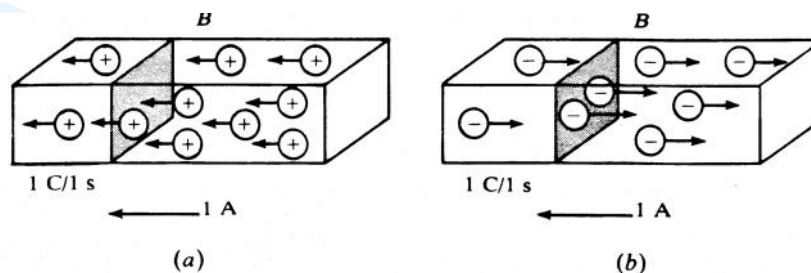

Positive ions

Negative ions

Dr. Hany Ahmed Atallah

## Current (4)



### Example 1

A conductor has a constant current of **5 A**.

How many electrons pass a fixed point on the conductor in **one minute**?

Dr. Hany Ahmed Atallah

## Current (5)



### Solution

$$i = q/t$$

Total no. of charges pass in 1 min that is given by 5 A

$$Q = (5 \text{ C/s})(60 \text{ s/min}) = 300 \text{ C/min}$$

Total no. of electronics pass in 1 min is given

$$\frac{300 \text{ C/min}}{1.602 \times 10^{-19} \text{ C/electron}} = 1.87 \times 10^{21} \text{ electrons/min}$$

Dr. Hany Ahmed Atallah

## Current (6)



### Example 2

Determine the total charge entering a terminal between  $t=1\text{s}$  and  $t=2\text{s}$  if the current passing the terminal is  $i = (3t^2 - t) \text{ A}$

Dr. Hany Ahmed Atallah

## Current (7)



### Solution

$$Q \triangleq \int_{t_0}^t i \, dt$$

$$\begin{aligned} Q &= \int_{t=1}^2 i \, dt = \int_1^2 (3t^2 - t) \, dt \\ &= \left( t^3 - \frac{t^2}{2} \right) \Big|_1^2 = (8 - 2) - \left( 1 - \frac{1}{2} \right) = 5.5 \text{ C} \end{aligned}$$

Dr. Hany Ahmed Atallah

## Voltage (1)



- Voltage (or potential difference) is the **energy** required to move a **unit charge** through an element, measured in volts (V).


- Mathematically,  $v_{ab} = dw/dq$  (volt)

-  $w$  is energy in joules (J) and  $q$  is charge in coulomb (C).

- The voltage between two points  $a$  and  $b$  in an electric circuit is the energy (or work) needed to move a unit charge from  $a$  to  $b$ ;

- $V_{ab} = V_a - V_b$
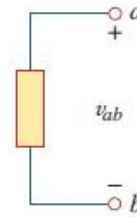
$$V = W/Q \quad \text{and} \quad Q = I \cdot t$$



Dr. Hany Ahmed Atallah

## Voltage (2)




- Electric voltage,  $v_{ab}$ , is always **across the circuit element** or **between two points in a circuit**.

$$V_{ab} = V_a - V_b$$

-  $v_{ab} > 0$  means the potential of  $a$  is higher than potential of  $b$ .

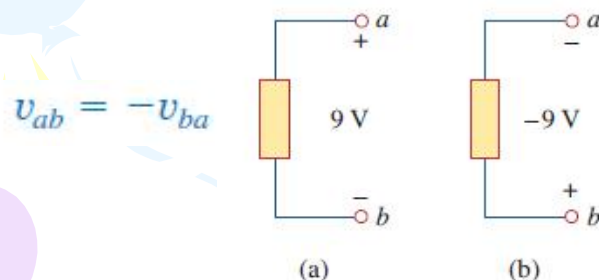-  $v_{ab} < 0$  means the potential of  $a$  is lower than potential of  $b$ .



Alessandro Antonio Volta (1745-1827)


Dr. Hany Ahmed Atallah
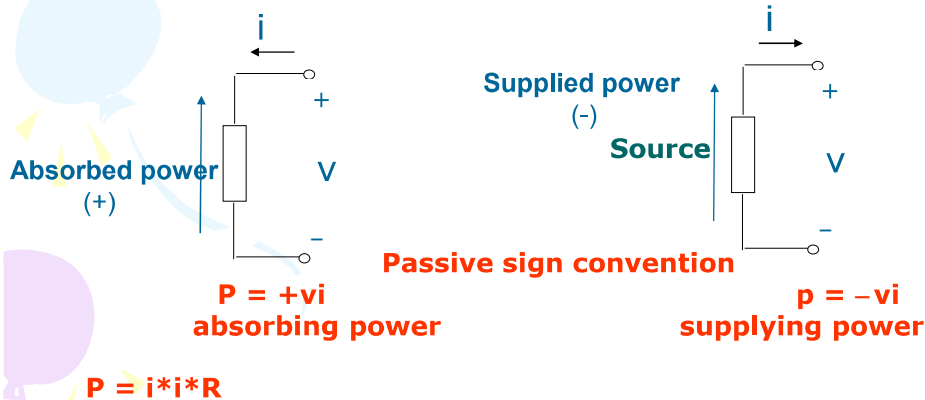
## Power and Energy (1)



- **Power** is the time rate of expending or absorbing energy, measured in watts (W).

- Mathematical expression:  $p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi$



Dr. Hany Ahmed Atallah

## Power and Energy (2)



- The law of conservation of energy

$$\sum p = 0$$

- Energy is the capacity to do work, measured in joules (J).

- Mathematical expression  $w = \int_{t_0}^t p dt = \int_{t_0}^t v i dt$

$$\mathbf{W \text{ (Joules)} = P \text{ (Watts)} * t \text{ (Seconds)}}$$

The electric power utility companies measure energy in Kilowatt-hour (**kWh**) instead of using Joule

$$\mathbf{W \text{ (Kilowatt-hours)} = P \text{ (Kilowatts)} * t \text{ (hours)}}$$


$$1 \text{ Wh} = 3,600 \text{ J}$$

Dr. Hany Ahmed Atallah


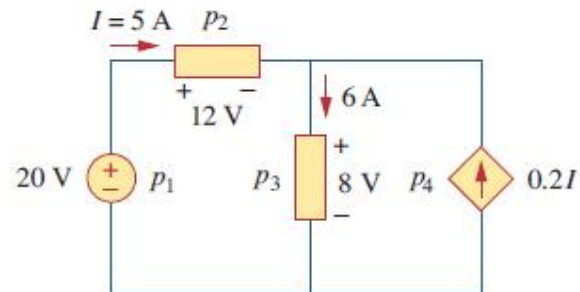
## Example

Calculate the power supplied or absorbed by each element




### Solution

$$p_1 = 20(-5) = -100 \text{ W} \quad \text{Supplied power}$$

$$p_2 = 12(5) = 60 \text{ W} \quad \text{Absorbed power}$$

Dr. Hany Ahmed Atallah

## Example

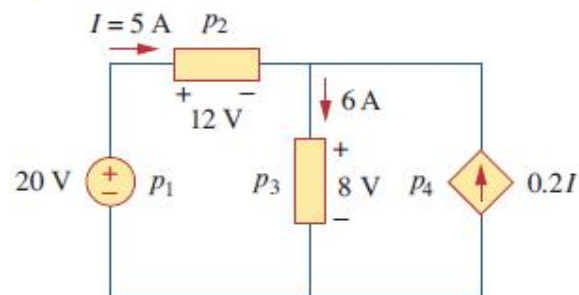

$$p_3 = 8(6) = 48 \text{ W} \quad \text{Absorbed power}$$

$$p_4 = 8(-0.2I) = 8(-0.2 \times 5) = -8 \text{ W} \quad \text{Supplied power}$$

The law of conservation of energy

$$\sum p = 0$$

$$p_1 + p_2 + p_3 + p_4 = -100 + 60 + 48 - 8 = 0$$

Dr. Hany Ahmed Atallah

## Power and Efficiency



- The Power output rating of devices (ex. motors ) is usually expressed in a power unit called horsepower (hp).

**1 hp = 745.7 watts (W).**

- The efficiency of a device can be calculated by

$$\text{Efficiency } (\%) = \text{Pout} / \text{Pin}$$

The output power divided by the input power (dimensionless)

Dr. Hany Ahmed Atallah


## Circuit Elements (1)



An active element is capable of generating energy while a passive element is not (consuming power)

**Active Elements**

**Passive Elements**

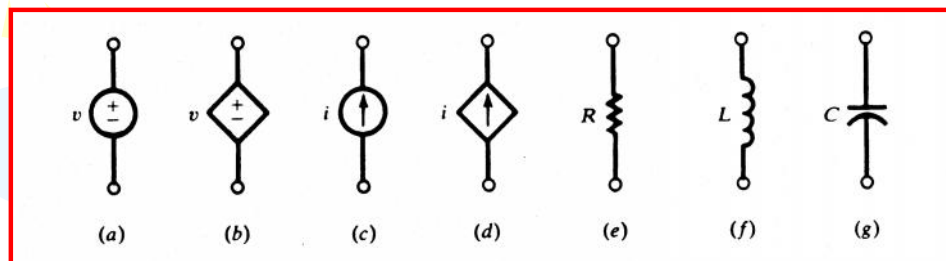

Independent sources      Dependent sources

- A dependent source is an active element in which the source quantity is controlled by another voltage or current.
- They have four different types: VCVS, CCVS, VCCS, CCCS. Keep in mind the signs of dependent sources.

Dr. Hany Ahmed Atallah



## Circuit Elements (1)



### Example 2

Obtain the voltage  $v$  in the branch shown in Figure 2.1.1P for  $i_2 = 1\text{ A}$ .

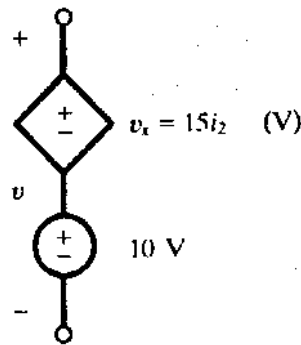


Figure 2.1.1P

Dr. Hany Ahmed Atallah

## Circuit Elements (1)



### Solution

Voltage  $v$  is the sum of the current-independent 10-V source and the current-dependent voltage source  $v_x$ .

Note that the factor 15 multiplying the control current carries the units  $\Omega$ .

Therefore,  $v = 10 + v_x = 10 + 15(1) = 25\text{ V}$

Dr. Hany Ahmed Atallah






## Force on A Moving Charge in Electric Field

The electric field between the plates is

$$E = \frac{V}{d}$$

The magnitude of the force on the electron and proton is

$$F = QE$$

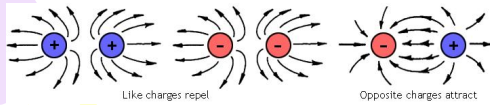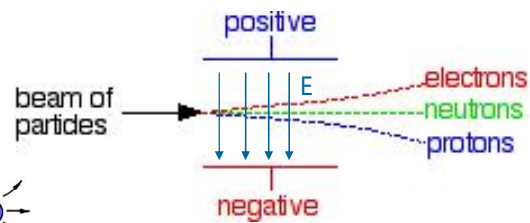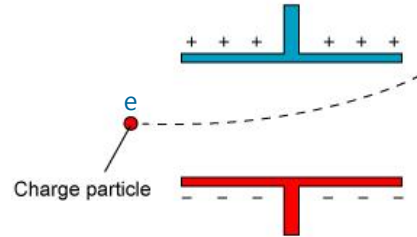



Dr. Hany Ahmed Atallah

## Applications (1)



### The Cathode-ray tube (CRT).

#### TV Picture Tube

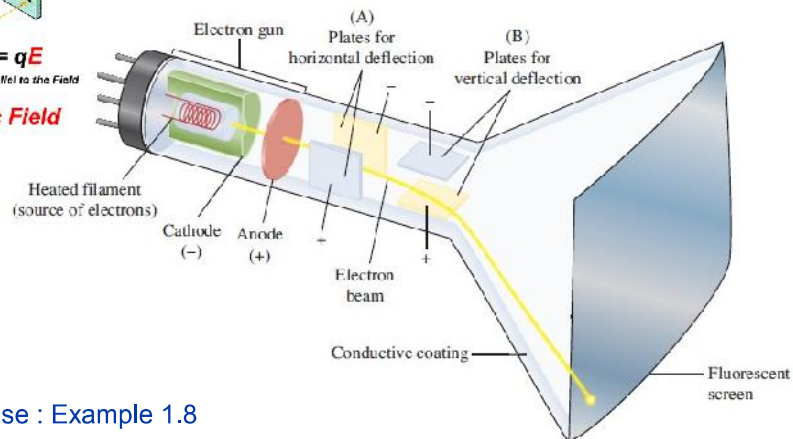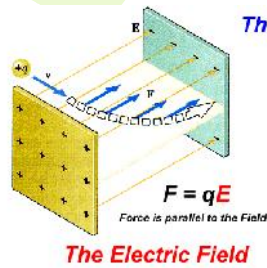

Exercise : Example 1.8

Dr. Hany Ahmed Atallah

## Applications (2)



### Electricity Bills

- The cost of electricity depends upon the amount of energy consumed in kilowatt-hours (kWh).

Dr. Hany Ahmed Atallah

## Applications (2)



A homeowner consumes 700 kWh in January. Determine the electricity bill for the month using the following residential rate schedule:

Base monthly charge of \$12.00.

First 100 kWh per month at 16 cents/kWh.

Next 200 kWh per month at 10 cents/kWh.

Over 300 kWh per month at 6 cents/kWh.

Dr. Hany Ahmed Atallah

## Applications (2)



### Solution:

We calculate the electricity bill as follows.

Base monthly charge = \$12.00

First 100 kWh @ \$0.16/kWh = \$16.00

Next 200 kWh @ \$0.10/kWh = \$20.00

Remaining 400 kWh @ \$0.06/kWh = \$24.00

Total charge = \$72.00

$$\text{Average cost} = \frac{\$72}{100 + 200 + 400} = 10.2 \text{ cents/kWh}$$

Dr. Hany Ahmed Atallah

## Home work



### Solving CH 1 Problems

Dr. Hany Ahmed Atallah



# Chapter 2

## Basic Laws

Dr. Hany Ahmed Atallah

### Basic Laws - Chapter 2



- 1 Ohm's Law.**
- 2 Nodes, Branches, and Loops.**
- 3 Kirchhoff's Laws.**
- 4 Series Resistors and Voltage Division.**
- 5 Parallel Resistors and Current Division.**
- 6 Wye-Delta Transformations.**
- 8 Applications**

Dr. Hany Ahmed Atallah

## Ohms Law (1)



Ohm's law states that the voltage across a resistor is directly proportional to the current  $I$  flowing through the resistor.



Georg Simon Ohm (1787–1854)

Dr. Hany Ahmed Atallah



## Ohms Law (2)




- Mathematical expression for Ohm's Law is as follows:

$$v = iR$$

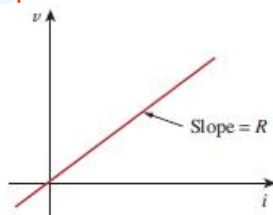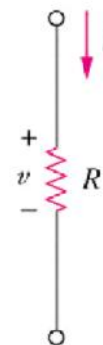- Two extreme possible values of  $R$ : **(zero)** and  $\infty$  **(infinite)** are related with two basic circuit concepts: **short circuit** and **open circuit**.



(a) a linear resistor,

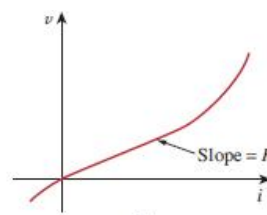

(b) a nonlinear resistor.

Dr. Hany Ahmed Atallah

## Ohms Law (3)




Materials in general have a characteristic behavior of resisting the flow of electric charge.

This physical property, or ability to resist current, is known as *resistance* and is represented by the symbol  $R$ .

$$R = \rho \frac{\ell}{A}$$

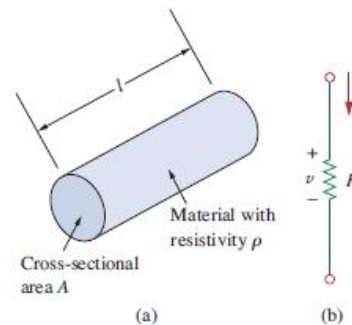where  $\rho$  is known as the *resistivity* of the material in ohm-meters



$$A = \pi r^2$$

Dr. Hany Ahmed Atallah

## Ohms Law (4)



$$R = \rho \frac{\ell}{A}$$

where  $\rho$  is known as the *resistivity* of the material in ohm-meters

### Resistivities of common materials.

Material	Resistivity ( $\Omega \cdot m$ )	Usage
Silver	$1.64 \times 10^{-8}$	Conductor
Copper	$1.72 \times 10^{-8}$	Conductor
Aluminum	$2.8 \times 10^{-8}$	Conductor
Gold	$2.45 \times 10^{-8}$	Conductor
Carbon	$4 \times 10^{-5}$	Semiconductor
Germanium	$47 \times 10^{-2}$	Semiconductor
Silicon	$6.4 \times 10^2$	Semiconductor
Paper	$10^{10}$	Insulator
Mica	$5 \times 10^{11}$	Insulator
Glass	$10^{12}$	Insulator
Teflon	$3 \times 10^{12}$	Insulator

Dr. Hany Ahmed Atallah


## Ohms Law (5)




Two extreme possible values of R:

**0 (zero) and  $\infty$  (infinite)** are related with two basic circuit concepts: **short circuit** and **open circuit**.

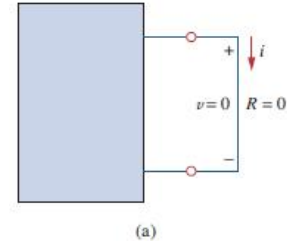A **short circuit** is a circuit element with resistance approaching zero.



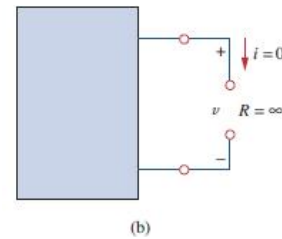An **open circuit** is a circuit element with resistance approaching infinity.



Dr. Hany Ahmed Atallah

## Ohms Law (6)



- **Conductance** is the ability of an element to conduct electric current; it is the reciprocal of resistance R and is measured in mhos or siemens.

$$G = \frac{1}{R} = \frac{i}{v}$$


- The power dissipated by a resistor:

$$p = vi = i^2 R = \frac{v^2}{R}$$

Dr. Hany Ahmed Atallah



# Type of Resistors

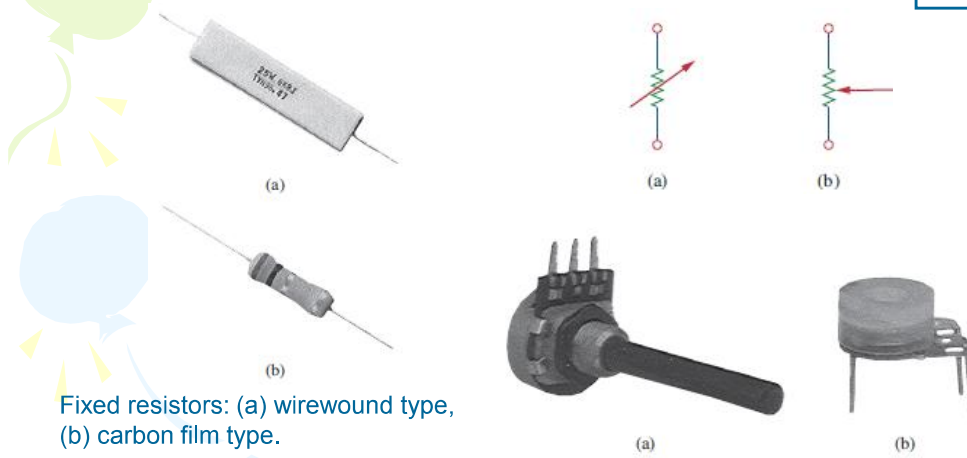


Fixed resistors: (a) wirewound type, (b) carbon film type.

Variable resistors: (a) composition type, (b) slider pot.

Dr. Hany Ahmed Atallah

# Resistor Color Code (1)

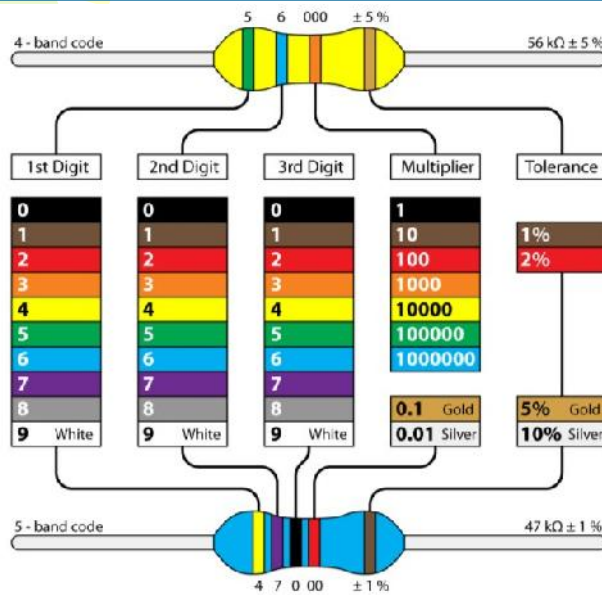

**Tolerance**  
**Gold 5%**  
**Silver 10%**  
**No 20%**


Dr. Hany Ahmed Atallah

## Resistor Color Code (2)



### سنحرص خزن مب

أبيض	رمادي	بنفسجي	أزرق	أخضر	أصفر	برتقالي	أحمر	بني	أسود
9	8	7	6	5	4	3	2	1	0

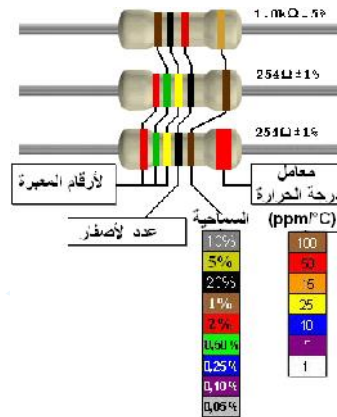

Dr. Hany Ahmed Atallah

## Resistor Color Code (3)




Colour	Digit	Multiplier	Tolerance
Black	0	1	
Brown	1	10	1%
Red	2	100	2%
Orange	3	1.000	
Yellow	4	10.000	
Green	5	100.000	0,5%
Blue	6	1.000.000	0,25%
Violet	7	10.000.000	0,1%
Grey	8		0,05%
White	9		
Gold		0,10	5%
Silver		0,01	10%

Dr. Hany Ahmed Atallah

## Series and Parallel Resistors Combinations




### 1-Series Resistors

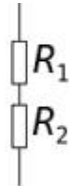

$$R_{TOTAL} = R_1 + R_2 \dots R_n$$

### 2-Parallel Resistors

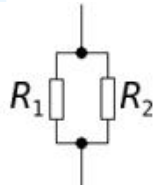


$$\frac{1}{R_{TOTAL}} = \frac{1}{R_1} + \frac{1}{R_2} \dots \frac{1}{R_n}$$

The **equivalent resistance** of two parallel resistors is equal to the product of their resistances divided by their sum.

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Dr. Hany Ahmed Atallah
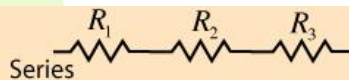
## Series and Parallel Resistors Combinations



Series

$$R_{equivalent} = R_1 + R_2 + R_3 + \dots$$

$$R_{equivalent} = \frac{V}{I} = \frac{V_1 + V_2 + V_3 + \dots}{I} = \frac{V_1}{I_1} + \frac{V_2}{I_2} + \frac{V_3}{I_3} + \dots = R_1 + R_2 + R_3 + \dots$$

Series key idea: The current is the same in each resistor by the current law.



Parallel

$$\frac{1}{R_{equivalent}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$\text{Parallel: } \frac{V}{R_{equivalent}} = I = I_1 + I_2 + I_3 + \dots = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \dots$$

$$\frac{1}{R_{equivalent}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

**Conductance**


$$G_{eq} = G_1 + G_2 + G_3 + \dots + G_N$$

Dr. Hany Ahmed Atallah

## Series and Parallel Resistors Combinations



### Exercises

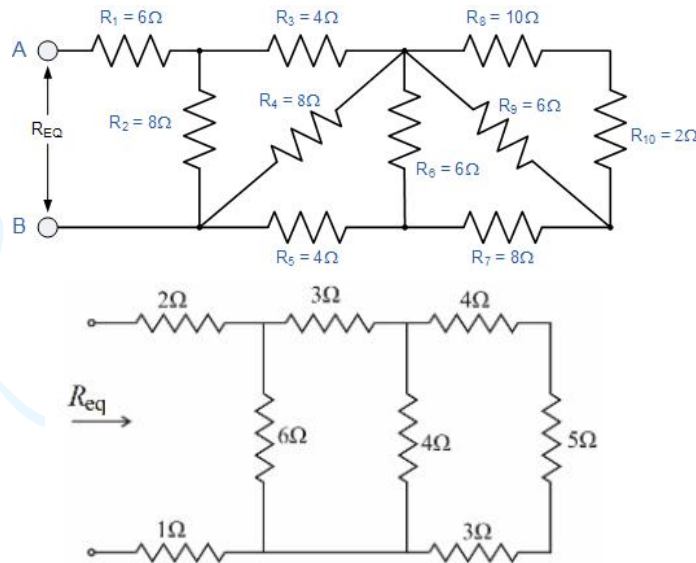


Dr. Hany Ahmed Atallah

## Nodes, Branches and Loops (1)



- A **branch** represents a single element such as a voltage source or a resistor. (ex.  $ac$ ,  $ab$ , ...)
- A **node** is the point of connection between two or more branches. (ex.  $a$ ,  $b$ ,  $c$ , ...)
- A **loop** is any closed path in a circuit.
- A network with  $b$  branches,  $n$  nodes, and  $l$  independent loops will satisfy the fundamental theorem of network topology:

$$b = l + n - 1$$

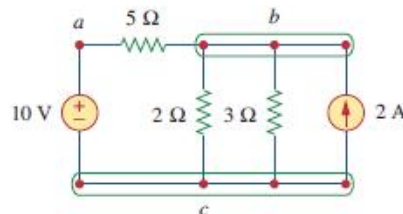


Dr. Hany Ahmed Atallah

## Nodes, Branches and Loops (2)




$$b = l + n - 1$$

### Example 1

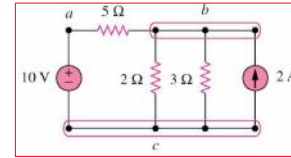

Original circuit

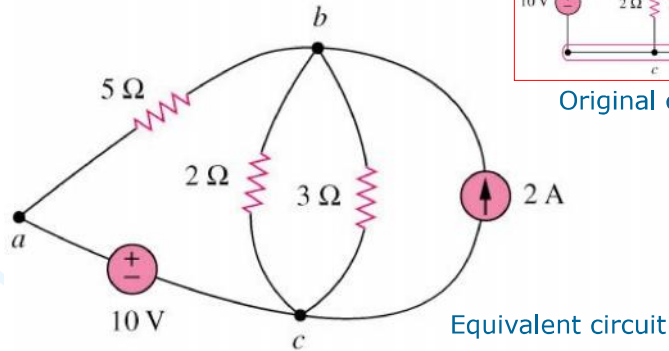

Equivalent circuit

How many branches, nodes and loops are there?

Dr. Hany Ahmed Atallah


## Nodes, Branches and Loops (3)



$$b = l + n - 1$$
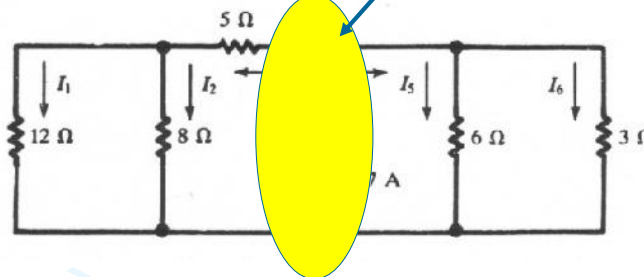
### Example 2

Should we consider it as one branch or two branches?



How many branches, nodes and loops are there?

Dr. Hany Ahmed Atallah



## Kirchhoff's Laws (1)



- **Kirchhoff's current law (KCL)** states that the algebraic sum of currents entering a node (or a closed boundary) is zero.



Gustav Robert Kirchhoff (1824-1887)

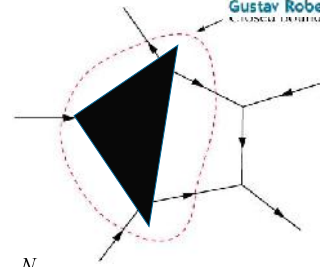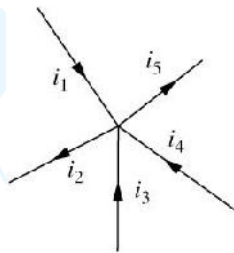

Mathematically,

$$\sum_{n=1}^N i_n = 0$$

where  $N$  is the number of branches connected to the node

Dr. Hany Ahmed Atallah


## Kirchhoff's Laws (2)



an alternative form of KCL: The sum of the currents entering a node is equal to the sum of the currents leaving the node.
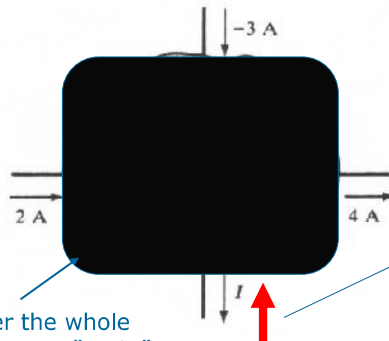
### Example 4

- Determine the current  $I$  for the circuit shown in the figure below.



$$I + 4 - (-3) - 2 = 0$$

$$\Rightarrow I = -5A$$

This indicates that the actual current for  $I$  is flowing in the opposite direction.


We can consider the whole enclosed area as one "node".

Dr. Hany Ahmed Atallah
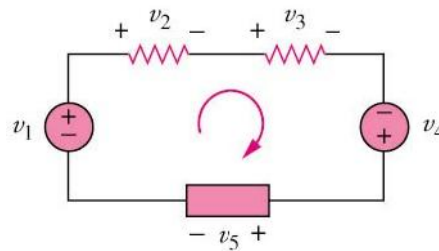
## Kirchhoff's Laws (3)



- **Kirchhoff's voltage law (KVL)** states that the algebraic sum of all voltages around a closed path (or loop) is zero.



Mathematically, 
$$\sum_{m=1}^M v_m = 0$$

where  $M$  is the number of voltages in the loop


Dr. Hany Ahmed Atallah

## Kirchhoff's Laws (4)


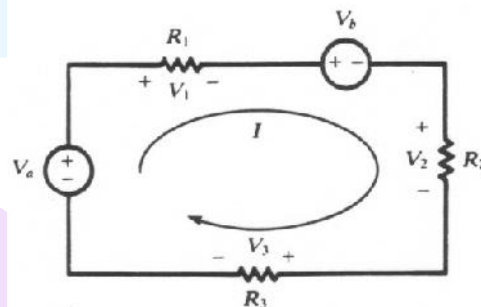
### Example 5

- Applying the KVL equation for the circuit of the figure below.



$$v_a - v_1 - v_b - v_2 - v_3 = 0$$

$$V_1 = IR_1 \quad v_2 = IR_2 \quad v_3 = IR_3$$

$$\Rightarrow v_a - v_b = I(R_1 + R_2 + R_3)$$

$$I = \frac{v_a - v_b}{R_1 + R_2 + R_3}$$

Dr. Hany Ahmed Atallah


## Kirchhoff's Laws (5)




an alternative form of KVL

**Sum of voltage drops = Sum of voltage rises**

$$v_2 + v_3 + v_5 = v_1 + v_4$$

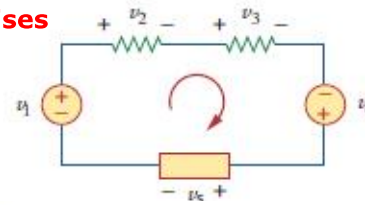

$$V_{ab} = V_1 + V_2 - V_3$$

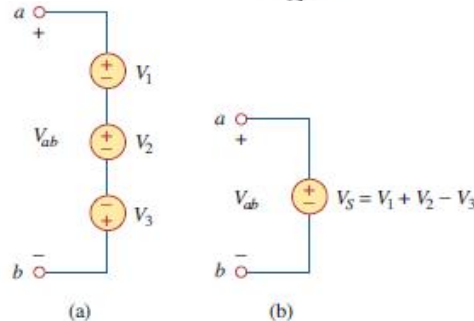

**Exercises: solving examples 2.5 to 2.8**

Dr. Hany Ahmed Atallah

## Series Resistors and Voltage Division (1)



- Series: Two or more elements are in series if they are cascaded or connected sequentially and consequently carry the same current.
- The equivalent resistance of any number of resistors connected in a series is the sum of the individual resistances.

$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{n=1}^N R_n$$

- The voltage divider can be expressed as

$$v_n = \frac{R_n}{R_1 + R_2 + \dots + R_N} v$$

Dr. Hany Ahmed Atallah



## Series Resistors and Voltage Division (2)



**KVL**


$$-v + v_1 + v_2 = 0$$

$$v = v_1 + v_2 = i(R_1 + R_2)$$

$$i = \frac{v}{R_1 + R_2}$$

$$v = iR_{eq}$$


$$R_{eq} = R_1 + R_2$$

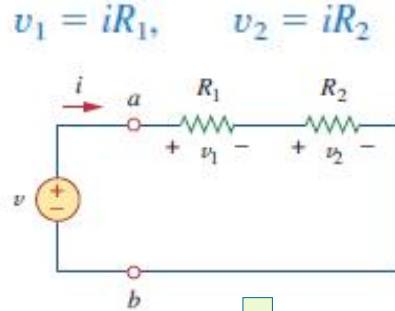

**Voltage Division**

$$v_1 = \frac{R_1}{R_1 + R_2} v,$$

$$v_2 = \frac{R_2}{R_1 + R_2} v$$

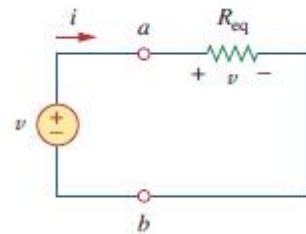


Dr. Hany Ahmed Atallah

## Series Resistors and Voltage Division (3)



**Example 3**

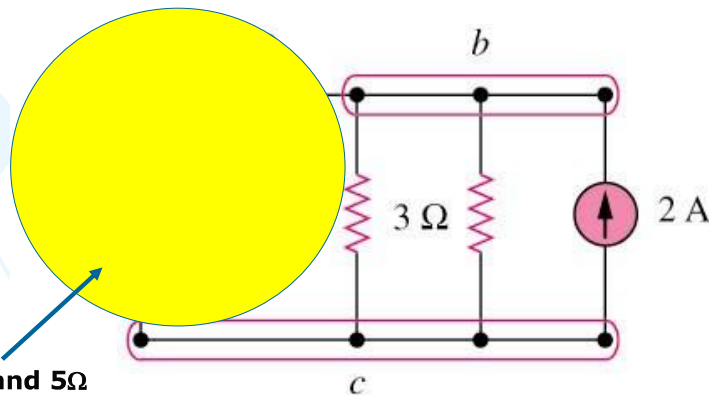

10V and 5Ω are in series

Dr. Hany Ahmed Atallah

## Parallel Resistors and Current Division (4)



- Parallel: Two or more elements are in parallel if they are connected to the same two nodes and consequently have the same voltage across them.
- The equivalent resistance of a circuit with N resistors in parallel is:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

- The total current  $i$  is shared by the resistors in inverse proportion to their resistances. The current divider can be expressed as:

$$i_n = \frac{v}{R_n} = \frac{iR_{eq}}{R_n}$$

Dr. Hany Ahmed Atallah

## Parallel Resistors and Current Division (5)



$$v = i_1 R_1 = i_2 R_2$$

$$i_1 = \frac{v}{R_1}, \quad i_2 = \frac{v}{R_2}$$


**KCL**  $i = i_1 + i_2$

$$i = \frac{v}{R_1} + \frac{v}{R_2} = v \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v}{R_{eq}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$
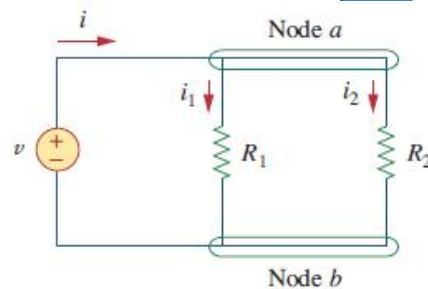
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$



Dr. Hany Ahmed Atallah

## Parallel Resistors and Current Division (6)



$$v = iR_{eq} = \frac{iR_1R_2}{R_1 + R_2}$$



$$i_1 = \frac{v}{R_1}, \quad i_2 = \frac{v}{R_2}$$

### Current Division

$$i_1 = \frac{R_2 i}{R_1 + R_2}, \quad i_2 = \frac{R_1 i}{R_1 + R_2}$$

$$i_1 = \frac{G_1}{G_1 + G_2} i, \quad i_2 = \frac{G_2}{G_1 + G_2} i$$

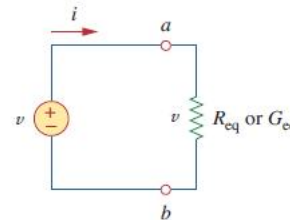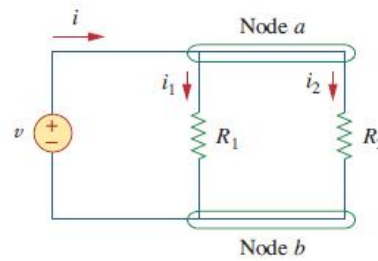
$$i_n = \frac{G_n}{G_1 + G_2 + \dots + G_N} i$$



$$G_{eq} = G_1 + G_2 + G_3 + \dots + G_N$$


Dr. Hany Ahmed Atallah
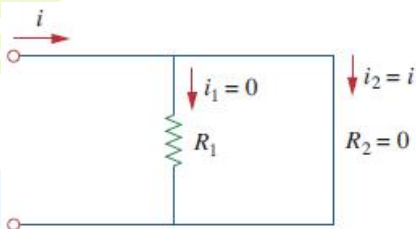
## Parallel Resistors and Current Division (7)



(a)

(a) A shorted circuit,

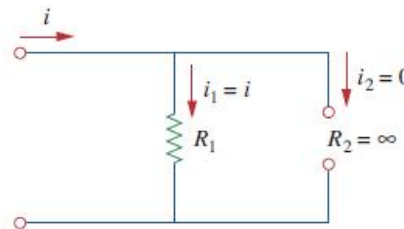


(b)

(b) an open circuit.

### Example

Find  $R_{eq}$

14.4  $\Omega$

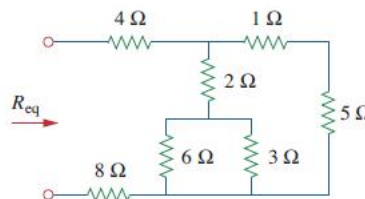


Dr. Hany Ahmed Atallah

## Parallel Resistors and Current Division (8)



### Example 4

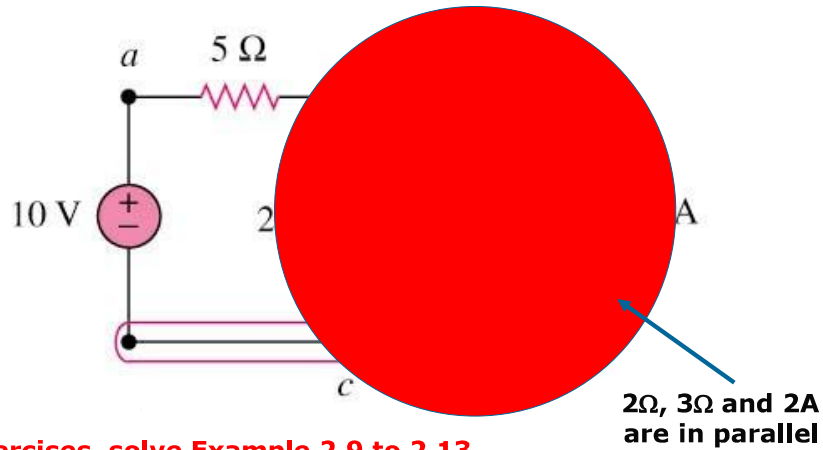


Exercises, solve Example 2.9 to 2.13

Dr. Hany Ahmed Atallah


## Wye-Delta Transformations (1)



the wye (Y) or tee (T) network

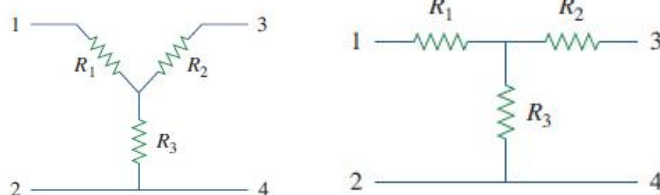

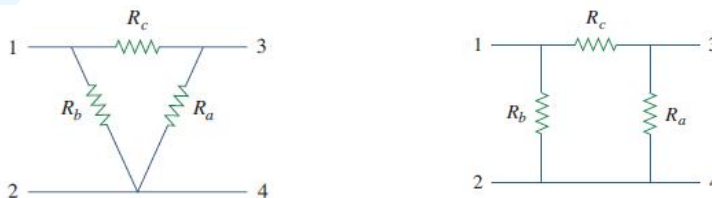the delta ( $\Delta$ ) or pi ( $\Pi$ ) network



Dr. Hany Ahmed Atallah

## Wye-Delta Transformations (2)




### Delta -> Star

$$R_1 = \frac{R_b R_c}{(R_a + R_b + R_c)}$$

$$R_2 = \frac{R_c R_a}{(R_a + R_b + R_c)}$$
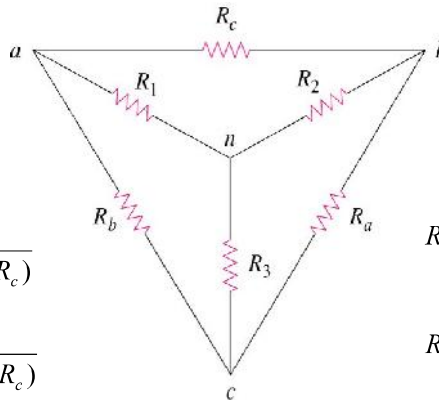
$$R_3 = \frac{R_a R_b}{(R_a + R_b + R_c)}$$



### Star -> Delta

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


**Exercises, solve Example 2.14 to 2.15**

Dr. Hany Ahmed Atallah


## Applications



### 1- Lighting Systems

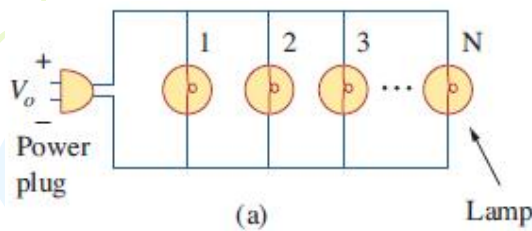


Parallel connection of light bulbs

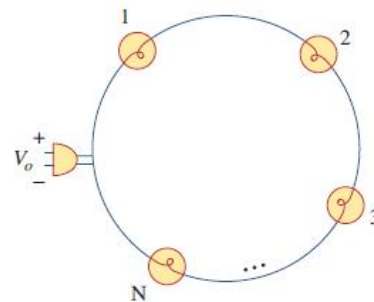

series connection of light bulbs.

**Thomas Alva Edison** (1847–1931)

**Invented the electric bulb**

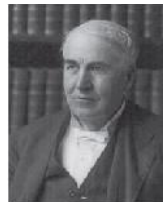

Dr. Hany Ahmed Atallah


## Applications



### 2- Design of DC Meters
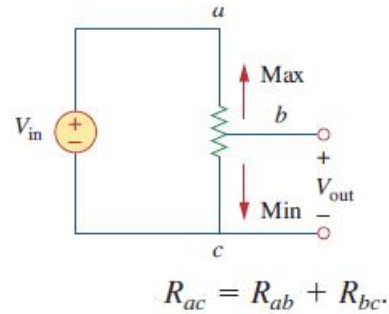
#### potentiometer

$$V_{out} = V_{bc} = \frac{R_{bc}}{R_{ac}} V_{in}$$



An instrument capable of measuring voltage, current, and resistance is called a *multimeter* or a *volt-ohm meter (VOM)*.


Dr. Hany Ahmed Atallah

## Applications



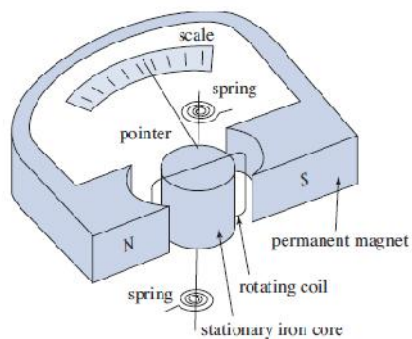
### 2- Design of DC Meters Moving Coil Instruments

An instrument capable of measuring **voltage**, **current**, and **resistance** is called a *multimeter* or a *volt-ohm meter (VOM)*.



d'Arsonval meter movement

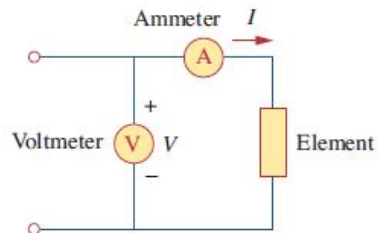

Dr. Hany Ahmed Atallah

# Home work



## Solving CH 2 Problems

Dr. Hany Ahmed Atallah

# Chapter 3

## Methods of Analysis



### Methods of Analysis - Chapter 3


- 3.1** Motivation
- 3.2** Nodal analysis.
- 3.3** Nodal analysis with voltage sources.
- 3.4** Mesh analysis.
- 3.5** Mesh analysis with current sources.
- 3.6** Nodal and mesh analysis by inspection.
- 3.7** Nodal versus mesh analysis.


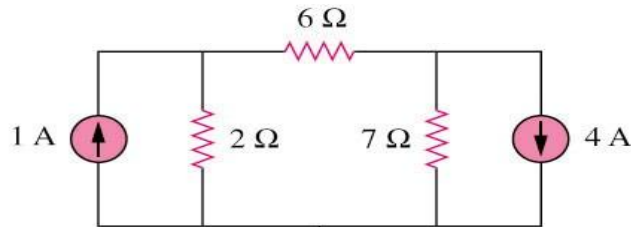
### 3.1 Motivation (1)



If you are given the following circuit, how can we determine (1) the voltage across each resistor, (2) current through each resistor. (3) power generated by each current source, etc.



What are the things which we need to know in order to determine the answers?

### 3.1 Motivation (2)



Things we need to know in solving any resistive circuit with current and voltage sources only:

- Kirchoff's Current Laws (KCL)
- Kirchoff's Voltage Laws (KVL)
- Ohm's Law


How should we apply these laws to determine the answers?

## 3.2 Nodal Analysis (1)



It provides a general procedure for analyzing circuits using **node voltages** as the circuit variables.

### Example 1

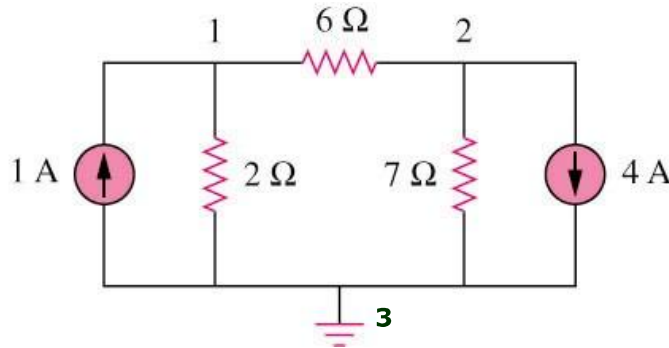

## 3.2 Nodal Analysis (2)



Steps to determine the node voltages:



1. Select a node as the reference node.
2. Assign voltages  $v_1, v_2, \dots, v_{n-1}$  to the remaining  $n-1$  nodes. The voltages are referenced with respect to the reference node.
3. Apply KCL to each of the  $n-1$  non-reference nodes. Use Ohm's law to express the branch currents in terms of node voltages.
4. Solve the resulting simultaneous equations to obtain the unknown node voltages.

## 3.2 Nodal Analysis (3)



### Example 2 – circuit independent current source only

Apply KCL at node 1 and 2

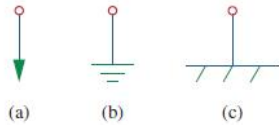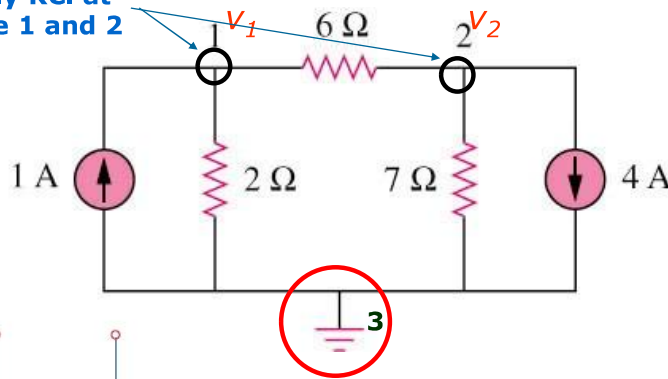

Common symbols for indicating a reference node, (a) common ground, (b) ground, (c) chassis ground.

\*Refer to in-class illustration, textbook, answer  $v_1 = -2V$ ,  $v_2 = -14V$


## 3.2 Nodal Analysis (4)



### Example


At node 1, applying KCL gives

$$I_1 = I_2 + i_1 + i_2$$

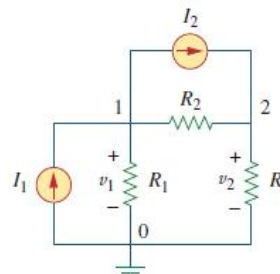

At node 2,

$$I_2 + i_2 = i_3$$

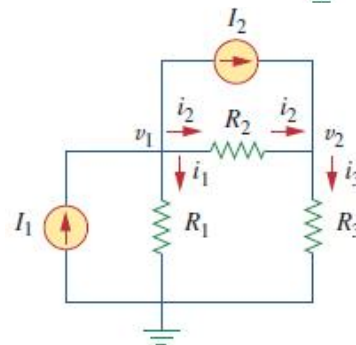


## 3.2 Nodal Analysis (5)



Current flows from a higher potential to a lower potential in

$$i = \frac{v_{\text{higher}} - v_{\text{lower}}}{R}$$
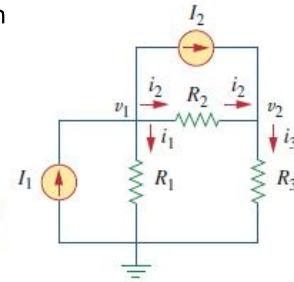
$$i_1 = \frac{v_1 - 0}{R_1} \quad i_2 = \frac{v_1 - v_2}{R_2} \quad i_3 = \frac{v_2 - 0}{R_3}$$



By Substituting

$$I_1 = I_2 + \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2}$$

$$I_2 + \frac{v_1 - v_2}{R_2} = \frac{v_2}{R_3}$$

$I_1$ ,  $I_2$ ,  $R_1$ ,  $R_2$ , and  $R_3$  are given

## Simultaneous Equations



### Appendix A Simultaneous Equations and Matrix Inversion

In circuit analysis, we often encounter a set of simultaneous equations having the form

$$a_{11}x_1 + a_{12}x_2 + \dots + a_{1n}x_n = b_1$$

$$a_{21}x_1 + a_{22}x_2 + \dots + a_{2n}x_n = b_2$$

$$\vdots \quad \quad \quad \vdots \quad \quad \quad \vdots$$

$$a_{n1}x_1 + a_{n2}x_2 + \dots + a_{nn}x_n = b_n$$

where there are  $n$  unknown to be determined. Equation (A.1) can be written in matrix form as

$$\begin{bmatrix} a_{11} & a_{12} & \dots & a_{1n} \\ a_{21} & a_{22} & \dots & a_{2n} \\ \vdots & \vdots & \dots & \vdots \\ a_{n1} & a_{n2} & \dots & a_{nn} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_n \end{bmatrix} = \begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_n \end{bmatrix}$$

## Simultaneous Equations



This matrix equation can be put in a compact form as

$$AX = B$$

where

$$A = \begin{bmatrix} a_{11} & a_{12} & \dots & a_{1n} \\ a_{21} & a_{22} & \dots & a_{2n} \\ \vdots & \vdots & \dots & \vdots \\ a_{n1} & a_{n2} & \dots & a_{nn} \end{bmatrix}, \quad X = \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_n \end{bmatrix}, \quad B = \begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_n \end{bmatrix}$$

## Cramer's Rule



Cramer's Rule where the  $\Delta_i$ 's are the determinants given by

$$x_1 = \frac{\Delta_1}{\Delta} \quad \Delta = \begin{vmatrix} a_{11} & a_{12} & \dots & a_{1n} \\ a_{21} & a_{22} & \dots & a_{2n} \\ \vdots & \vdots & \dots & \vdots \\ a_{n1} & a_{n2} & \dots & a_{nn} \end{vmatrix}, \quad \Delta_1 = \begin{vmatrix} b_1 & a_{12} & \dots & a_{1n} \\ b_2 & a_{22} & \dots & a_{2n} \\ \vdots & \vdots & \dots & \vdots \\ b_n & a_{n2} & \dots & a_{nn} \end{vmatrix}$$

$$x_2 = \frac{\Delta_2}{\Delta} \quad \vdots$$

$$x_n = \frac{\Delta_n}{\Delta} \quad \Delta_2 = \begin{vmatrix} a_{11} & b_1 & \dots & a_{1n} \\ a_{21} & b_2 & \dots & a_{2n} \\ \vdots & \vdots & \dots & \vdots \\ a_{n1} & b_n & \dots & a_{nn} \end{vmatrix}, \dots, \Delta_n = \begin{vmatrix} a_{11} & a_{12} & \dots & b_1 \\ a_{21} & a_{22} & \dots & b_2 \\ \vdots & \vdots & \dots & \vdots \\ a_{n1} & a_{n2} & \dots & b_n \end{vmatrix}$$

## Cramer's Rule



$$\Delta = \begin{vmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{vmatrix} = a_{11}a_{22} - a_{12}a_{21}$$

$$\begin{aligned} \Delta &= \begin{vmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{vmatrix} = a_{11}(-1)^2 \begin{vmatrix} a_{22} & a_{23} \\ a_{32} & a_{33} \end{vmatrix} + a_{21}(-1)^3 \begin{vmatrix} a_{12} & a_{13} \\ a_{32} & a_{33} \end{vmatrix} \\ &\quad + a_{31}(-1)^4 \begin{vmatrix} a_{12} & a_{13} \\ a_{22} & a_{23} \end{vmatrix} \\ &= a_{11}(a_{22}a_{33} - a_{32}a_{23}) - a_{21}(a_{12}a_{33} - a_{32}a_{13}) \\ &\quad + a_{31}(a_{12}a_{23} - a_{22}a_{13}) \end{aligned}$$

## Cramer's Rule - Example



$$\begin{aligned} 4x_1 - 3x_2 &= 17, \\ -3x_1 + 5x_2 &= -21 \end{aligned}$$

$$\begin{bmatrix} 4 & -3 \\ -3 & 5 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} 17 \\ -21 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 4 & -3 \\ -3 & 5 \end{vmatrix} = 4 \times 5 - (-3)(-3) = 11$$

$$\Delta_1 = \begin{vmatrix} 17 & -3 \\ -21 & 5 \end{vmatrix} = 17 \times 5 - (-3)(-21) = 22$$

$$\Delta_2 = \begin{vmatrix} 4 & 17 \\ -3 & -21 \end{vmatrix} = 4 \times (-21) - 17 \times (-3) = -33$$

$$x_1 = \frac{\Delta_1}{\Delta} = \frac{22}{11} = 2, \quad x_2 = \frac{\Delta_2}{\Delta} = \frac{-33}{11} = -3$$

## Cramer's Rule - Example



Obtain the solution of this set of simultaneous equations:

$$\begin{aligned} 3x_1 - x_2 - 2x_3 &= 1 \\ -x_1 + 6x_2 - 3x_3 &= 0 \\ -2x_1 - 3x_2 + 6x_3 &= 6 \end{aligned}$$

**Answer:**  $x_1 = 3 = x_3, x_2 = 2.$

## The elimination method for solving linear systems



Another way of solving a linear system is to use the elimination method. In the elimination method you either add or subtract the equations to get an equation in one variable.

$$\begin{aligned} 3y + 2x &= 6 \\ 5y - 2x &= 10 \end{aligned}$$

We can eliminate the x-variable by addition of the two equations.

$$\begin{aligned} 3y + 2x &= 6 \\ + 5y - 2x &= 10 \\ \hline 8y &= 16 \\ y &= 2 \end{aligned}$$

The value of y can now be substituted into either of the original equations to find the value of x

$$\begin{aligned} 3y + 2x &= 6 \\ 3 \cdot 2 + 2x &= 6 \\ 6 + 2x &= 6 \\ \hline x &= 0 \end{aligned}$$

## The Gaussian elimination method for solving linear systems



$$\begin{array}{l}
 3x + 5y = 9 \\
 2x + 3y = 5
 \end{array}
 \quad \text{Want: } \left| \begin{array}{cc|c} 1 & 0 & x \\ 0 & 1 & y \end{array} \right|$$
  

$$\left| \begin{array}{cc|c} 3 & 5 & 9 \\ 2 & 3 & 5 \end{array} \right| \dots \left| \begin{array}{cc|c} 1 & 0 & -2 \\ 0 & 1 & 3 \end{array} \right| = \begin{array}{l} x \\ y \end{array}$$

## The Gaussian elimination method for solving linear systems



$$\begin{array}{l}
 2x + 3y = 7 \\
 3x - 2y = 4
 \end{array}$$

Solve for x and y

$$\left[ \begin{array}{cc|c} 2 & 3 & 7 \\ 3 & -2 & 4 \end{array} \right]$$

$$\left[ \begin{array}{cc|c} 1 & \frac{3}{2} & \frac{7}{2} \\ 3 & -2 & 4 \end{array} \right]$$

$R_2 = r_2 + r_1 * -3$

$$\left[ \begin{array}{cc|c} 1 & \frac{3}{2} & \frac{7}{2} \\ 0 & \frac{-13}{2} & \frac{-13}{2} \end{array} \right]$$

$$\left[ \begin{array}{cc|c} 1 & \frac{3}{2} & \frac{7}{2} \\ 0 & 1 & 1 \end{array} \right]$$

$R_2 = r_2 * -2/13$

$$\left[ \begin{array}{cc|c} 1 & 0 & 2 \\ 0 & 1 & 1 \end{array} \right]$$

$\uparrow$   
x

$\uparrow$   
y

$R_1 = r_1 + r_2 * -2/3$

$$\begin{array}{l}
 x = 2 \\
 y = 1
 \end{array}$$



## The Gaussian elimination method for solving linear systems



$$\begin{aligned} x + 2y - z &= -2 \\ x &+ z = 0 \\ 2x - y - z &= -3 \end{aligned}$$

Solve for  $x$ ,  $y$ , and  $z$

$$\left[ \begin{array}{ccc|c} 1 & 2 & -1 & -2 \\ 1 & 0 & 1 & 0 \\ 2 & -1 & -1 & -3 \end{array} \right]$$

$$\left[ \begin{array}{ccc|c} 1 & 2 & -1 & -2 \\ 0 & -2 & 2 & 2 \\ 0 & -5 & 1 & 1 \end{array} \right]$$



$$\left[ \begin{array}{ccc|c} 1 & 0 & 1 & 0 \\ 0 & 1 & -1 & -1 \\ 0 & 0 & -4 & -4 \end{array} \right]$$

$$\left[ \begin{array}{ccc|c} 1 & 0 & 0 & -1 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 1 \end{array} \right] \quad \begin{aligned} x &= -1 \\ y &= 0 \\ z &= 1 \end{aligned}$$

## 3.2 Nodal Analysis (6)



**Example**

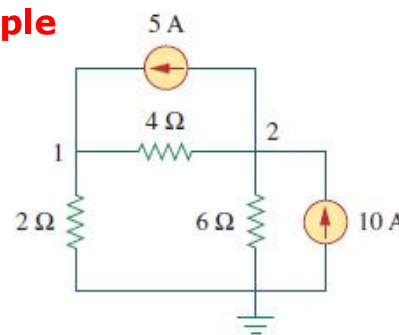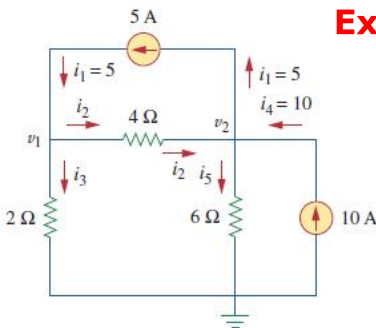

At node 1, applying KCL and Ohm's law gives

$$i_1 = i_2 + i_3 \quad \Rightarrow \quad 5 = \frac{v_1 - v_2}{4} + \frac{v_1 - 0}{2}$$

$$3v_1 - v_2 = 20$$

## 3.2 Nodal Analysis (7)



At node 2, we do the same thing and get


$$i_2 + i_4 = i_1 + i_5 \Rightarrow \frac{v_1 - v_2}{4} + 10 = 5 + \frac{v_2 - 0}{6}$$

$$-3v_1 + 5v_2 = 60$$

**Equations**

$$3v_1 - v_2 = 20$$

$$-3v_1 + 5v_2 = 60$$

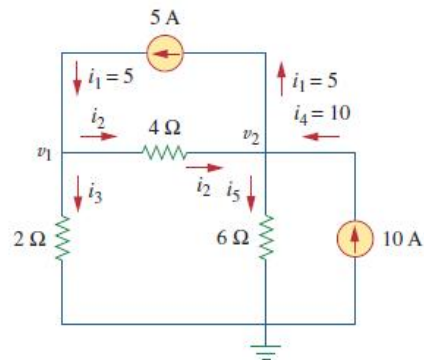

## 3.2 Nodal Analysis (8)



**METHOD 1 Using the elimination technique**

$$3v_1 - v_2 = 20$$

$$-3v_1 + 5v_2 = 60$$

we add Eqs.

$$4v_2 = 80 \Rightarrow v_2 = 20 \text{ V}$$

Substituting

$$3v_1 - 20 = 20 \Rightarrow v_1 = \frac{40}{3} = 13.333 \text{ V}$$

If we need the currents, we can easily calculate them from the values of the nodal voltages.

$$i_1 = 5 \text{ A}, \quad i_2 = \frac{v_1 - v_2}{4} = -1.6668 \text{ A}, \quad i_3 = \frac{v_1}{2} = 6.666 \text{ A}$$

$$i_4 = 10 \text{ A}, \quad i_5 = \frac{v_2}{6} = 3.333 \text{ A}$$

## 3.2 Nodal Analysis (9)



**METHOD 2** To use Cramer's rule,

$$\begin{aligned} 3v_1 - v_2 &= 20 \\ -3v_1 + 5v_2 &= 60 \end{aligned} \quad \begin{bmatrix} 3 & -1 \\ -3 & 5 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 60 \end{bmatrix}$$

The determinant of the matrix is

$$\Delta = \begin{vmatrix} 3 & -1 \\ -3 & 5 \end{vmatrix} = 15 - 3 = 12$$

$$v_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 20 & -1 \\ 60 & 5 \end{vmatrix}}{\Delta} = \frac{100 + 60}{12} = 13.333 \text{ V}$$


$$v_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 3 & 20 \\ -3 & 60 \end{vmatrix}}{\Delta} = \frac{180 + 60}{12} = 20 \text{ V}$$

**Exercise Example 3.2**

## 3.2 Nodal Analysis (10)



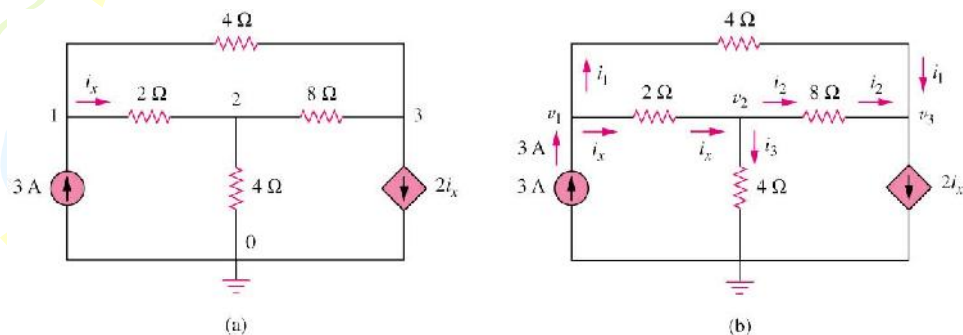**Example 3** – current with dependant current source




answer  $v_1 = 4.8\text{V}$ ,  $v_2 = 2.4\text{V}$ ,  $v_3 = -2.4\text{V}$

### 3.3 Nodal Analysis with Voltage Source (1)



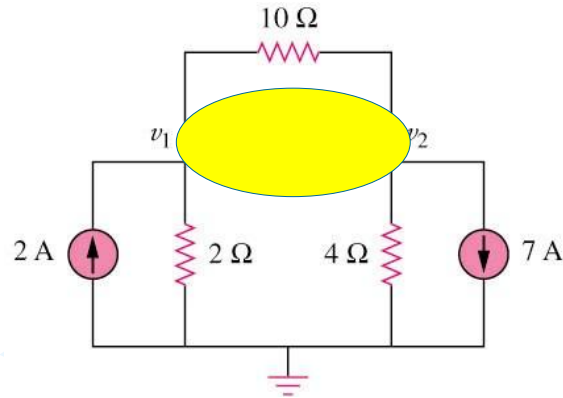**Example 4** –circuit with independent voltage source



How to handle the 2V voltage source?

### 3.3 Nodal Analysis with Voltage Source (2)



A super-node is formed by enclosing a (dependent or independent) voltage source connected between two non-reference nodes and any elements connected in parallel with it.

\*Note: We analyze a circuit with super-nodes using the same three steps mentioned above except that the super-nodes are treated differently.

### 3.3 Nodal Analysis with Voltage Source (3)



Basic steps:

1. Take off all voltage sources in super-nodes and apply KCL to super-nodes.
2. Put voltage sources back to the nodes and apply KVL to relative loops.


### 3.3 Nodal Analysis with Voltage Source (4)



**Example 5 – circuit with independent voltage source**

Super-node  $\Rightarrow 2 - i_1 - i_2 - 7 = 0$

$i_1 = v_1/2$  ,  $i_2 = v_2/4$

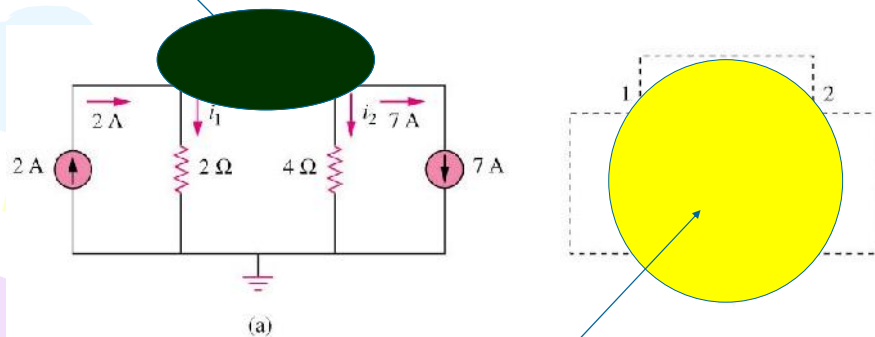


Apply KVL  $\Rightarrow v_1 + 2 - v_2 = 0$

### 3.3 Nodal Analysis with Voltage Source (5)



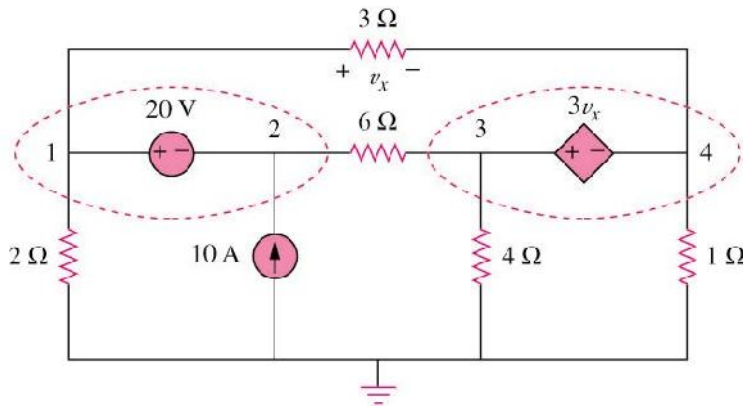
**Example 6** – circuit with two independent voltage sources



### 3.3 Nodal Analysis with Voltage Source (6)



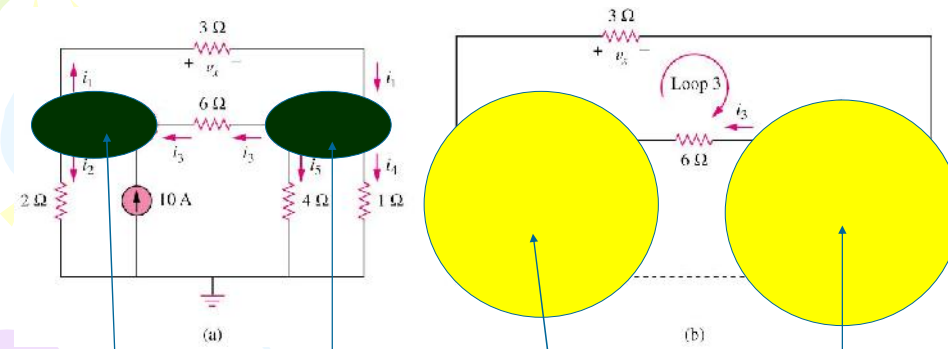**Example 7** – circuit with two independent voltage sources



$$-i_1 - i_2 + 10 + i_3 = 0 \quad -i_3 - i_5 - i_4 + i_1 = 0 \quad v_1 - 20 - v_2 = 0 \quad v_3 - 3v_x - v_4 = 0$$

## 3.4 Mesh or Loop Analysis (1)



1. Mesh analysis provides another general procedure for analyzing circuits using mesh currents as the circuit variables.
2. Nodal analysis applies KCL to find unknown voltages in a given circuit, while mesh analysis applies KVL to find unknown currents.
3. A mesh is a loop which does not contain any other loops within it.

## 3.4 Mesh Analysis (2)




Steps to determine the mesh currents:

1. Assign mesh currents  $i_1, i_2, \dots$ , in to the  $n$  meshes.
2. Apply KVL to each of the  $n$  meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
3. Solve the resulting  $n$  simultaneous equations to get the mesh currents.

## 3.4 Mesh Analysis (3)


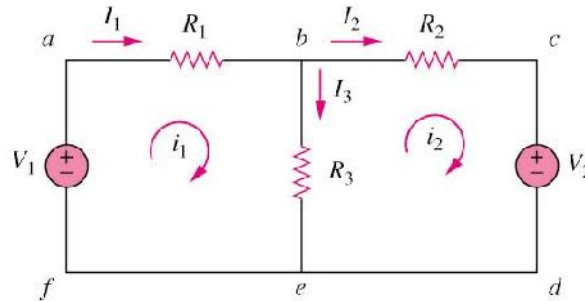
### Example 8 – circuit with independent voltage sources



**Note:**

$i_1$  and  $i_2$  are mesh current (imaginative, not measurable directly)

$I_1$ ,  $I_2$  and  $I_3$  are branch current (real, measurable directly)

$$I_1 = i_1; I_2 = i_2; I_3 = i_1 - i_2$$


## 3.4 Mesh Analysis (4)



As the second step, we apply KVL to each mesh. Applying KVL to mesh 1, we obtain

$$-V_1 + R_1 i_1 + R_3 (i_1 - i_2) = 0$$

$$(R_1 + R_3) i_1 - R_3 i_2 = V_1$$

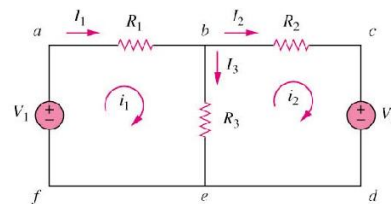

For mesh 2, applying KVL gives

$$R_2 i_2 + V_2 + R_3 (i_2 - i_1) = 0$$

$$-R_3 i_1 + (R_2 + R_3) i_2 = -V_2$$

$$I_1 = i_1, \quad I_2 = i_2, \quad I_3 = i_1 - i_2$$

$$\begin{bmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$



### 3.4 Mesh Analysis (5)



**Apply mesh analysis to find  $V_o$  in the circuit**

We first obtain the mesh currents using KVL. For mesh 1,


$$-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$$

$$3i_1 - 2i_2 = 1$$

For mesh 2,

$$6i_2 + 4i_2 + 10(i_2 - i_1) - 10 = 0$$

$$i_1 = 2i_2 - 1$$

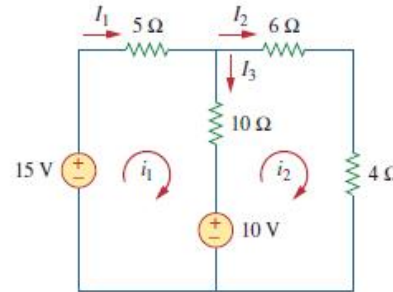


$$\begin{bmatrix} 3 & -2 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix} \quad \begin{matrix} i_1 = 1 \text{ A} \\ i_2 = 1 \text{ A} \end{matrix}$$

$$I_1 = i_1 = 1 \text{ A}, \quad I_2 = i_2 = 1 \text{ A}, \quad I_3 = i_1 - i_2 = 0$$

### 3.4 Mesh Analysis (6)



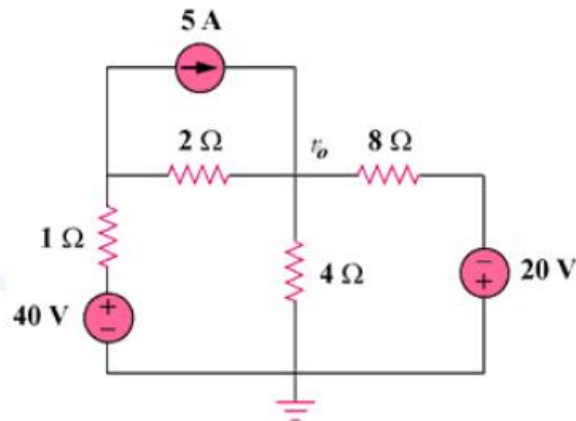**Apply mesh analysis to find  $V_o$  in the circuit**




\* answer  $v_o = 20 \text{ v}$

## 3.4 Mesh Analysis (7)


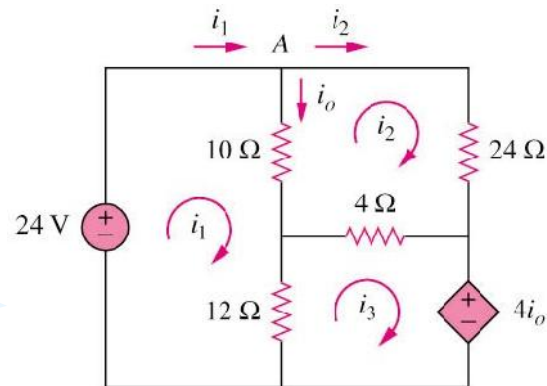
### Example 9 – circuit with dependent voltage source




\*Refer to in-class illustration, textbook, answer  $I_o = 1.5A$


## 3.5 Mesh Analysis with Current Source (1)



### Circuit with current source

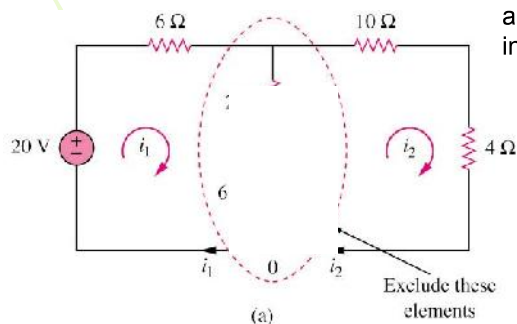

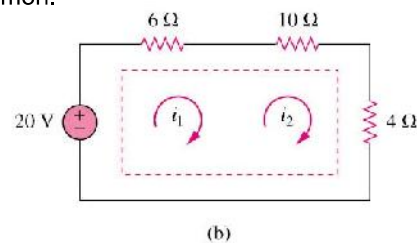A **supermesh** results when two meshes have a (dependent or independent) current source in common.



A **super-mesh** results when two meshes have a (dependent or independent) current source in common as shown in (a). We create a super-mesh by excluding the current source and any elements connected in series with it as shown in (b).

## 3.5 Mesh Analysis with Current Source (1)




applying **KVL** to the supermesh

$$-20 + 6i_1 + 10i_2 + 4i_2 = 0$$

$$6i_1 + 14i_2 = 20$$

We apply **KCL** to a node in the branch where the two meshes intersect. Applying KCL to node 0

$$i_2 = i_1 + 6$$

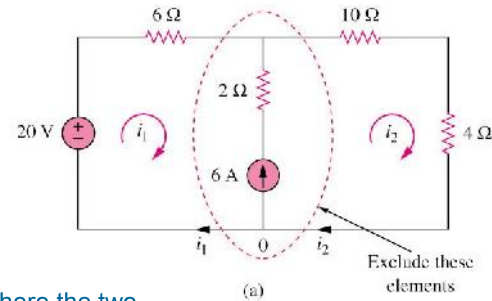

$$i_1 = -3.2 \text{ A}, \quad i_2 = 2.8 \text{ A}$$

**Exercise Example 3.7**

## 3.5 Mesh Analysis with Current Source (2)



The properties of a **super-mesh**:

1. The current source in the super-mesh is not completely ignored; it provides the constraint equation necessary to solve for the mesh currents.
2. A super-mesh has no current of its own.
3. A super-mesh requires the application of both KVL and KCL.

## 3.7 Nodal versus Mesh Analysis (1)



To select the method that results in the smaller number of equations. For example:

1. Choose nodal analysis for circuit with fewer nodes than meshes.
  - \*Choose mesh analysis for circuit with fewer meshes than nodes.
  - \*Networks that contain many series connected elements, voltage sources, or supermeshes are more suitable for mesh analysis.
  - \*Networks with parallel-connected elements, current sources, or supernodes are more suitable for nodal analysis.
2. If node voltages are required, it may be expedient to apply nodal analysis. If branch or mesh currents are required, it may be better to use mesh analysis.



# Chapter 4

## Circuit Theorems



## Circuit Theorems - Chapter 4



- 4.1** Motivation and Introduction
- 4.2** Linearity Property.
- 4.3** Superposition.
- 4.4** Source Transformation.
- 4.5** Thevenin's Theorem.
- 4.6** Norton's Theorem.
- 4.8** Maximum Power Transfer.

## 4.1 Motivation (1)



Enhancing Your Skills and Your Career


*Your success as an engineer will be directly proportional to your ability to communicate!*

—Charles K. Alexander
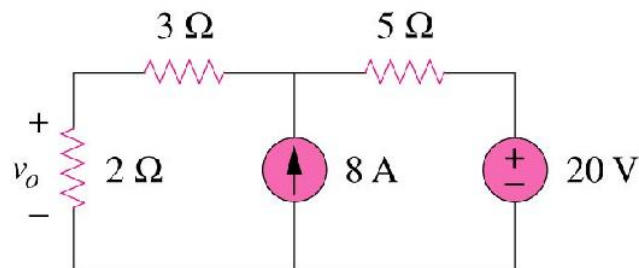
## 4.1 Motivation (2)



If you are given the following circuit, are there any other alternative(s) to determine the voltage across  $2\Omega$  resistor?



What are they? And how?

## 4.2 Linearity Property (1)



It is the property of an element describing a linear relationship between cause and effect.

The property is a combination of both the homogeneity (scaling) property and the additivity property.

A linear circuit is one whose output is linearly related (or directly proportional) to its input.

### Homogeneity (scaling) property

If the current is increased by a constant  $k$ , then the voltage increases correspondingly by  $k$ ;

$$v = i R \quad \rightarrow \quad k v = k i R$$

## 4.2 Linearity Property (1)



### Additive property

The additivity property requires that the response to a sum of inputs is the sum of the responses to each input applied separately.


$$v_1 = i_1 R \quad \text{and} \quad v_2 = i_2 R$$

then applying  $(i_1 + i_2)$  gives

$$\rightarrow v = (i_1 + i_2) R = v_1 + v_2$$

**We say that a resistor is a linear element because the voltage-current relationship satisfies both the homogeneity and the additivity properties.**

## 4.2 Linearity Property (2)

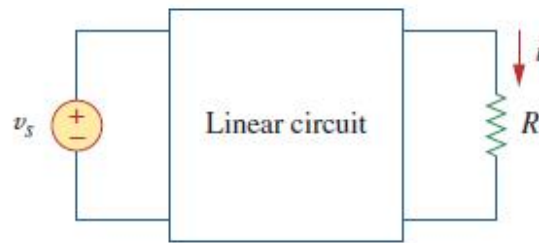

Suppose  $v_s = 10 \text{ V}$  gives  $i = 2 \text{ A}$ . According to the linearity principle,  $v_s = 1 \text{ V}$  will give  $i = 0.2 \text{ A}$ . By the same token,  $i = 1 \text{ mA}$  must be due to  $v_s = 5 \text{ mV}$ .


\*Refer to in-class illustration, text book, answer  $I_o = 3 \text{ A}$

## 4.2 Linearity Property (2)


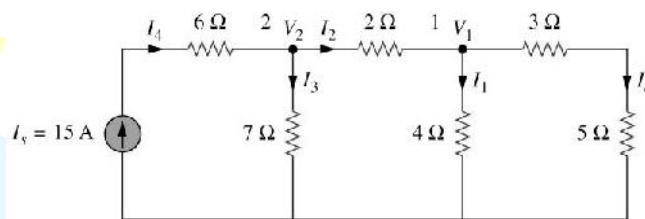
### Example 1

By assume  $I_o = 1 \text{ A}$ , use linearity to find the actual value of  $I_o$  in the circuit shown below.



If  $I_o = 1 \text{ A}$ , then  $V_1 = (3 + 5)I_o = 8 \text{ V}$  and  $I_1 = V_1/4 = 2 \text{ A}$ . Applying KCL at node 1 gives

$$I_2 = I_1 + I_o = 3 \text{ A}$$

$$V_2 = V_1 + 2I_2 = 8 + 6 = 14 \text{ V}, \quad I_3 = \frac{V_2}{7} = 2 \text{ A}$$

Applying KCL at node 2 gives

$$I_4 = I_3 + I_2 = 5 \text{ A}$$

Therefore,  $I_s = 5 \text{ A}$ . This shows that assuming  $I_o = 1$  gives  $I_s = 5 \text{ A}$ , the actual source current of  $15 \text{ A}$  will give  $I_o = 3 \text{ A}$  as the actual value.

\*Refer to in-class illustration, text book, answer  $I_o = 3 \text{ A}$



### 4.3 Superposition Theorem (1)




It states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltage across (or currents through) that element due to EACH independent source acting alone.

The principle of superposition helps us to analyze a linear circuit with more than one independent source by calculating the contribution of each independent source separately.
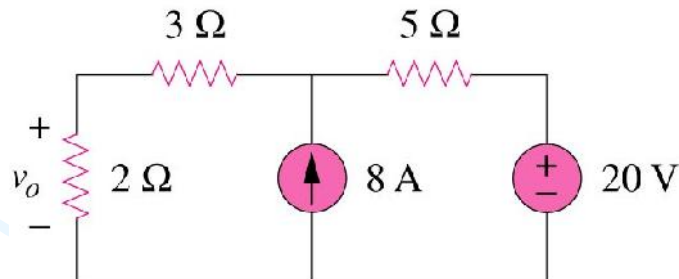
### 4.3 Superposition Theorem (2)



We consider the effects of 8A and 20V one by one, then add the two effects together for final  $v_o$ .



### 4.3 Superposition Theorem (3)



Steps to apply superposition principle

1. Turn off all independent sources except one source. Find the output (voltage or current) due to that active source using nodal or mesh analysis.
2. Repeat step 1 for each of the other independent sources.
3. Find the total contribution by adding algebraically all the contributions due to the independent sources.

### 4.3 Superposition Theorem (4)



Two things have to be keep in mind:


1. When we say turn off all other independent sources:
  - Independent voltage sources are replaced by 0 V (short circuit) and
  - Independent current sources are replaced by 0 A (open circuit).
2. Dependent sources are left intact because they are controlled by circuit variables.

## 4.3 Superposition Theorem (5)


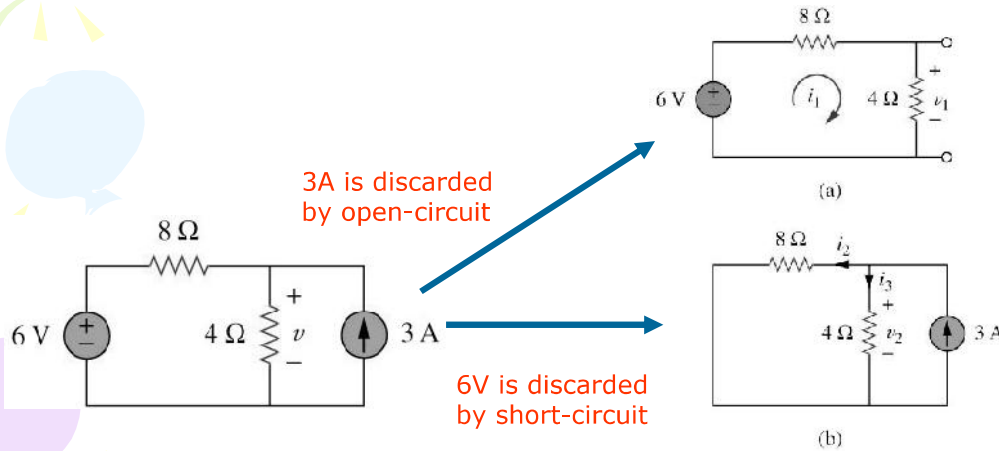
### Example 2

Use the superposition theorem to find  $v$  in the circuit shown below.




\*Refer to in-class illustration, text book, answer  $v = 10V$

## 4.3 Superposition Theorem (5)



(a) calculating  $v_1$ ,

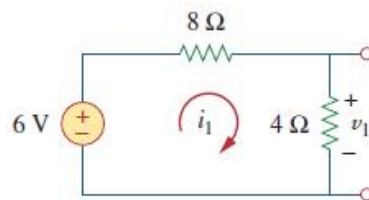

we set the current source to zero

Applying KVL to the loop

$$12i_1 - 6 = 0 \quad \Rightarrow \quad i_1 = 0.5 \text{ A}$$

$$v_1 = 4i_1 = 2 \text{ V}$$

We may also use voltage division to get  $v_1$  by writing


$$v_1 = \frac{4}{4 + 8}(6) = 2 \text{ V}$$

## 4.3 Superposition Theorem (5)



(b) calculating  $v_2$ .

we set the voltage source to zero

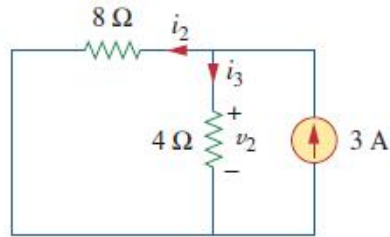

Using current division,

$$(b) \quad i_3 = \frac{8}{4 + 8}(3) = 2 \text{ A}$$

$$v_2 = 4i_3 = 8 \text{ V}$$

Use the superposition theorem

$$v = v_1 + v_2 = 2 + 8 = 10 \text{ V}$$


## 4.3 Superposition Theorem (6)



### Example 3

Use superposition to find  $v_x$  in the circuit below.


$$v = v_1 + v_2$$

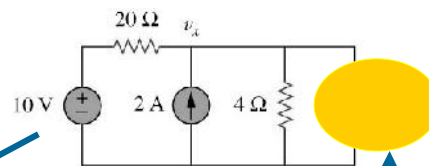


2A is discarded by open-circuit

10V is discarded by open-circuit

Dependant source keep unchanged

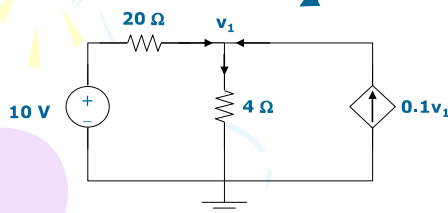

(a)

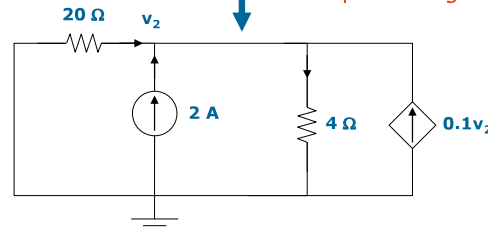

(b)


\*Refer to in-class illustration, text book, answer  $V_x = 12.5\text{V}$

## 4.4 Source Transformation (1)



- It is the process of replacing a voltage source  $v_s$  in series with a resistor  $R$  by a current source  $i_s$  in parallel with a resistor  $R$ , or vice versa.
- An equivalent circuit is one whose  $v-i$  characteristics are identical with the original circuit.

## 4.4 Source Transformation (2)

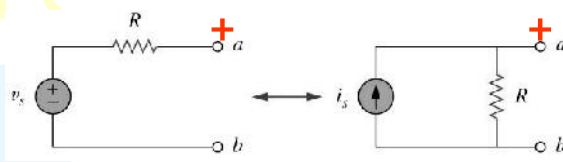


(a) Independent source transform

$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$

- The arrow of the current source is directed toward the positive terminal of the voltage source.
- The source transformation is not possible when  $R = 0$  for voltage source and  $R = \infty$  for current source.

## 4.4 Source Transformation (3)

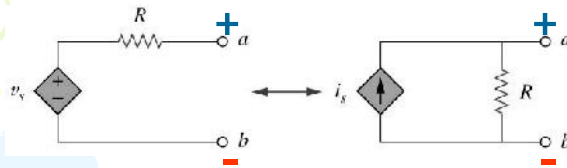

(b) Dependent source transform


$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$

- The arrow of the current source is directed toward the positive terminal of the voltage source.
- The source transformation is not possible when  $R = 0$  for voltage source and  $R = \infty$  for current source.

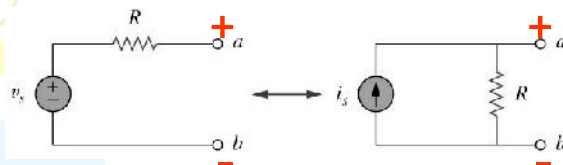
## 4.4 Source Transformation (2)



$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$



(a) Independent source transform

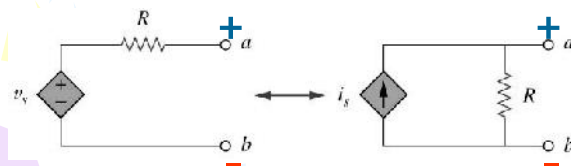

(b) Dependent source transform



- The arrow of the current source is directed toward the positive terminal of the voltage source.
- The source transformation is not possible when  $R = 0$  for voltage source and  $R = \infty$  for current source.

## 4.4 Source Transformation (3)


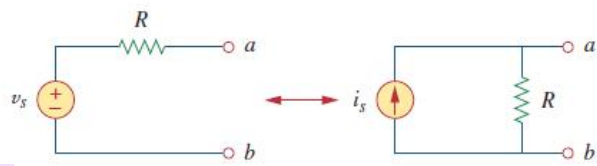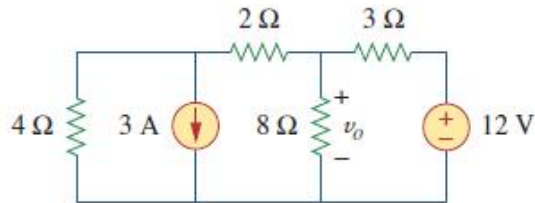
### Example 4

Using source transformation to find  $v_o$  in the circuit shown below.



$$i_s = \frac{v_s}{R}$$

$$i_s = 4 \text{ A}$$


$$R = 3 \text{ ohms}$$

## 4.4 Source Transformation (4)



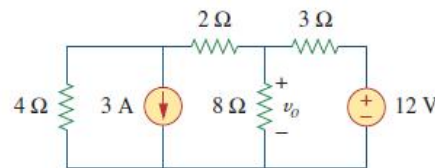
### Example 4

Using source transformation to find  $v_o$  in the circuit shown below.


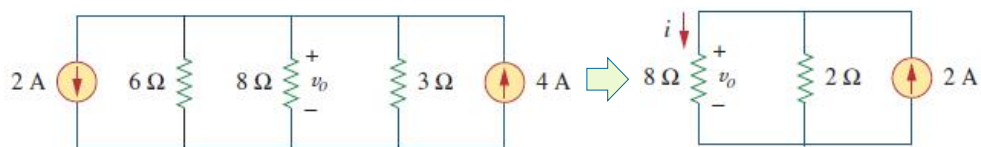
$$3 \parallel 6 = \frac{3 \cdot 6}{9} = 2 \text{ ohms}$$



We use current division

$$i = \frac{2}{2 + 8}(2) = 0.4 \text{ A}$$


$$v_o = 8i = 8(0.4) = 3.2 \text{ V}$$

## 4.4 Source Transformation (5)


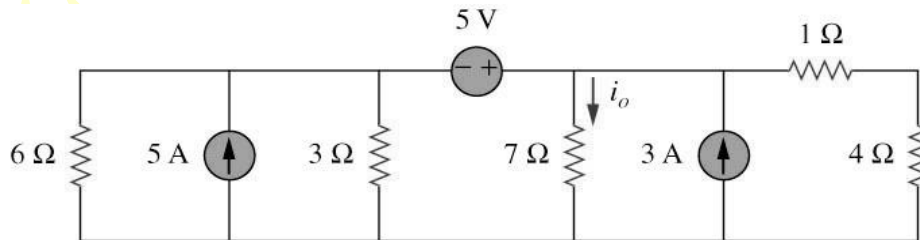
### Example 4

Find  $i_o$  in the circuit shown below using source transformation.



\*Refer to in-class illustration, textbook, answer  $i_o = 1.78A$


## 4.5 Thevenin's Theorem (1)




It states that a linear two-terminal circuit (Fig. a) can be replaced by an equivalent circuit (Fig. b) consisting of a voltage source  $V_{TH}$  in series with a resistor  $R_{TH}$ .

where

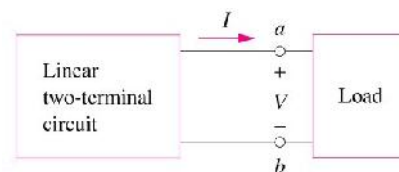- $V_{TH}$  is the open-circuit voltage at the terminals.
- $R_{TH}$  is the input or equivalent resistance at the terminals when the **independent** sources are **turned off**.



(a)

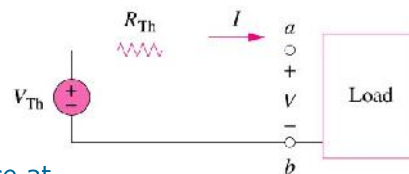

(b)



## 4.5 Thevenin's Theorem (2)




### • RTH

- Case 1: **independent** sources are **turned off**.

- Case 2: **dependent sources**.

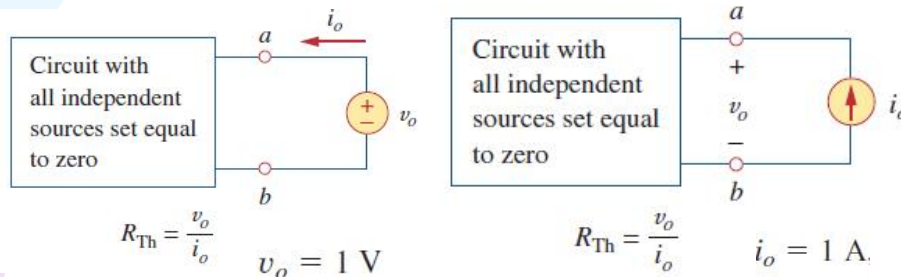we turn off all independent sources. As with superposition, dependent sources are not to be turned off because they are controlled by circuit variables.



$$R_{Th} = \frac{v_o}{i_o} \quad v_o = 1 \text{ V}$$


$$R_{Th} = \frac{v_o}{i_o} \quad i_o = 1 \text{ A}$$

## 4.5 Thevenin's Theorem (3)


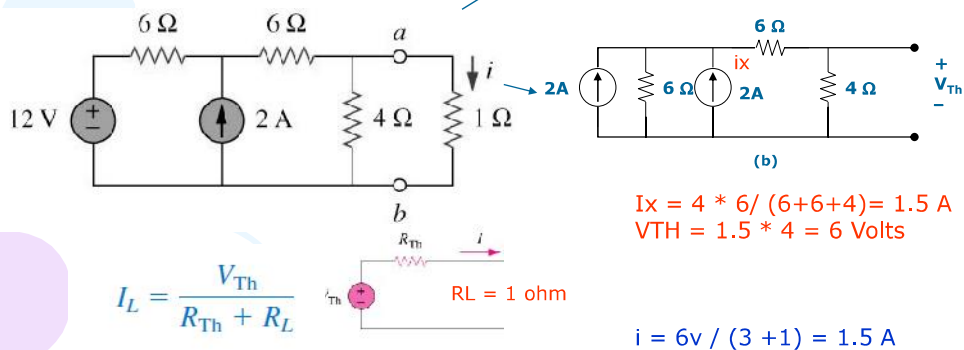
### Example 5

Using Thevenin's theorem, find the equivalent circuit to the left of the terminals in the circuit shown below. Hence find  $i$ .



$$R_{th} = 12/4 = 3 \text{ ohms}$$

(a)

(b)

$$I_x = 4 * 6 / (6+6+4) = 1.5 \text{ A}$$

$$V_{TH} = 1.5 * 4 = 6 \text{ Volts}$$

$$i = 6 \text{ V} / (3 + 1) = 1.5 \text{ A}$$


\*Refer to in-class illustration, textbook, answer  $V_{TH} = 6\text{V}$ ,  $R_{TH} = 3\Omega$ ,  $i = 1.5\text{A}$

## 4.5 Thevenin's Theorem (4)


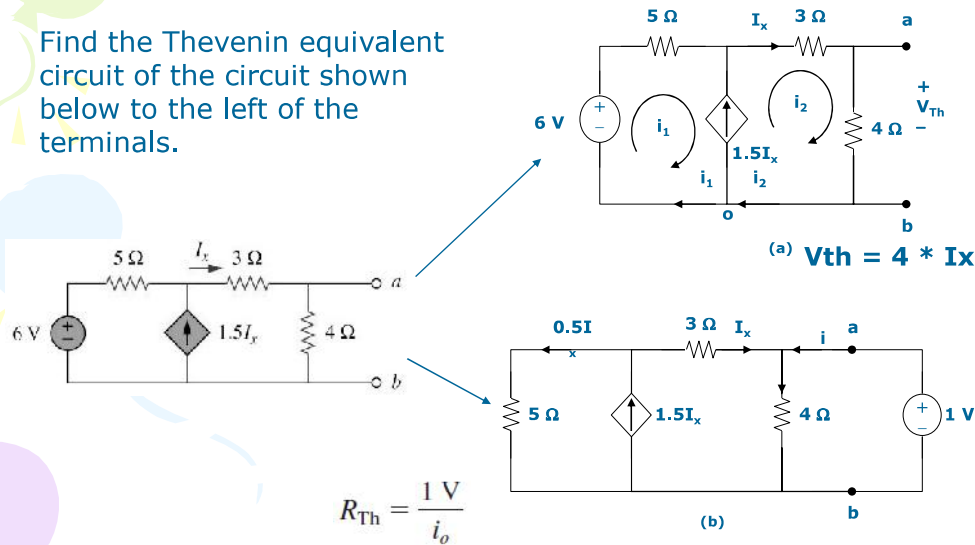
### Example 6

Find the Thevenin equivalent circuit of the circuit shown below to the left of the terminals.



\*Refer to in-class illustration, textbook, answer  $V_{TH} = 5.33\text{V}$ ,  $R_{TH} = 3\Omega$


## 4.6 Norton's Theorem (1)



It states that a linear two-terminal circuit can be replaced by an equivalent circuit of a current source  $I_N$  in parallel with a resistor  $R_N$ ,

Where

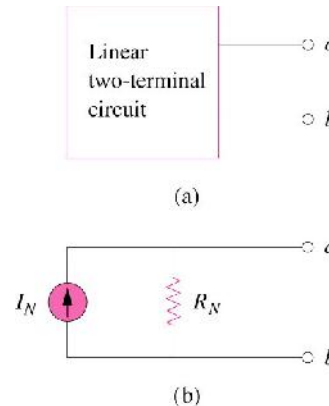- $I_N$  is the short circuit current through the terminals.
- $R_N$  is the input or equivalent resistance at the terminals when the independent sources are turned off.




**The Thevenin's and Norton equivalent circuits are related by a source transformation.**
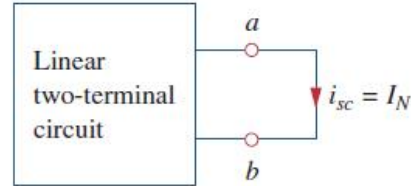
## 4.6 Norton's Theorem (2)



- $I_N$  is the short circuit current through the terminals.




- $R_N$  is the input or equivalent resistance at the terminals when the independent sources are turned off.  
(estimation like Rth (two cases))

$$R_N = R_{Th}$$
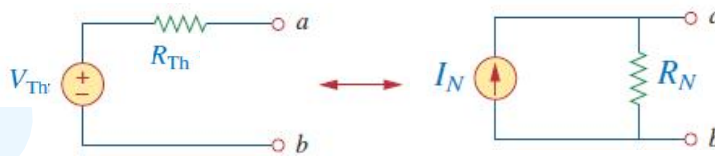
## 4.6 Norton's Theorem (3)



The Thevenin's and Norton equivalent circuits are related by a source transformation.



$$R_N = R_{Th}$$

$$V_{Th} = v_{oc}$$

$$I_N = i_{sc}$$

$$I_N = \frac{V_{Th}}{R_{Th}}$$


$$R_{Th} = \frac{v_{oc}}{i_{sc}} = R_N$$

## 4.6 Norton's Theorem (4)


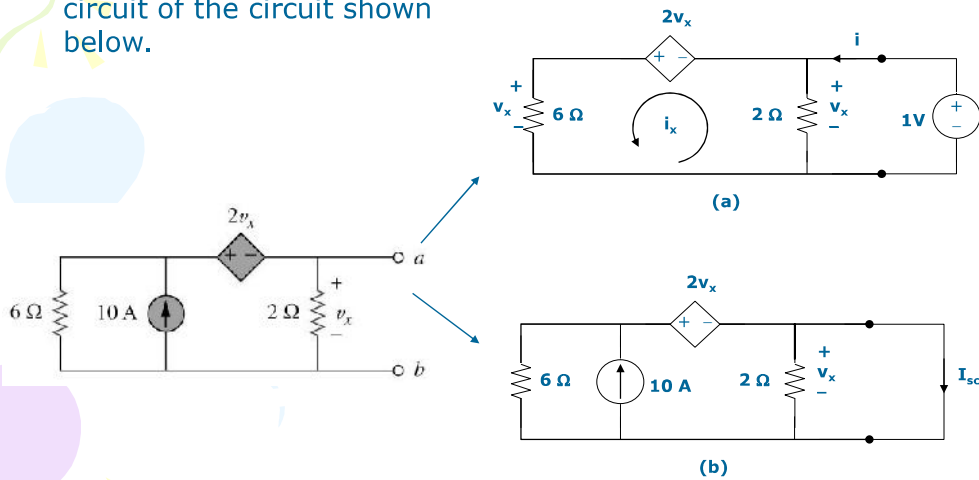
### Example 7

Find the Norton equivalent circuit of the circuit shown below.



\*Refer to in-class illustration, textbook,  $R_N = 1\Omega$ ,  $I_N = 10A$ .

## 4.7 Maximum Power Transfer (1)





If the entire circuit is replaced by its **Thevenin equivalent** except for the load, the power delivered to the load is:

$$P = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

For maximum power dissipated in  $R_L$ ,  $P_{max}$ , for a given  $R_{TH}$ , and  $V_{TH}$ ,
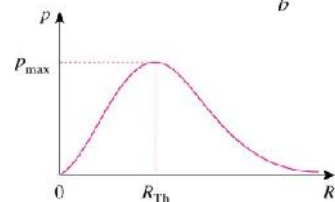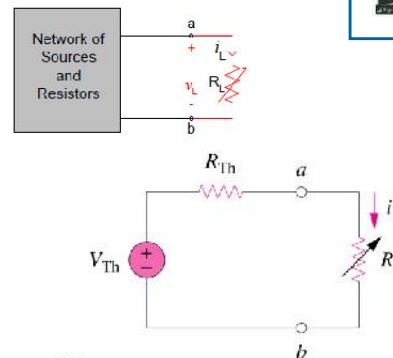
$$R_L = R_{TH} \Rightarrow P_{max} = \frac{V_{Th}^2}{4R_L}$$




The power transfer profile with different  $R_L$
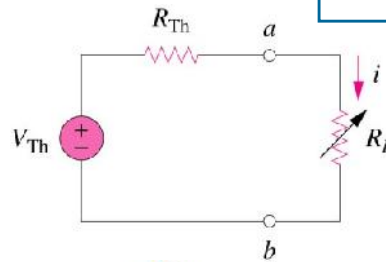
## 4.7 Maximum Power Transfer (1)



Power absorbed by load resistor:

$$P_L = i^2 R_L = \left( \frac{V_{Th}}{R_L + R_{Th}} \right)^2 R_L$$




To find the value of  $R_L$  for which  $P_L$  is maximum, set  $\frac{dP_L}{dR_L} = 0$

$$\frac{dP_L}{dR_L} = V_{Th}^2 \left[ \frac{(R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L)}{(R_{Th} + R_L)^4} \right] = 0$$

$$\Rightarrow (R_{Th} + R_L)^2 = 2R_L(R_{Th} + R_L)$$

$$\Rightarrow \boxed{R_{Th} = R_L}$$

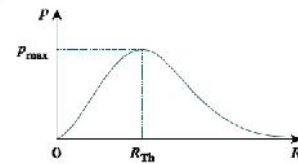

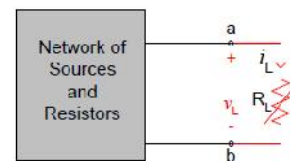
## 4.7 Maximum Power Transfer (1)




The maximum power transferred to the load

$$P_{max} = P_L(R_L = R_{Th}) = \frac{V_{Th}^2}{4R_{Th}}$$



The efficiency of power transfer
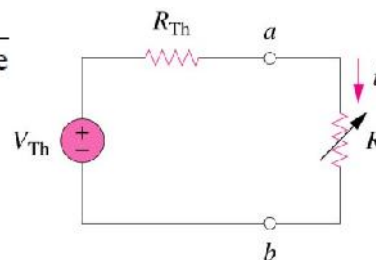
$$\eta = \frac{P_L}{P_s} = \frac{\text{power delivered to the load}}{\text{power generated by the source}}$$





## 4.7 Maximum Power Transfer (2)


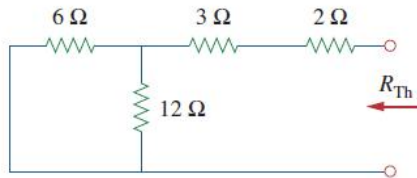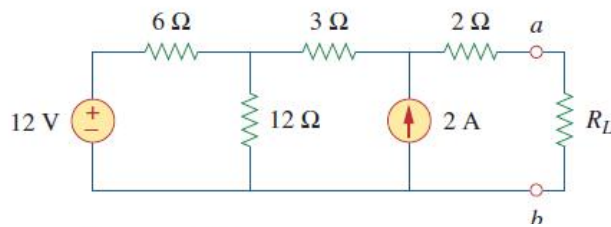
### Example 8

Determine the value of  $R_L$  that will draw the maximum power. Calculate the maximum power.




$$R_{Th} = 2 + 3 + 6 \parallel 12 = 5 + \frac{6 \times 12}{18} = 9 \Omega$$
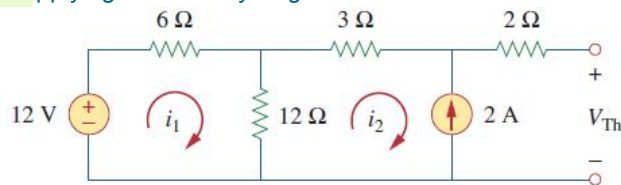
## 4.7 Maximum Power Transfer (2)



**V<sub>th</sub>** : Applying mesh analysis gives



$$-12 + 18i_1 - 12i_2 = 0, \quad i_2 = -2 \text{ A} \quad i_1 = -2/3.$$

Applying KVL around the outer loop to get **V<sub>th</sub>**

$$-12 + 6i_1 + 3i_2 + 2(0) + V_{Th} = 0 \quad V_{Th} = 22 \text{ V}$$

For maximum power transfer,

$$R_L = R_{Th} = 9 \Omega$$

the maximum power is


$$p_{\max} = \frac{V_{Th}^2}{4R_L} = \frac{22^2}{4 \times 9} = 13.44 \text{ W}$$

## 4.7 Maximum Power Transfer (2)


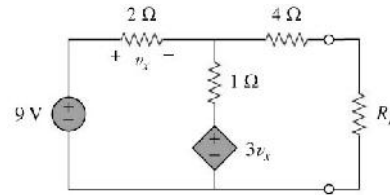
### Example 8

Determine the value of  $R_L$  that will draw the maximum power from the rest of the circuit shown below. Calculate the maximum power.



(a)

(b)

Fig. a  
=> To determine  $R_{TH}$

Fig. b  
=> To determine  $V_{TH}$

$$P_{max} = \frac{V_{Th}^2}{4R_L}$$

\*Refer to in-class illustration, textbook,  $R_L = 4.22\Omega$ ,  $P_m = 2.901W$



## Chapter 5



# Operational Amplifier
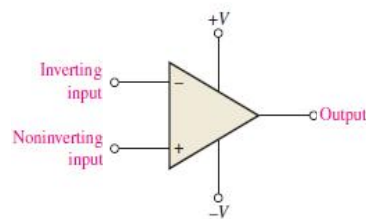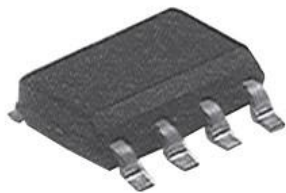
## Introduction



The op amp is an electronic unit that behaves like a **voltage-controlled voltage source**.

An op amp may also be regarded as a voltage amplifier with very high gain.





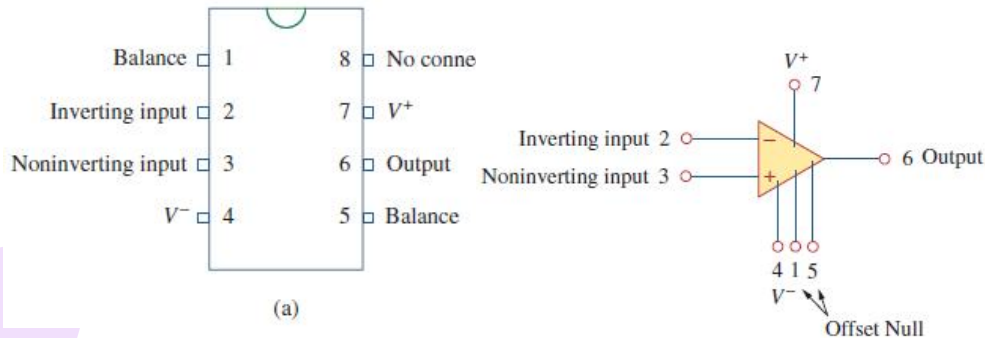
## Operational Amplifiers



An **op amp** is an active circuit element designed to perform mathematical operations of addition, subtraction, multiplication, division, differentiation, and integration.


The pin diagram corresponds to the 741 general purpose op amp made by Fairchild Semiconductor.



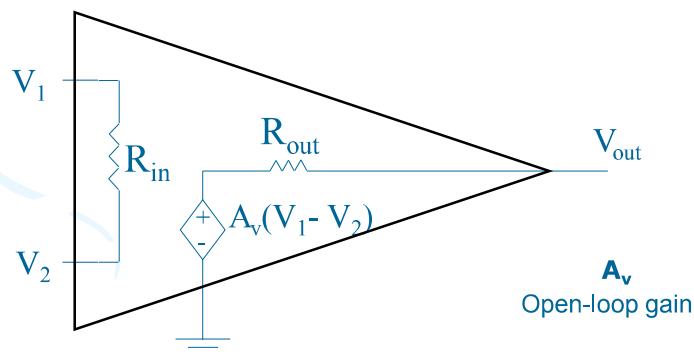
## Operational Amplifier Model



- An operational amplifier circuit is designed so that
  - $V_{out} = A_v (V_1 - V_2)$  ( $A_v$  is a very large gain)
  - Input resistance ( $R_{in}$ ) is very large
  - Output resistance ( $R_{out}$ ) is very low



## Practical Operational Amplifiers

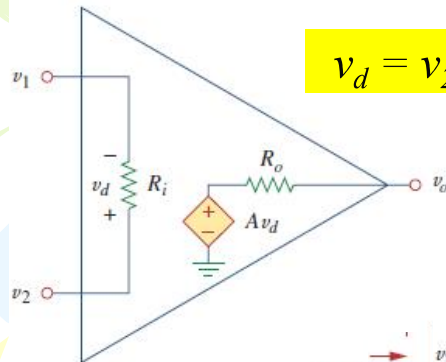


$$v_d = v_2 - v_1; \quad v_o = Av_d = A(v_2 - v_1)$$

$$v_o = Av_d = A(v_2 - v_1)$$

The equivalent circuit of the non-ideal op amp

$$v_d = v_2 - v_1$$

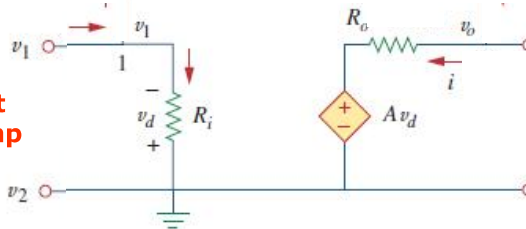

## Operational Amplifiers




Op amp output voltage  $v_o$  as a function of the differential input voltage  $v_d$ .

A practical limitation of the op amp is that the magnitude of its output voltage cannot exceed  $|V_{CC}|$ .

$$-V_{CC} \leq v_o \leq V_{CC}$$

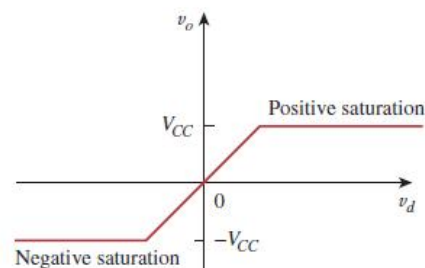the op amp can operate in three modes, depending on the differential input voltage  $v_d$ .



Op Amp output:  $v_o$  as a function of  $V_d$

1. Positive saturation,  $v_o = V_{CC}$ .
2. Linear region,  $-V_{CC} \leq v_o = Av_d \leq V_{CC}$ .
3. Negative saturation,  $v_o = -V_{CC}$ .


## Saturation




- $V_{OUT}$  cannot exceed the supply voltages.

$$-V_{CC} \leq v_o \leq V_{CC}$$

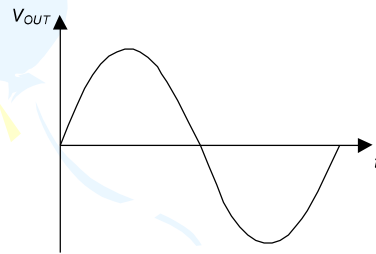- In fact, typically  $V_{OUT}$  can only get to within about 1.5 V of the supplies.



Desired Output Waveform

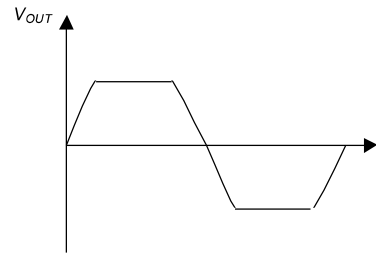



Actual Output Waveform
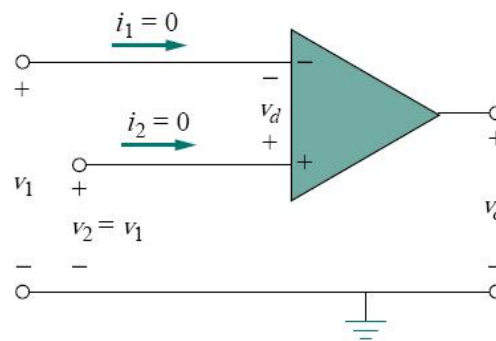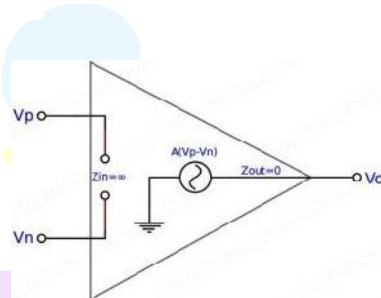
## Ideal Operational Amplifiers



An ideal op amp has the following characteristics:

- Infinite open-loop voltage gain,  $A_V \approx \infty$ .
- Infinite input resistance,  $R_i \approx \infty$ .
- Zero output resistance,  $R_o \approx 0$ .
- The output voltage  $V_o = 0$ ; when  $V_d = V_2 - V_1 = 0$



## Ideal Operational Amplifiers



An **ideal op amp** is an amplifier with infinite open-loop gain, infinite input resistance, and zero output resistance.

$$R_{in} \rightarrow \infty$$

$$A \rightarrow \infty$$

Two important characteristics of the ideal op amp are:


1. The currents into both input terminals are zero:

$$i_1 = 0, \quad i_2 = 0$$

2. The voltage across the input terminals is equal to zero; i.e.,

$$v_d = v_2 - v_1 = 0$$

$$v_1 = v_2$$

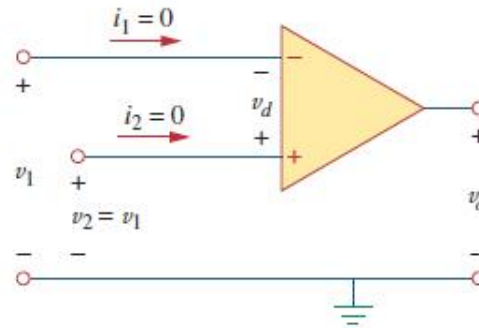

## Practical and Ideal Op-Amp Data



Typical ranges for op amp parameters

Parameter	Typical range	Ideal values
Open-loop gain, A	$10^5$ to $10^8 \Omega$	$\infty$
Input resistance, $R_i$	$10^5$ to $10^{13} \Omega$	$\infty \Omega$
Output resistance, $R_o$	10 to 100 $\Omega$	0 $\Omega$
Supply voltage, $V_{CC}$	5 to 24 V	

## Practical Op-Amp Circuits



These Op-amp circuits are commonly used:

### 1- Linear Applications:

- Inverting Amplifier
- Noninverting Amplifier
- Unity Follower
- Summing Amplifier (Adder)
- Difference Amplifier (Subtractor)
- Integrator
- Differentiator
- Active Filters.

**Digital-to Analog Converter (DAC)**

## Practical Op-Amp Circuits



These Op-amp circuits are commonly used:

### 2- Nonlinear Applications:

- Logarithmic Amplifiers.
- Exponential Amplifiers.
- Analog Multipliers and Divisions.
- Comparators.
- Precision Rectifiers.
- Waveform Generators.

## Inverting Amplifier




Assuming an ideal op amp,

Applying KCL at node 1

$$i_1 = i_2 \Rightarrow \frac{v_i - v_1}{R_1} = \frac{v_1 - v_o}{R_f}$$

$$v_1 = v_2 \quad v_1 = v_2 = 0$$

$$\frac{v_i}{R_1} = -\frac{v_o}{R_f}$$

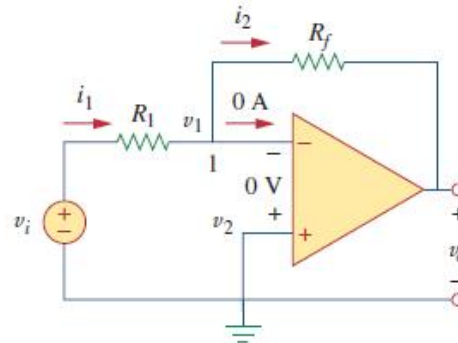

The voltage gain is  $A_v = v_o/v_i = -R_f/R_1$ .

$$v_o = -\frac{R_f}{R_1}v_i$$

An inverting amplifier reverses the polarity of the input signal while amplifying it.


## Inverting Amplifier



Refer to the op amp in Fig. If  $v_i = 0.5$  V, calculate: (a) the output voltage  $v_o$ , and (b) the current in the 10-k $\Omega$  resistor.

$$\frac{v_o}{v_i} = -\frac{R_f}{R_1} = -\frac{25}{10} = -2.5$$
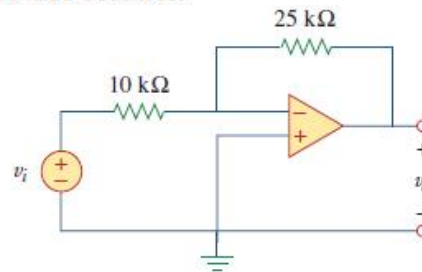
$$v_o = -2.5v_i = -2.5(0.5) = -1.25 \text{ V}$$




(b) The current through the 10-k $\Omega$  resistor is

$$i = \frac{v_i - 0}{R_1} = \frac{0.5 - 0}{10 \times 10^3} = 50 \mu\text{A}$$

## Operational Amplifiers



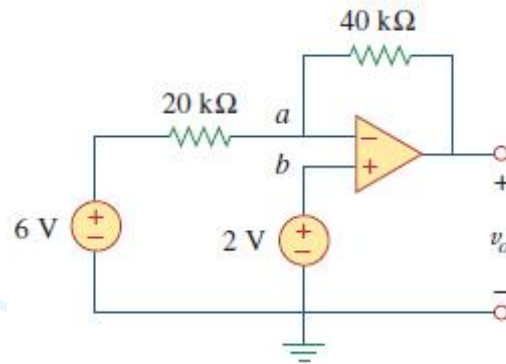**TASK** Determine  $v_o$  in the op amp circuit shown in



## Noninverting Amplifier




Assuming an ideal op amp,

$$i_1 = i_2 \Rightarrow \frac{0 - v_1}{R_1} = \frac{v_1 - v_o}{R_f}$$

$$v_1 = v_2 = v_i$$

$$\frac{-v_i}{R_1} = \frac{v_i - v_o}{R_f}$$
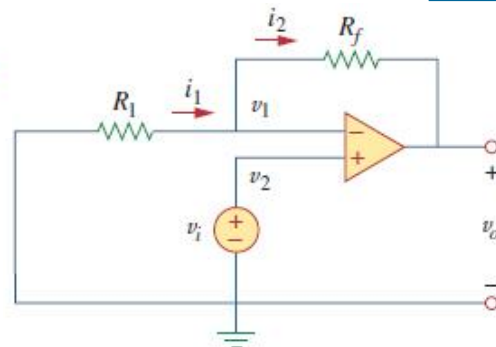
$$v_o = \left(1 + \frac{R_f}{R_1}\right)v_i$$



A noninverting amplifier is an op amp circuit designed to provide a positive voltage gain.

The voltage gain is

$$A_v = v_o/v_i = 1 + R_f/R_1,$$

## Noninverting Amplifier



For the op amp circuit in Fig., calculate the output voltage  $v_o$ .

**METHOD 1** Using superposition,


■ **METHOD 2** Applying KCL at node  $a$ ,

$$\frac{6 - v_a}{4} = \frac{v_a - v_o}{10}$$

But  $v_a = v_b = 4$ , and so

$$\frac{6 - 4}{4} = \frac{4 - v_o}{10} \quad \Rightarrow \quad 5 = 4 - v_o$$


$$v_o = -1 \text{ V,}$$

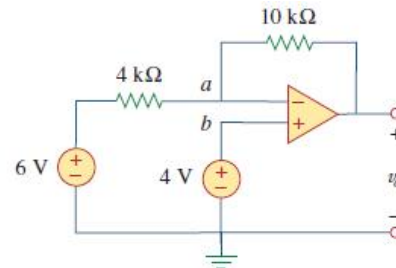

## Noninverting Amplifier



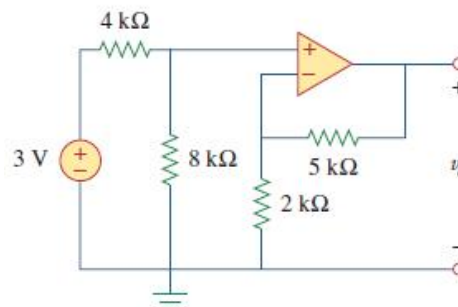**TASK** For the op amp circuit in Fig., calculate the output voltage  $v_o$ .






## The voltage follower



called a *voltage follower* (or *unity gain amplifier*) because the output follows the input

### Unity Follower

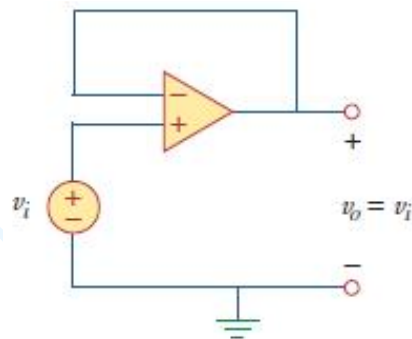


$$v_o = v_i$$

## The voltage follower



A voltage follower used to isolate two cascaded stages of a circuit.

$$(R_f = 0 \text{ and } R_i = \infty),$$

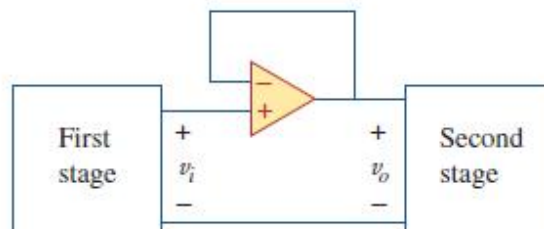

Such a circuit has a very high input impedance and is therefore useful as an intermediate-stage (or buffer) amplifier to isolate one circuit from another,

## Summing Amplifier




Summing Amplifier is an op amp circuit that combines several inputs and produces an output that is the weighted sum of the inputs.

$$i = i_1 + i_2 + i_3 \quad v_a = 0$$

$$i_1 = \frac{v_1 - v_a}{R_1}, \quad i_2 = \frac{v_2 - v_a}{R_2}$$
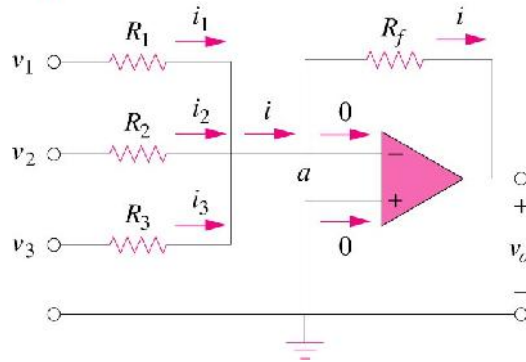
$$i_3 = \frac{v_3 - v_a}{R_3}, \quad i = \frac{v_a - v_o}{R_f}$$



$$v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3\right)$$


## Summing Amplifier



Calculate  $v_o$  and  $i_o$  in the op amp circuit shown below.

$$v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3\right)$$
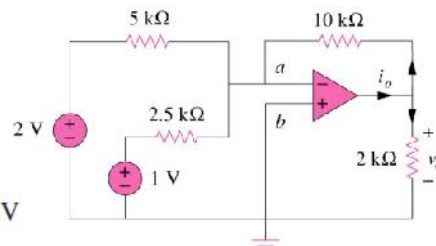
$$v_o = -\left[\frac{10}{5}(2) + \frac{10}{2.5}(1)\right] = -(4 + 4) = -8 \text{ V}$$



- ▶ The current  $i_o$  is the sum of the currents through the 10-k $\Omega$  and 2-k $\Omega$  resistors. Both of these resistors have voltage  $v_o = -8 \text{ V}$  across them, since  $v_a = v_b = 0$ . Hence,

$$i_o = \frac{v_o - 0}{10} + \frac{v_o - 0}{2} \text{ mA} = -0.8 - 4 = -4.8 \text{ mA}$$

## Difference Amplifier




A difference amplifier is a device that amplifies the difference between two inputs but rejects any signals common to the two inputs.

Applying KCL to node  $a$ ,

$$\frac{v_1 - v_a}{R_1} = \frac{v_a - v_o}{R_2}$$
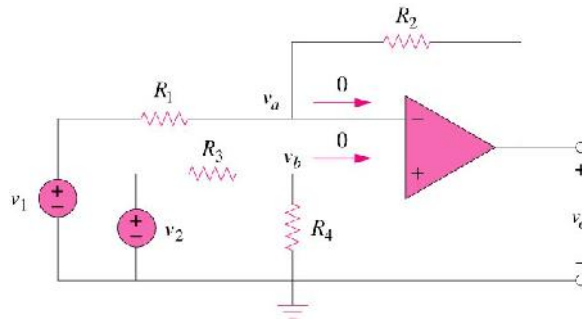
$$v_o = \left( \frac{R_2}{R_1} + 1 \right) v_a - \frac{R_2}{R_1} v_1$$



Applying KCL to node  $b$ ,

$$\frac{v_2 - v_b}{R_3} = \frac{v_b - 0}{R_4}$$

$$v_b = \frac{R_4}{R_3 + R_4} v_2 \quad \text{But } v_a = v_b.$$

## Difference Amplifier



$$v_o = \left( \frac{R_2}{R_1} + 1 \right) \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} v_1$$

$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1$$

$$v_o = \frac{R_2}{R_1} (v_2 - v_1) \quad \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

If  $R_2 = R_1$  and  $R_3 = R_4$ ,

$$v_o = v_2 - v_1$$


$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1 \Rightarrow v_o = v_2 - v_1, \text{ if } \frac{R_2}{R_1} = \frac{R_3}{R_4} = 1$$
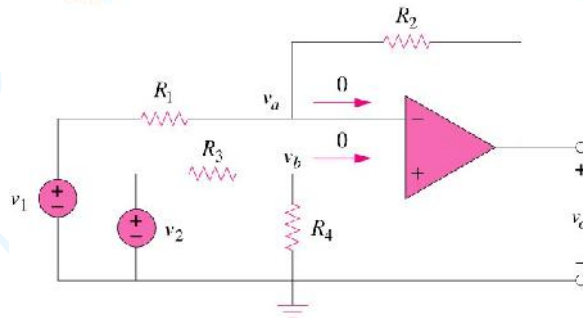
## Difference Amplifier



Design a difference amplifier with gain 7.5.

$$v_o = \frac{R_2}{R_1}(v_2 - v_1) \quad \frac{R_1}{R_2} = \frac{R_3}{R_4}$$



**Answer:** Typical:  $R_1 = R_3 = 20\text{k}\Omega$ ,  $R_2 = R_4 = 150\text{ k}\Omega$ .

## Design Amplifier



Design an op amp circuit with inputs  $v_1$  and  $v_2$  such that

$$v_o = -5v_1 + 3v_2.$$

### Design 1


The circuit requires that

difference amplifier

$$v_o = 3v_2 - 5v_1$$

Comparing

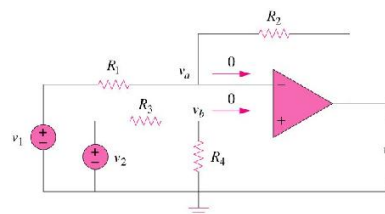
$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)}v_2 - \frac{R_2}{R_1}v_1$$


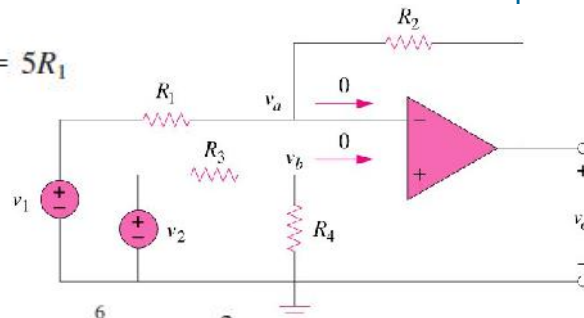
## Difference Amplifier



$$\frac{R_2}{R_1} = 5 \Rightarrow R_2 = 5R_1$$



$$5 \frac{(1 + R_1/R_2)}{(1 + R_3/R_4)} = 3 \Rightarrow \frac{\frac{6}{5}}{1 + R_3/R_4} = \frac{3}{5}$$

$$2 = 1 + \frac{R_3}{R_4} \Rightarrow R_3 = R_4$$

If we choose  $R_1 = 10 \text{ k}\Omega$  and  $R_3 = 20 \text{ k}\Omega$ , then  $R_2 = 50 \text{ k}\Omega$  and  $R_4 = 20 \text{ k}\Omega$ .

## Difference Amplifier



### Design 2


$$v_o = 3v_2 - 5v_1$$

If we desire to use more than one op amp, we may cascade an inverting amplifier and a two-input inverting summer, as shown in Fig.

For the summer,

$$v_o = -v_a - 5v_1 \quad v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3\right)$$

$$v_a = -3v_2$$

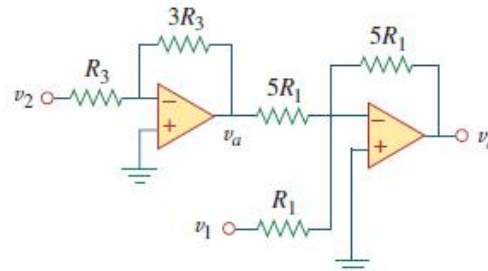

which is the desired result. In Fig. 5.25, we may select  $R_1 = 10 \text{ k}\Omega$  and  $R_3 = 20 \text{ k}\Omega$  or  $R_1 = R_3 = 10 \text{ k}\Omega$ .



# Chapter 6

## Capacitors and Inductors



## Capacitors and Inductors-Chapter 6



- 6.1** Introduction.
- 6.2** Capacitors.
- 6.3** Series and Parallel Capacitors.
- 6.4** Inductors.
- 6.5** Series and Parallel Inductors.

## 6.1 Introduction




*In contrast to a resistor, which spends or dissipates energy irreversibly, an inductor or capacitor stores or releases energy (i.e., has a memory).*

**For this reason, capacitors and inductors are called storage elements.**
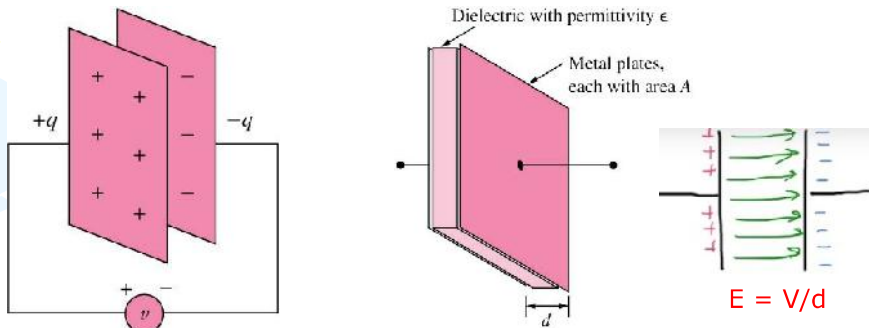
## 6.2 Capacitors (1)



- A capacitor is a passive element designed to **store energy** in its **electric field**.




- A **capacitor** consists of two conducting plates separated by an insulator (or dielectric).
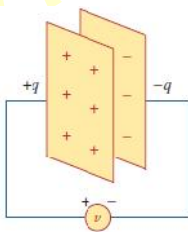
## 6.2 Capacitors (2)



- **Capacitance**  $C$  is the ratio of the charge  $q$  on one plate of a capacitor to the voltage difference  $v$  between the two plates, measured in farads (F).



$$q = C v \quad \text{and} \quad C = \frac{\epsilon A}{d}$$


1 farad = 1 coulomb/volt.

- Where  $\epsilon$  is the permittivity of the dielectric material between the plates,  $A$  is the surface area of each plate,  $d$  is the distance between the plates.
- Unit: F, pF ( $10^{-12}$ ), nF ( $10^{-9}$ ), and  $\mu\text{F}$  ( $10^{-6}$ )
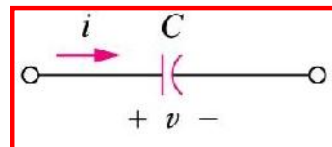
## 6.2 Capacitors (3)



- If  $i$  is flowing into the +ve terminal of  $C$ 
  - Charging  $\Rightarrow i$  is +ve
  - Discharging  $\Rightarrow i$  is -ve



- The current-voltage relationship of capacitor according to above convention is

$$i = C \frac{d v}{d t} \quad \text{and} \quad v = \frac{1}{C} \int_{t_0}^t i d t + v(t_0)$$

$$q = C v \quad \frac{dq}{dt} = C \frac{dv}{dt}$$



## 6.2 Capacitors (4)



The instantaneous power delivered to the capacitor is

$$p = vi = Cv \frac{dv}{dt}$$

The energy stored in the capacitor is


$$w = \int_{-\infty}^t p(\tau) d\tau = C \int_{-\infty}^t v \frac{dv}{d\tau} d\tau = C \int_{v(-\infty)}^{v(t)} v dv = \frac{1}{2} Cv^2 \Big|_{v(-\infty)}^{v(t)}$$

## 6.2 Capacitors (5)



- The energy,  $w$ , stored in the capacitor is

$$w = \frac{1}{2} C v^2$$

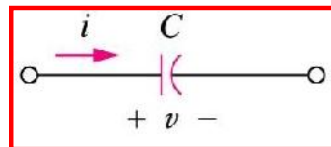


$$p = vi = Cv \frac{dv}{dt}$$


$$w = \int_{-\infty}^t p(\tau) d\tau = C \int_{-\infty}^t v \frac{dv}{d\tau} d\tau = C \int_{v(-\infty)}^{v(t)} v dv = \frac{1}{2} Cv^2 \Big|_{v(-\infty)}^{v(t)}$$

- A capacitor is
  - an **open circuit** to dc ( $dv/dt = 0$ ).
  - its voltage **cannot change abruptly**.

## 6.2 Capacitors (6)

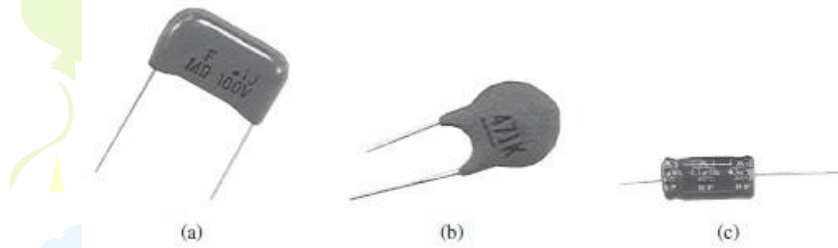

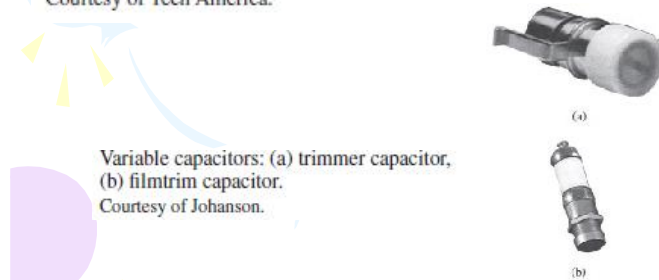Fixed capacitors: (a) polyester capacitor, (b) ceramic capacitor, (c) electrolytic capacitor.  
Courtesy of Tech America.




Variable capacitors: (a) trimmer capacitor,  
(b) filmtrim capacitor.  
Courtesy of Johanson.
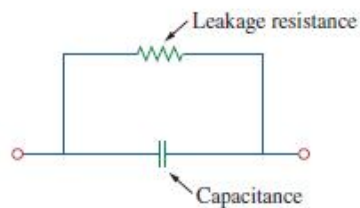
## 6.2 Capacitors (7)



The ideal capacitor does not dissipate energy. It takes power from the circuit when storing energy in its field and returns previously stored energy when delivering power to the circuit.

A real, nonideal capacitor has a parallel-model leakage resistance



Circuit model of a nonideal capacitor.


## 6.2 Capacitors (8)


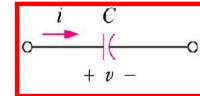
### Example 1

The current through a 100- $\mu\text{F}$  capacitor is

$$i(t) = 50 \sin(120 \pi t) \text{ mA.}$$



Calculate the voltage across it at  $t = 1 \text{ ms}$  and  $t = 5 \text{ ms}$ .

Take  $v(0) = 0$ .

$$v = \frac{1}{C} \int_0^t i dt + v(0) \text{ and } v(0) = 0,$$

**Answer:**

$$v(1\text{ms}) = 93.14\text{mV}$$

$$v(5\text{ms}) = 1.7361\text{V}$$

## 6.2 Capacitors (9)



$$\begin{aligned}
 i(t) &= 50 \sin(120\pi t) \text{ mA} \\
 v &= \frac{1}{C} \int_0^t i dt = \frac{1}{C} \int_0^{1\text{ms}} 50 \sin(120\pi t) dt \\
 &= \frac{50 \times 10^{-3}}{C} \frac{1}{120\pi} \left[ -\cos(120\pi t) \right]_0^{1\text{ms}} \\
 &= \frac{50 \times 10^{-3}}{120\pi C} \left[ +\cos(0) - \cos(120\pi \times 1 \times 10^{-3}) \right] \\
 &= \frac{50 \times 10^{-3}}{120 \times 3.14 \times 100 \times 10^{-6}} \left[ 1 - \cos(21.6^\circ) \right] \\
 &= \frac{50 \times 10^{-3} \times 0.07022}{120 \times 3.14 \times 100 \times 10^{-6}} = 0.09318 \text{ V} \\
 &= 93.18 \text{ mV}
 \end{aligned}$$

**Answer:**

$$v(1\text{ms}) = 93.14\text{mV}$$

$$v(5\text{ms}) = 1.7361\text{V}$$

## 6.2 Capacitors (11)




### Example 2

An initially uncharged 1-mF capacitor has the current shown below across it.

Calculate the voltage across it at  $t = 2$  ms and  $t = 5$  ms.

$$\frac{y - y_1}{x - x_1} = \frac{y_2 - y_1}{x_2 - x_1}$$

$$y - y_1 = m(x - x_1)$$

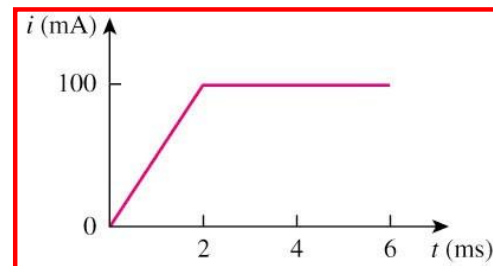

**Answer:**

$$v(2\text{ms}) = 100 \text{ mV}$$

$$v(5\text{ms}) = 500 \text{ mV}$$

## 6.2 Capacitors (12)



### Example 2

$$x \rightarrow t$$

$$y \rightarrow i$$

$$i = 50 t$$


$$\frac{y - y_1}{x - x_1} = \frac{y_2 - y_1}{x_2 - x_1}$$

$$y - y_1 = m(x - x_1)$$

$$v = \frac{1}{C} \int_0^t i dt$$

$$V = \frac{50}{1\text{mF}} \left. \frac{t^2}{2} \right|_0^2$$
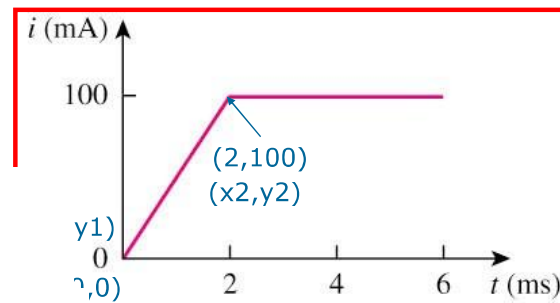
$$V = \frac{50 \cdot 10^{-6} \cdot 4/2}{1 \cdot 10^{-3}} = 100 \text{ mV}$$



**Answer:**


$$v(2\text{ms}) = 100 \text{ mV}$$

$$v(5\text{ms}) = 500 \text{ mV}$$
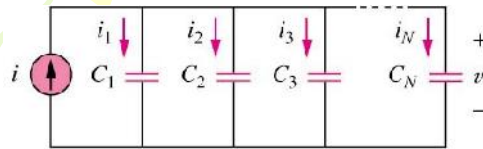
## 6.3 Series and Parallel Capacitors (1)



- The equivalent capacitance of  $N$  **parallel-connected** capacitors is the sum of the individual capacitances.




(a)

$$i = i_1 + i_2 + i_3 + \dots + i_N$$

But  $i_k = C_k dv/dt$ . Hence,

$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt}$$
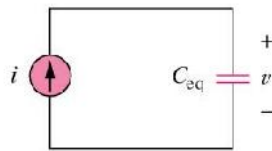
$$= \left( \sum_{k=1}^N C_k \right) \frac{dv}{dt} = C_{eq} \frac{dv}{dt}$$




(b)

$$C_{eq} = C_1 + C_2 + \dots + C_N$$
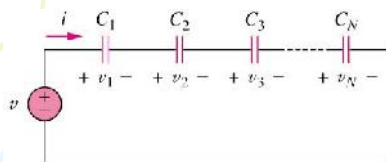
## 6.3 Series and Parallel Capacitors (2)



- The equivalent capacitance of  $N$  **series-connected** capacitors is the reciprocal of the sum of the reciprocals of the individual capacitances.



(a)

$$v = v_1 + v_2 + v_3 + \dots + v_N$$

But  $v_k = \frac{1}{C_k} \int_{t_0}^t i(\tau) d\tau + v_k(t_0)$ . Therefore,


$$v = \frac{1}{C_1} \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i(\tau) d\tau + v_2(t_0)$$

$$+ \dots + \frac{1}{C_N} \int_{t_0}^t i(\tau) d\tau + v_N(t_0)$$

$$= \left( \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + v_2(t_0)$$

$$+ \dots + v_N(t_0)$$
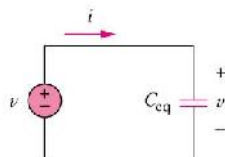
$$= \frac{1}{C_{eq}} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$



(b)


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

### 6.3 Series and Parallel Capacitors (3)



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

#### Example 6.6

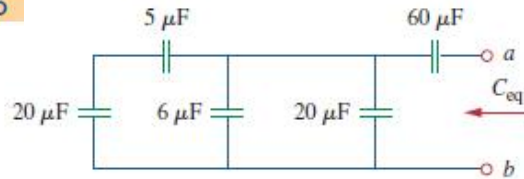

$$\frac{20 \times 5}{20 + 5} = 4 \mu\text{F}$$

$$4 + 6 + 20 = 30 \mu\text{F}$$


$$C_{eq} = \frac{30 \times 60}{30 + 60} = 20 \mu\text{F}$$

### 6.3 Series and Parallel Capacitors (4)


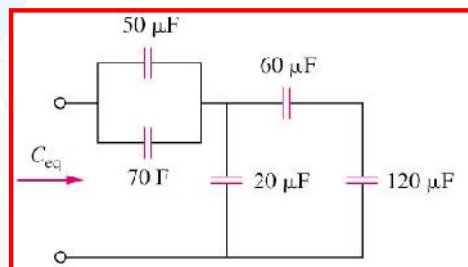
#### Example 3

Find the equivalent capacitance seen at the terminals of the circuit in the circuit shown below:



**Answer:**

$$C_{eq} = 40 \mu\text{F}$$

## 6.3 Series and Parallel Capacitors (5)





### Example 4

Find the voltage across each of the capacitors in the circuit shown below:

$$C_{\text{eq}} = \frac{1}{\frac{1}{60} + \frac{1}{30} + \frac{1}{20}} \text{ mF} = 10 \text{ mF}$$

The total charge is
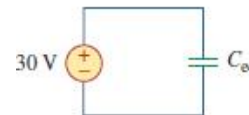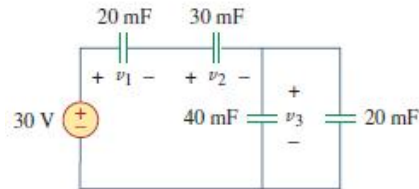
$$q = C_{\text{eq}}v = 10 \times 10^{-3} \times 30 = 0.3 \text{ C}$$




This is the charge on the 20-mF and 30-mF capacitors, because they are in series with the 30-V source. (A crude way to see this is to imagine that charge acts like current, since  $i = dq/dt$ .) Therefore,
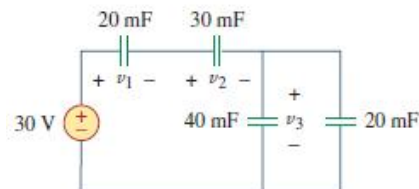
## 6.3 Series and Parallel Capacitors (6)



$$v_1 = \frac{q}{C_1} = \frac{0.3}{20 \times 10^{-3}} = 15 \text{ V}$$

$$v_2 = \frac{q}{C_2} = \frac{0.3}{30 \times 10^{-3}} = 10 \text{ V}$$



Having determined  $v_1$  and  $v_2$ , we now use KVL to determine  $v_3$  by

$$v_3 = 30 - v_1 - v_2 = 5 \text{ V}$$

Alternatively, since the 40-mF and 20-mF capacitors are in parallel, they have the same voltage  $v_3$  and their combined capacitance is  $40 + 20 = 60 \text{ mF}$ . This combined capacitance is in series with the 20-mF and 30-mF capacitors and consequently has the same charge on it. Hence,


$$v_3 = \frac{q}{60 \text{ mF}} = \frac{0.3}{60 \times 10^{-3}} = 5 \text{ V}$$

## 6.3 Series and Parallel Capacitors (7)


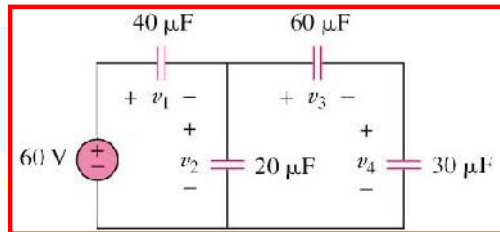
### Example 4

Find the voltage across each of the capacitors in the circuit shown below:



**Answer:**

$$v_1 = 30V$$

$$v_2 = 30V$$



$$v_3 = 10V$$

$$v_4 = 20V$$
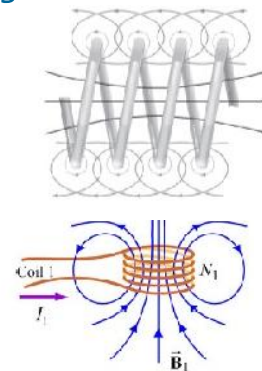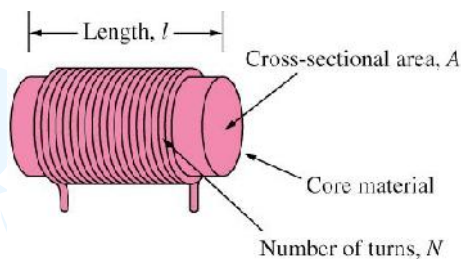
## 6.4 Inductors (1)



- An inductor is a passive element designed to store energy in its magnetic field.



- An inductor consists of a coil of conducting wire.



## 6.4 Inductors (2)



Inductors may be fixed or variable.

The core may be made of iron, steel, plastic, or air.

The terms *coil* and *choke* are also used for inductors.

Various types of inductors: (a) solenoidal wound inductor, (b) toroidal inductor, (c) chip inductor.

Courtesy of Tech America.



(a)



(b)



(c)

## 6.4 Inductors (3)




- Inductance is the property whereby an inductor exhibits opposition to the change of current flowing through it, measured in henrys (H).

$$v = L \frac{d i}{d t} \quad \text{and} \quad L = \frac{N^2 \mu A}{l}$$

where  $N$  is the number of turns,  $l$  is the length,  $A$  is the cross-sectional area, and  $\mu$  is the permeability of the core.

- The unit of inductors is Henry (H), mH ( $10^{-3}$ ) and  $\mu\text{H}$  ( $10^{-6}$ ).

## 6.4 Inductors (4)

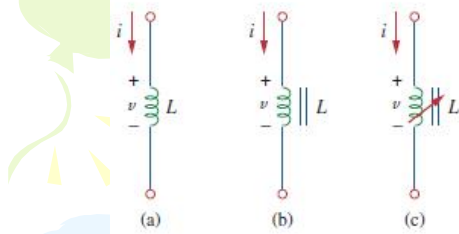

Circuit symbols for inductors: (a) air-core, (b) iron-core, (c) variable iron-core.

$$p = vi = \left( L \frac{di}{dt} \right) i$$

- The energy stored is

$$w = \int_{-\infty}^t p(\tau) d\tau = L \int_{-\infty}^t \frac{di}{d\tau} i d\tau \quad \text{Since } i(-\infty) = 0,$$


$$= L \int_{-\infty}^t i di = \frac{1}{2} Li^2(t) - \frac{1}{2} Li^2(-\infty) \quad w = \frac{1}{2} Li^2$$
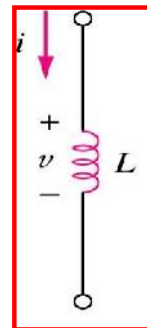
## 6.4 Inductors (5)



- The current-voltage relationship of an inductor:

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$



- The power stored by an inductor:


$$w = \frac{1}{2} L i^2$$

- An inductor acts like a short circuit to dc ( $di/dt = 0$ )
- its current cannot change abruptly.
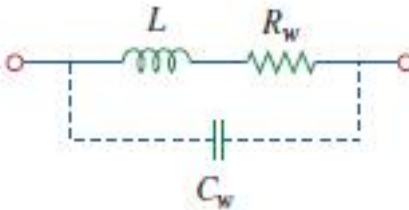
## 6.4 Inductors (6)



Since an inductor is often made of a highly conducting wire, it has a very small resistance.



Circuit model for a practical inductor.

## 6.4 Inductors (7)




### Example 5

The terminal voltage of a 2-H inductor is  $v = 10(1-t)$  V. Find the current flowing through it at  $t = 4$  s and the energy stored in it within  $0 < t < 4$  s.

Assume  $i(0) = 2$  A.

$$\text{Since } i = \frac{1}{L} \int v(t) dt + i(t_0) :$$

$$\begin{aligned} i &= \frac{10}{2} \left[ 4 - \frac{t^2}{2} \Big|_0^4 \right] + 2 \\ &= 5 [4 - 8] + 2 = -20 + 2 \\ i &= -18 \text{ A} \end{aligned}$$

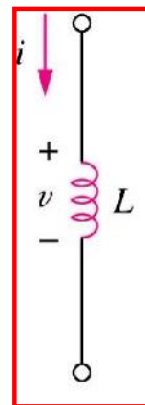

**Answer:**  
 $i(4s) = -18A$   
 $w(4s) = 320J$

## 6.4 Inductors (8)



### Example 6



Determine  $v_C$ ,  $i_L$ , and the energy stored in the capacitor and inductor in the circuit.

- (a) Under dc conditions, we replace the capacitor with an open circuit and the inductor with a short circuit

$$i = i_L = \frac{12}{1 + 5} = 2 \text{ A}$$

The voltage  $v_C$  is the same as the voltage across the 5- $\Omega$  resistor. Hence,

$$v_C = 5i = 10 \text{ V}$$

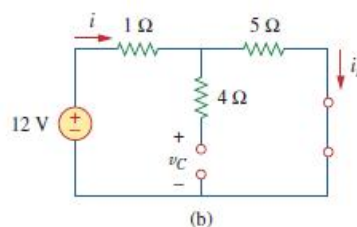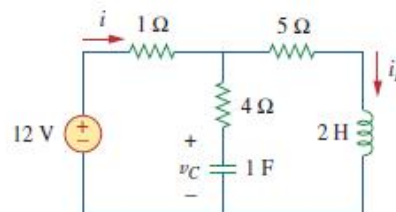

## 6.4 Inductors (9)



The voltage  $v_C$  is the same as the voltage across the 5- $\Omega$  resistor. Hence,


$$v_C = 5i = 10 \text{ V}$$

- (b) The energy in the capacitor is

$$w_C = \frac{1}{2} C v_C^2 = \frac{1}{2} (1)(10^2) = 50 \text{ J}$$

and that in the inductor is
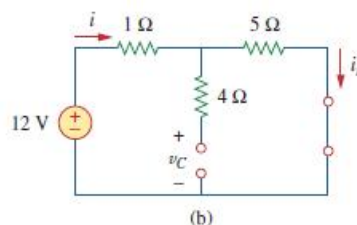
$$w_L = \frac{1}{2} L i_L^2 = \frac{1}{2} (2)(2^2) = 4 \text{ J}$$




## 6.4 Inductors (10)


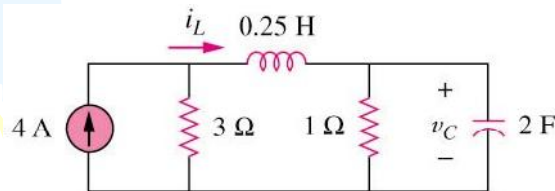
### Example 6

Determine  $v_C$ ,  $i_L$ , and the energy stored in the capacitor and inductor in the circuit of circuit shown below under dc conditions.



**Answer:**

$$i_L = 3A$$

$$v_C = 3V$$

$$w_L = 1.125J$$


$$w_C = 9J$$

31
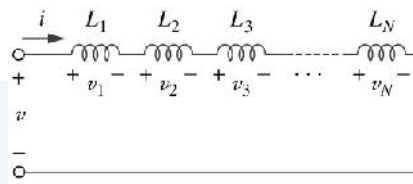
## 6.4 Series and Parallel Inductors (1)



- The equivalent inductance of **series-connected** inductors is the sum of the individual inductances.




(a)

$$v = v_1 + v_2 + v_3 + \dots + v_N$$

$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + \dots + L_N \frac{di}{dt}$$

$$= (L_1 + L_2 + L_3 + \dots + L_N) \frac{di}{dt}$$
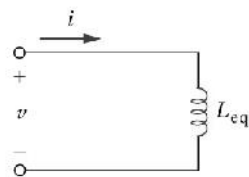
$$= \left( \sum_{k=1}^N L_k \right) \frac{di}{dt} = L_{eq} \frac{di}{dt}$$



(b)



$$L_{eq} = L_1 + L_2 + \dots + L_N$$

32
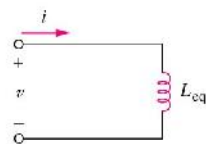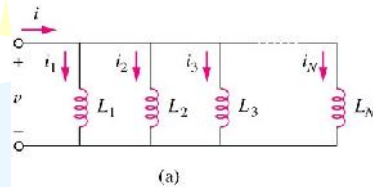
## 6.4 Series and Parallel Inductors (2)



- The equivalent capacitance of **parallel** inductors is the reciprocal of the sum of the reciprocals of the individual inductances.



$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

$$i = i_1 + i_2 + i_3 + \dots + i_N$$

$$\text{But } i_k = \frac{1}{L_k} \int_{t_0}^t v \, dt + i_k(t_0); \text{ hence,}$$

$$\begin{aligned} i &= \frac{1}{L_1} \int_{t_0}^t v \, dt - i_1(t_0) + \frac{1}{L_2} \int_{t_0}^t v \, dt + i_2(t_0) \\ &\quad - \dots + \frac{1}{L_N} \int_{t_0}^t v \, dt + i_N(t_0) \\ &= \left( \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right) \int_{t_0}^t v \, dt + i_1(t_0) + i_2(t_0) \\ &\quad + \dots + i_N(t_0) \\ &= \left( \sum_{k=1}^N \frac{1}{L_k} \right) \int_{t_0}^t v \, dt + \sum_{k=1}^N i_k(t_0) = \frac{1}{L_{eq}} \int_{t_0}^t v \, dt + i(t_0) \end{aligned}$$


33

## 6.4 Series and Parallel Inductors (3)


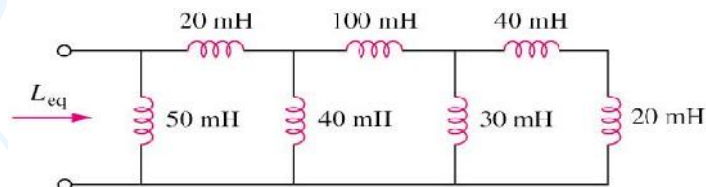
### Example 7

Calculate the equivalent inductance for the inductive ladder network in the circuit shown below:



**Answer:**  
 **$L_{eq} = 25\text{mH}$**


34

## 6.4 Series and Parallel Inductors (4)


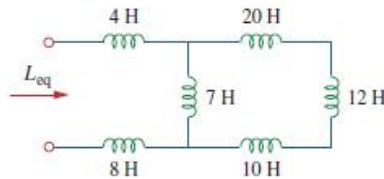
### Example 6.11

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} \quad \text{or} \quad L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$



$$\frac{7 \times 42}{7 + 42} = 6 \text{ H}$$

$$L_{eq} = 4 + 6 + 8 = 18 \text{ H}$$

Practice Problem 6.12

## Important characteristics of the basic elements



- Current and voltage relationship for R, L, C

Circuit element	Units	Voltage	Current	Power
 <b>Resistance</b>	ohms ( $\Omega$ )	$v = Ri$ (Ohm's law)	$i = \frac{v}{R}$	$p = vi = i^2 R$
 <b>Inductance</b>	henries (H)	$v = L \frac{di}{dt}$	$i = \frac{1}{L} \int v dt + k_1$	$p = vi = Li \frac{di}{dt}$
 <b>Capacitance</b>	farads (F)	$v = \frac{1}{C} \int i dt + k_2$	$i = C \frac{dv}{dt}$	$p = vi = Cv \frac{dv}{dt}$

## Important characteristics of the basic elements



Relation	Resistor ( $R$ )	Capacitor ( $C$ )	Inductor ( $L$ )
$v$ - $i$ :	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$	$v = L \frac{di}{dt}$
$i$ - $v$ :	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$
$p$ or $w$ :	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{\text{eq}} = R_1 + R_2$	$C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{\text{eq}} = L_1 + L_2$
Parallel:	$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{\text{eq}} = C_1 + C_2$	$L_{\text{eq}} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit
Circuit variable that cannot change abruptly:	Not applicable	$v$	$i$





# **Chapter 7**

## **Transistors and its Applications**



### **Bipolar Junction Transistor (BJT)**

# Bipolar Junction Transistor (BJT)




- 1 Device Structure and Physical Operation
- 2 Current-Voltage Characteristics
- 3 Modes of Operations
- 4 DC analysis of BJT circuits
- 5 AC analysis
- 6 BJT as Amplifier (C.E)
- 8 BJT as Switch
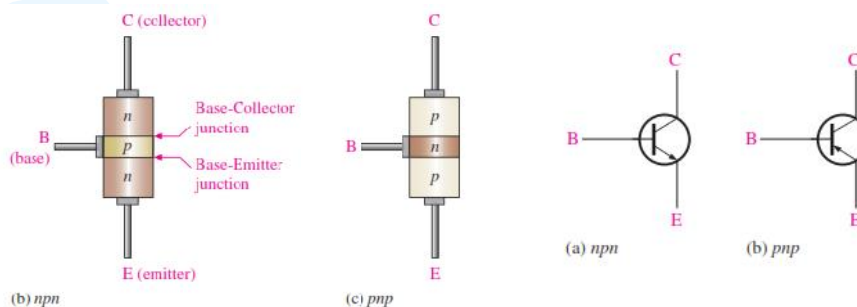
## Device Structure and Physical Operation



The BJT is constructed with three doped semiconductor regions separated by two pn junctions, as shown in the epitaxial planar structure in Figure (a). The three regions are called emitter, base, and collector.




## Current Controlled Current Source
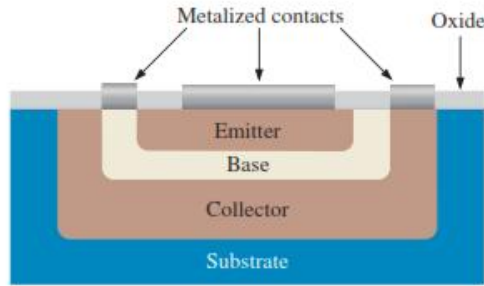
## Device Structure and Physical Operation



The pn junction joining the base region and the emitter region is called the base-emitter junction. The pn junction joining the base region and the collector region is called the base-collector junction




(a) Basic epitaxial planar structure


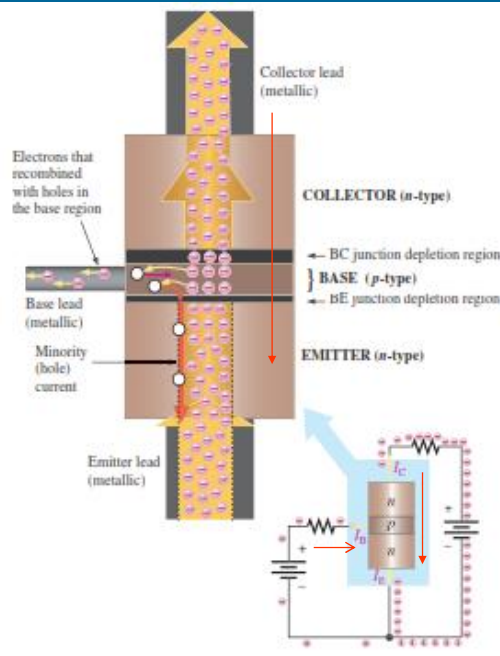
## Device Structure and Physical Operation



BJT consists of two pn junctions constructed in a special way and connected in series, back to back




# Modes of operation


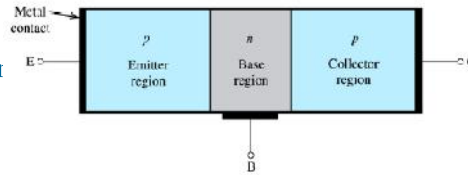
## Modes of operation

- The two junctions of BJT can be either forward or reverse-biased
- The BJT can operate in different modes depending on the junction bias
- The BJT operates in active mode for amplifier circuits
- Switching applications utilize both the cutoff and saturation modes




Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward

# Device Structure and Physical Operation




## Basic models of BJT


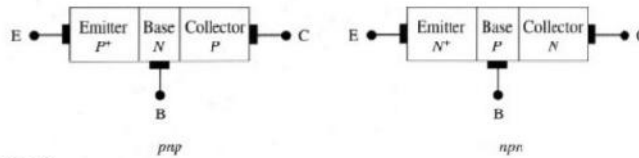
### Bipolar Junction Transistor Fundamentals



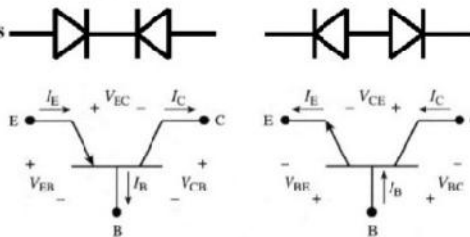Looks sort of like two diodes back to back



## Current-Voltage Characteristics

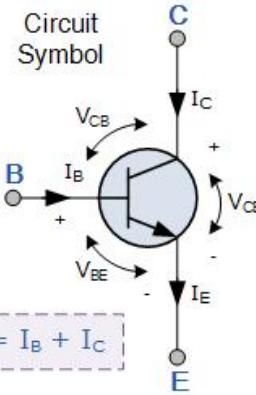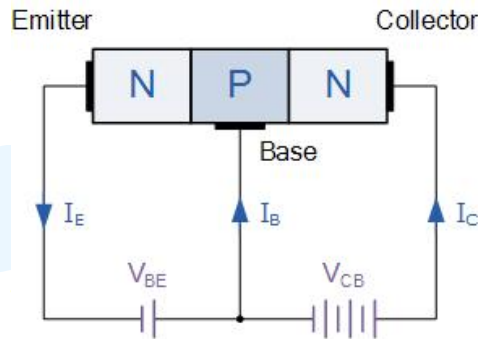



**KCL**

$$I_E = I_C + I_B$$

**KVL**

$$V_{CE} = V_{BE} + V_{BC}$$

## Current-Voltage Characteristics

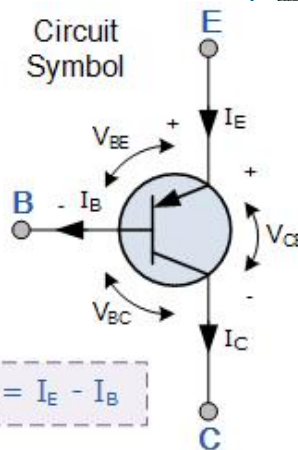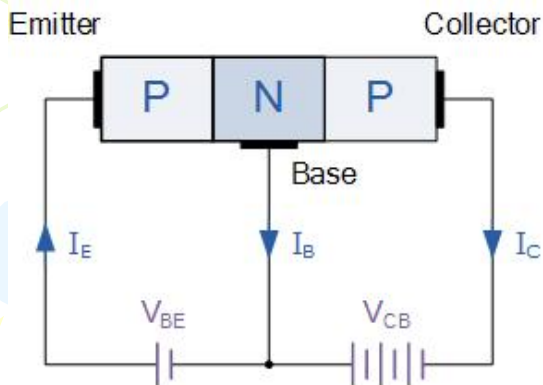

**KCL**

$$I_E = I_C + I_B$$

**KVL**

$$V_{CE} = V_{BE} + V_{BC}$$

## Current-Voltage Characteristics



### DC Beta ( $\beta_{DC}$ ) and DC Alpha ( $\alpha_{DC}$ )

The dc current **gain** of a transistor is the ratio of the dc collector current ( $I_C$ ) to the dc base current ( $I_B$ ) and is designated dc **beta** ( $\beta_{DC}$ ).

$$\beta_{DC} = \frac{I_C}{I_B} \qquad h_{FE} = \beta_{DC}$$

Typical values of  $\beta_{DC}$  range from less than 20 to 200 or higher.

The ratio of the dc collector current ( $I_C$ ) to the dc emitter current ( $I_E$ ) is the dc **alpha** ( $\alpha_{DC}$ ). The alpha is a less-used parameter than beta in transistor circuits.

$$\alpha_{DC} = \frac{I_C}{I_E}$$

Typically, values of  $\alpha_{DC}$  range from 0.95 to 0.99 or greater, but  $\alpha_{DC}$  is always less than 1.

## BJT



### Current Controlled (dependent) Current Source (CCCS)

Common-base current gain


Common-emitter current gain:

$$i_E = i_C + i_B$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

## Biasing

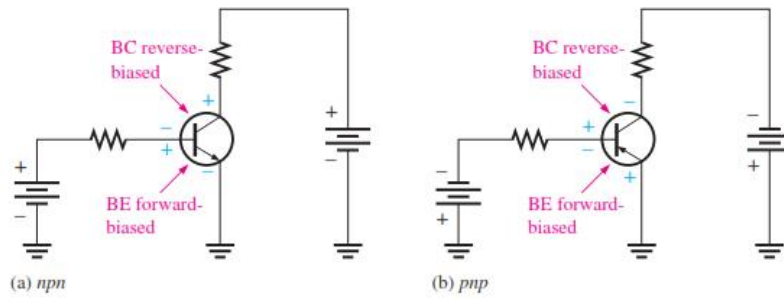


## DC Biasing

## Biasing



## Voltage divider

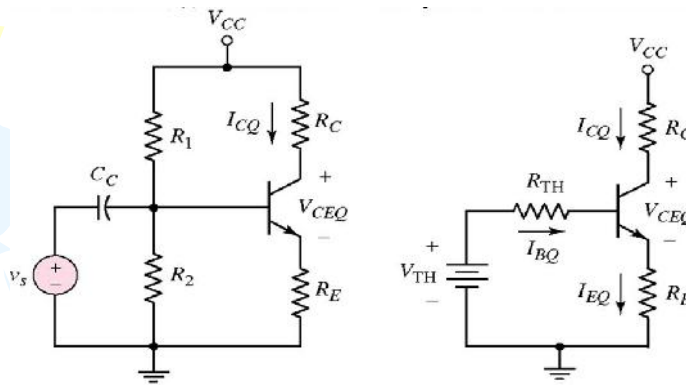

$$V_{TH} = V_{CC} \frac{R_2}{R_1 + R_2}$$

$$R_{TH} = R_1 // R_2$$

$$V_{TH} = V_{CC} * R_2 / (R_2 + R_1)$$

# Biasing




## Voltage divider bias or Self bias

$$I_{\bar{i}} = \frac{V_{BB} - V_{BE}}{R_{\bar{B}} + R_B / (\beta + 1)}$$


$$V_{HH} \gg V_{BE}$$

$$R_E \gg \frac{R_B}{(\beta + 1)}$$

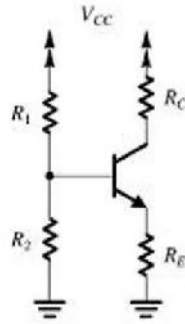

(a)



Circuit

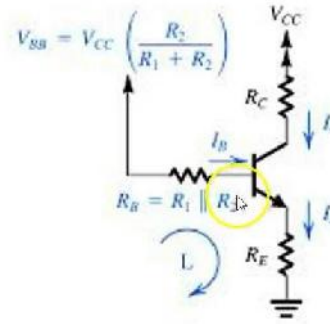

(b)


Equivalent circuit with  $V_{TH}$  &  $R_{TH}$
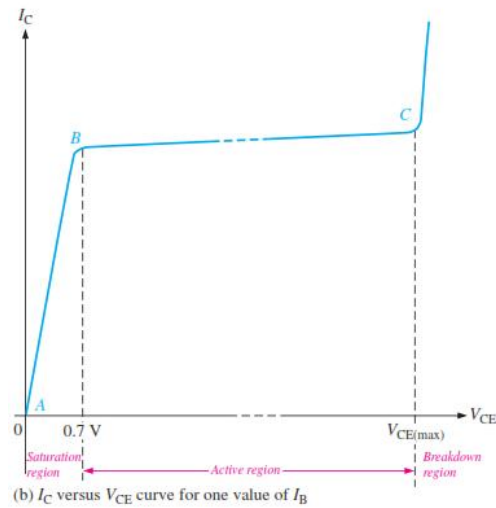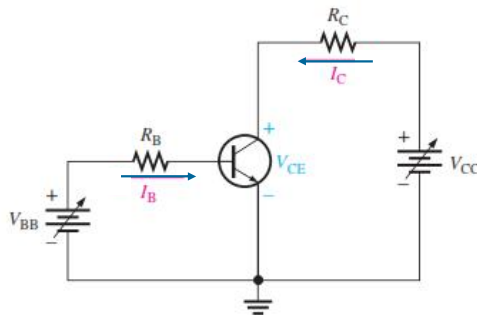
## Current-voltage characteristics of BJT





## Current-Voltage Characteristics

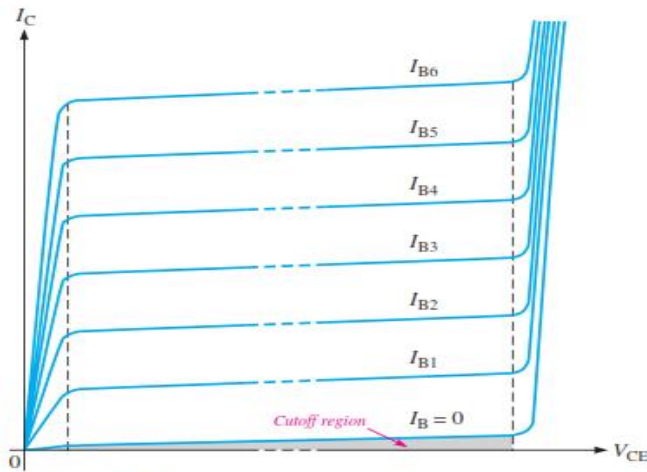

(c) Family of  $I_C$  versus  $V_{CE}$  curves for several values of  $I_B$   
( $I_{B1} < I_{B2} < I_{B3}$ , etc.)

## The Early effect




**Early voltage** ( $V_A$ ) is used for the linear approximation of Early Effect

The  $i_C$  curve has a finite slope due to **Early effect**

□ The characteristics lines meet at  $v_{CE} = -V_A$

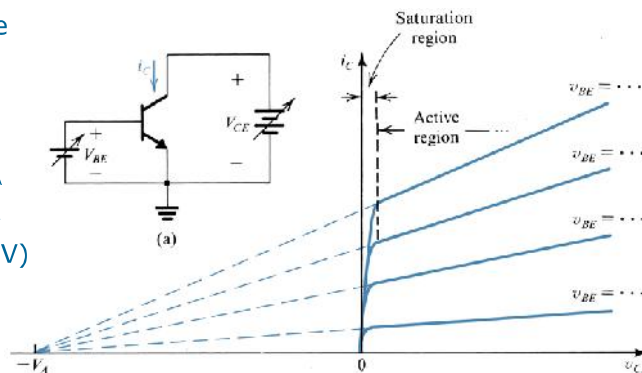□  $V_A$  is called the **Early Voltage** ( $\sim 50$  to  $100$  V)



## Regions of Operation



### 1- Cut off

$$I_B = 0, I_C = 0, V_{CE} = V_{CC}, \\ V_{BE} < 0.5V,$$

### 2- Saturation Beta is Low


$$i_C = I_S e^{v_{EB}/V_T}$$

$$V_{CE} < 0.3V, V_{BE} = 0.7V$$

### 3- Active Beta is High

$$V_{CE} > 0.3V$$


$$i_B = \frac{i_C}{\beta}$$

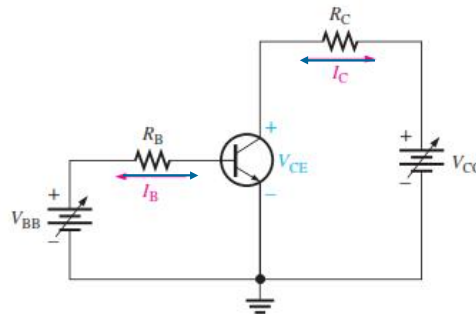
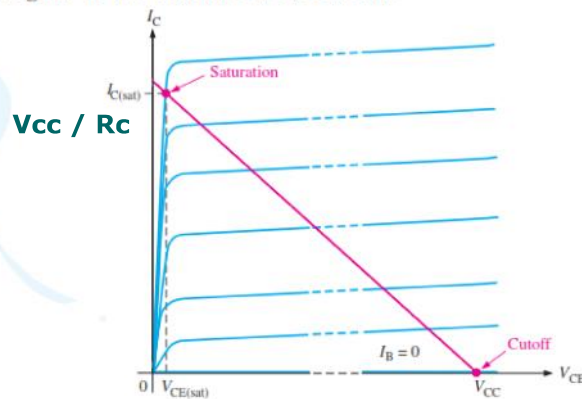
## DC Load Line



The bottom of the load line is at ideal cutoff where  $I_C = 0$  and  $V_{CE} = V_{CC}$ . The top of the load line is at saturation where  $I_C = I_{C(sat)}$  and  $V_{CE} = V_{CE(sat)}$ . In between cutoff and saturation along the load line is the *active region* of the transistor's operation.





## DC analysis of BJT circuits



### DC analysis of BJT circuits

- Step 1: assume the operation mode
- Step 2: use the conditions or model for circuit analysis.
- Step 3: verify the solution
- Step 4: repeat the above steps with another assumption if necessary


## BJT Circuits at DC

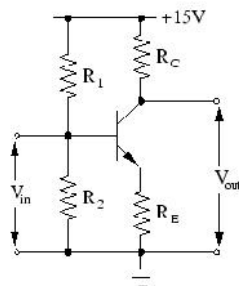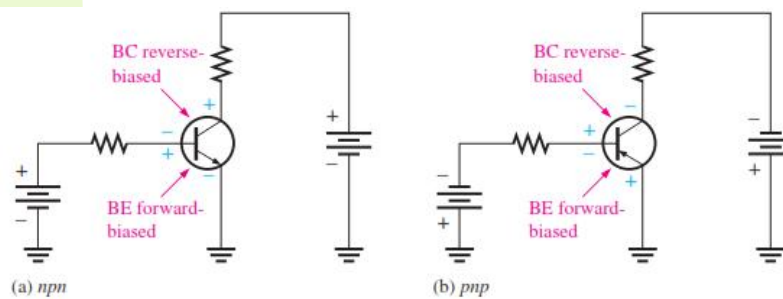
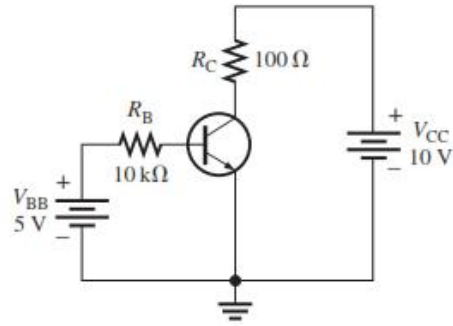
## BJT



Determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{BE}$ ,  $V_{CE}$ , and  $V_{CB}$  in the circuit of Figure 4–9. The transistor has a  $\beta_{DC} = 150$ .



## BJT



Determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{BE}$ ,  $V_{CE}$ , and  $V_{CB}$  in the circuit of Figure 4–9. The transistor has a  $\beta_{DC} = 150$ .

**Solution** From Equation 4–3,  $V_{BE} \cong 0.7 \text{ V}$ . Calculate the base, collector, and emitter currents as follows:

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = 430 \mu\text{A}$$

$$I_C = \beta_{DC} I_B = (150)(430 \mu\text{A}) = 64.5 \text{ mA}$$

$$I_E = I_C + I_B = 64.5 \text{ mA} + 430 \mu\text{A} = 64.9 \text{ mA}$$

Solve for  $V_{CE}$  and  $V_{CB}$ .

$$V_{CE} = V_{CC} - I_C R_C = 10 \text{ V} - (64.5 \text{ mA})(100 \Omega) = 10 \text{ V} - 6.45 \text{ V} = 3.55 \text{ V}$$


$$V_{CB} = V_{CE} - V_{BE} = 3.55 \text{ V} - 0.7 \text{ V} = 2.85 \text{ V}$$

Since the collector is at a higher voltage than the base, the collector-base junction is reverse-biased.
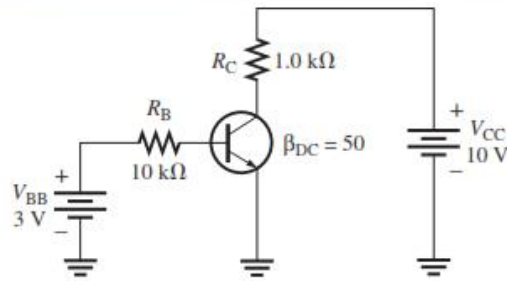
## BJT



Determine whether or not the transistor in Figure 4–16 is in saturation. Assume  $V_{CE(\text{sat})} = 0.2 \text{ V}$ .



## BJT



Determine whether or not the transistor in Figure 4–16 is in saturation. Assume  $V_{CE(\text{sat})} = 0.2 \text{ V}$ .

**Solution** First, determine  $I_{C(\text{sat})}$ .

$$I_{C(\text{sat})} = \frac{V_{CC} - V_{CE(\text{sat})}}{R_C} = \frac{10 \text{ V} - 0.2 \text{ V}}{1.0 \text{ k}\Omega} = \frac{9.8 \text{ V}}{1.0 \text{ k}\Omega} = 9.8 \text{ mA}$$

Now, see if  $I_B$  is large enough to produce  $I_{C(\text{sat})}$ .

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{3 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = \frac{2.3 \text{ V}}{10 \text{ k}\Omega} = 0.23 \text{ mA}$$

$$I_C = \beta_{DC} I_B = (50)(0.23 \text{ mA}) = 11.5 \text{ mA}$$

This shows that with the specified  $\beta_{DC}$ , this base current is capable of producing an  $I_C$  greater than  $I_{C(\text{sat})}$ . Therefore, the **transistor is saturated**, and the collector current value of 11.5 mA is never reached. If you further increase  $I_B$ , the collector current remains at its saturation value of 9.8 mA.

## BJT Datasheet



A partial datasheet for the 2N3904 *npn* transistor is shown in Figure 4–20. Notice that the maximum collector-emitter voltage ( $V_{CEO}$ ) is 40 V. The CEO subscript indicates that the voltage is measured from collector (C) to emitter (E) with the base open (O). In the text, we use  $V_{CE(max)}$  for this parameter. Also notice that the maximum collector current is 200 mA.

The  $\beta_{DC}$  ( $h_{FE}$ ) is specified for several values of  $I_C$ . As you can see,  $h_{FE}$  varies with  $I_C$  as we previously discussed.


The collector-emitter saturation voltage,  $V_{CE(sat)}$  is 0.2 V maximum for  $I_{C(sat)} = 10$  mA and increases with the current.

## BJT Datasheet




**FAIRCHILD**  
SEMICONDUCTOR

**2N3904**




TO-92

**MMBT3904**

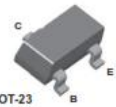

SOT-23  
Mark: 1A

**PZT3904**

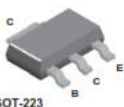

SOT-223

**NPN General Purpose Amplifier**

This device is designed as a general purpose amplifier and switch. The useful dynamic range extends to 100 mA as a switch and to 100 MHz as an amplifier.

**Absolute Maximum Ratings\***  $T_J = 25^\circ\text{C}$  unless otherwise noted

Symbol	Parameter	Value	Units
$V_{CE0}$	Collector-Emitter Voltage	40	V
$V_{CB0}$	Collector-Base Voltage	60	V
$V_{EB0}$	Emitter-Base Voltage	6.0	V
$I_C$	Collector Current - Continuous	200	mA
$T_J, T_{stg}$	Operating and Storage Junction Temperature Range	-55 to +150	$^\circ\text{C}$

\*These ratings are limiting values above which the serviceability of any semiconductor device may be impaired.

# BJT Datasheet








Electrical Characteristics <small>T<sub>a</sub> = 25°C unless otherwise noted</small>					
Symbol	Parameter	Test Conditions	Min	Max	Units
<b>OFF CHARACTERISTICS</b>					
V <sub>BRCEO</sub>	Collector-Emitter Breakdown Voltage	I <sub>C</sub> = 1.0 mA, I <sub>B</sub> = 0	40		V
V <sub>BRCEO</sub>	Collector-Base Breakdown Voltage	I <sub>C</sub> = 10 μA, I <sub>E</sub> = 0	60		V
V <sub>BRCEO</sub>	Emitter-Base Breakdown Voltage	I <sub>E</sub> = 10 μA, I <sub>C</sub> = 0	6.0		V
I <sub>BL</sub>	Base Cutoff Current	V <sub>CE</sub> = 30 V, V <sub>EB</sub> = 3V		50	nA
I <sub>CX</sub>	Collector Cutoff Current	V <sub>CE</sub> = 30 V, V <sub>EB</sub> = 3V		50	nA
<b>ON CHARACTERISTICS*</b>					
h <sub>FE</sub>	DC Current Gain	I <sub>C</sub> = 0.1 mA, V <sub>CE</sub> = 1.0 V I <sub>C</sub> = 1.0 mA, V <sub>CE</sub> = 1.0 V I <sub>C</sub> = 10 mA, V <sub>CE</sub> = 1.0 V I <sub>C</sub> = 50 mA, V <sub>CE</sub> = 1.0 V I <sub>C</sub> = 100 mA, V <sub>CE</sub> = 1.0 V	40 70 100 60 30	300	
V <sub>CE(sat)</sub>	Collector-Emitter Saturation Voltage	I <sub>C</sub> = 10 mA, I <sub>B</sub> = 1.0 mA I <sub>C</sub> = 50 mA, I <sub>B</sub> = 5.0 mA		0.2 0.3	V
V <sub>BE(sat)</sub>	Base-Emitter Saturation Voltage	I <sub>C</sub> = 10 mA, I <sub>B</sub> = 1.0 mA I <sub>C</sub> = 50 mA, I <sub>B</sub> = 5.0 mA	0.65	0.65 0.65	V
<b>SMALL SIGNAL CHARACTERISTICS</b>					
f <sub>T</sub>	Current Gain - Bandwidth Product	I <sub>C</sub> = 10 mA, V <sub>CE</sub> = 20 V, f = 100 MHz	300		MHz
C <sub>ob</sub>	Output Capacitance	V <sub>CE</sub> = 5.0 V, I <sub>B</sub> = 0, f = 1.0 MHz		4.0	pF
C <sub>ib</sub>	Input Capacitance	V <sub>BE</sub> = 0.5 V, I <sub>C</sub> = 0, f = 1.0 MHz		6.0	pF
NF	Noise Figure	I <sub>C</sub> = 100 μA, V <sub>CE</sub> = 5.0 V, R <sub>g</sub> = 1.0 kΩ, f = 10 Hz to 15.7 kHz		5.0	dB

# BJT Configurations



**V<sub>in</sub> >>> E or B**

**V<sub>out</sub> >>> E or C**

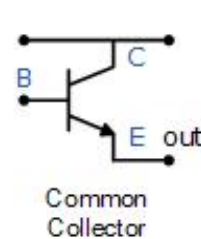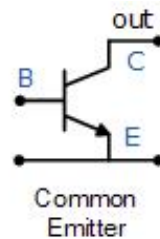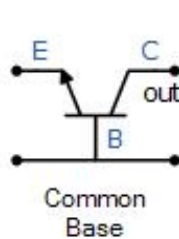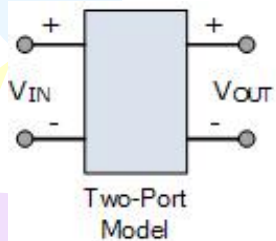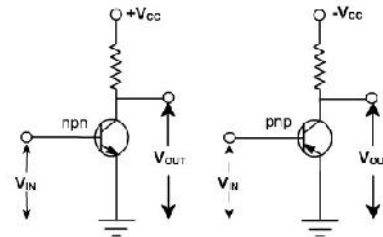


## BJT Configurations



$V_{input} \gg E$  or  $B$

$V_{output} \gg E$  or  $C$

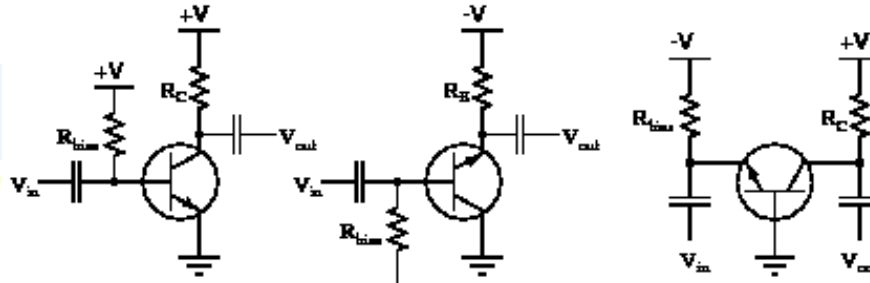

Grounded-emitter  
(Common-emitter)

Grounded-collector  
(Common-collector)

Grounded-base  
(Common-base)

## BJT Configurations




$V_{input} \gg E$  or  $B$

$V_{output} \gg E$  or  $C$

Common-Emitter (CE)




Common-Base (CB)

Common-Collector (CC)

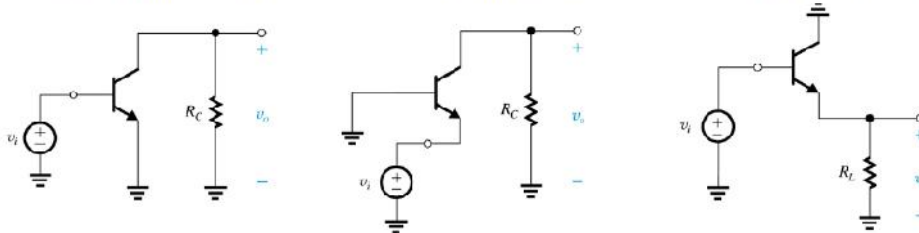



## AC analysis

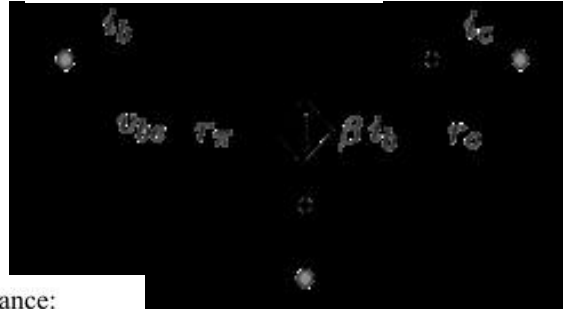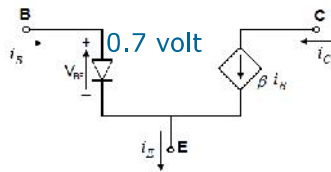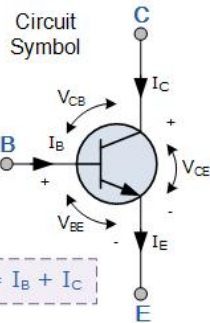

Input resistance:

$$r_{\pi} = \frac{\beta_o V_T}{I_C}$$

At Q point

Output resistance:


$$r_o = \frac{V_A + V_{CE}}{I_C}$$

small signal model analysis  
Active region
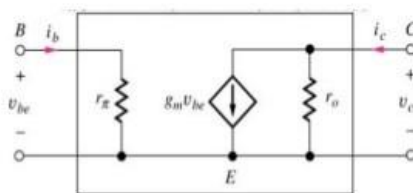
## AC analysis



Hybrid-Pi Small-signal AC Model for the BJT



- The hybrid-pi small-signal model is the intrinsic low-frequency representation of the BJT.
- The small-signal parameters are controlled by the Q-point and are independent of the geometry of the BJT.

Transconductance:

$$g_m = \frac{I_C}{V_T} \cong 40 I_C$$

Input resistance:

$$r_{\pi} = \frac{\beta_o V_T}{I_C} = \frac{\beta_o}{g_m}$$

Output resistance:


$$r_o = \frac{V_A + V_{CE}}{I_C}$$

$$r_{\pi} = \frac{V_T}{I_B} = \beta \frac{V_T}{I_C} \quad r_o = \frac{|V_A|}{I_C} \quad r_x = \frac{\beta}{g_m}$$
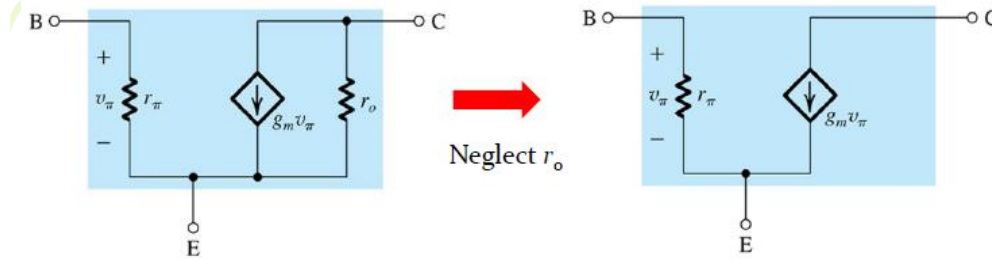
## AC analysis



small signal model analysis  
Active region



## BJT Applications



Used as Amplifier in Active Region

Used as Switch in Saturation and Cut off Region

Used as Logic Gates in Saturation(on) and Cut off (off) Region

## BJT as Amplifier : AC analysis




The electrical properties of the amplifier is represented by  $R_{in}$ ,  $R_o$  and  $A_{vo}$

The analysis is based on the small-signal or linear equivalent circuit (dc components not included)

$$\square \text{Voltage gain: } A_v \equiv \frac{v_o}{v_i} = \frac{R_L}{R_L + R_o} A_{vo}$$
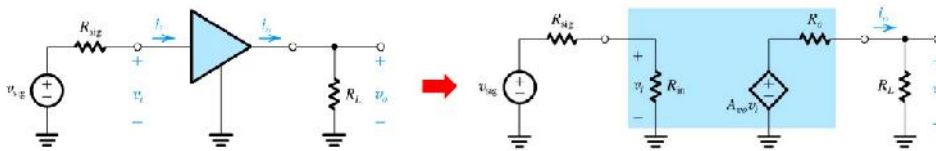
$$\text{Overall voltage gain } G_v \equiv \frac{v_o}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} A_v = \frac{R_{in}}{R_{in} + R_{sig}} \frac{R_L}{R_L + R_o} A_{vo}$$




## BJT as Amplifier



CE

### Voltage Amplification

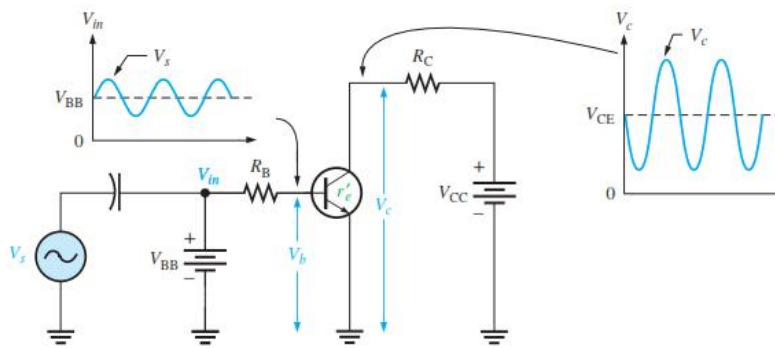


Since  $I_c \cong I_e$ , the ac collector voltage is

$$V_c \cong I_e R_C$$


## BJT as Amplifier



CE

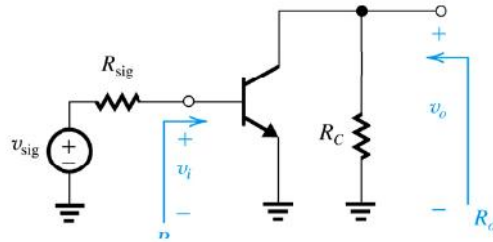

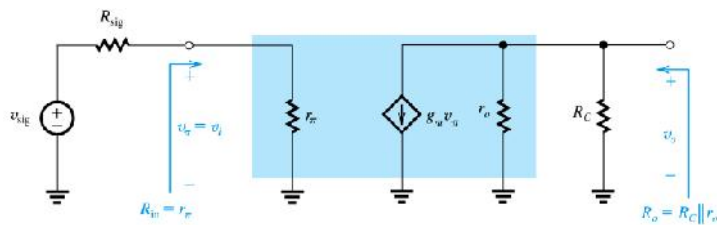
Characteristic parameters of the CE amplifier



## BJT as Amplifier



CE

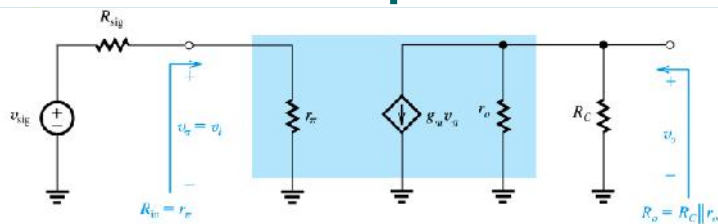


Characteristic parameters of the CE amplifier

- Input resistance:  $R_m = r_\pi$   $r_\pi = \frac{\beta}{g_m}$
- Output resistance:  $R_o = R_C \parallel r_o \approx R_C$
- Open-circuit voltage gain:  $A_{vo} = -g_m (R_C \parallel r_o) \approx -g_m R_C$
- Voltage gain:  $A_v = -g_m (R_C \parallel R_L \parallel r_o) \approx -g_m (R_C \parallel R_L)$
- Overall voltage gain:  $G_v = -\frac{r_\pi}{r_\pi + R_{sig}} g_m (R_C \parallel R_L \parallel r_o) \approx -g_m \frac{r_\pi}{r_\pi + R_{sig}} (R_C \parallel R_L)$

## The common-emitter (CE) amplifier



### Common Emitter Amplifier

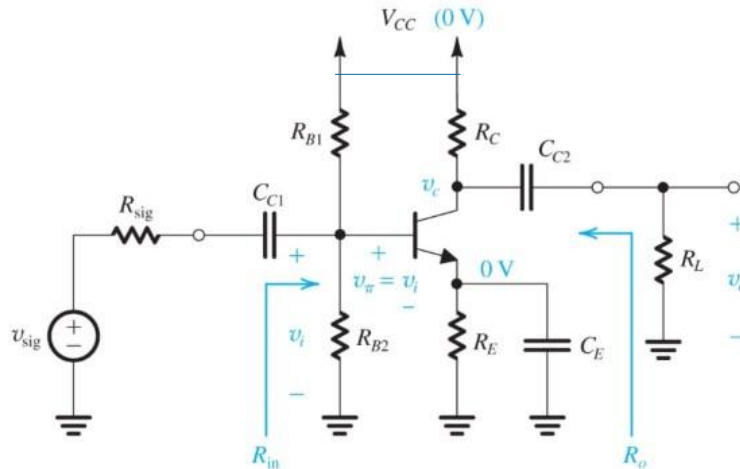

The capacitor  $C_E$  is called a bypass capacitor.

## The common-emitter (CE) amplifier



### DC analysis (Determine Q point)

(a) Replace the capacitors with open circuits. Look out of the BJT terminals and make Thévenin equivalent circuits as shown in Fig.

(b) Calculate  $g_m$ ,  $r_\pi$ ,  $r_e$ , and  $r_o$  from the DC solution.


$$g_m = \frac{I_C}{V_T} \quad r_\pi = \frac{V_T}{I_B} \quad r_e = \frac{V_T}{I_E} \quad r_o = \frac{V_A + V_{CE}}{I_C}$$

$$r_\pi = \frac{V_T}{I_B} = \beta \frac{V_T}{I_C} \quad r_\pi = \frac{\beta}{g_m}$$

## The common-emitter (CE) amplifier



### DC analysis (Determine Q point)

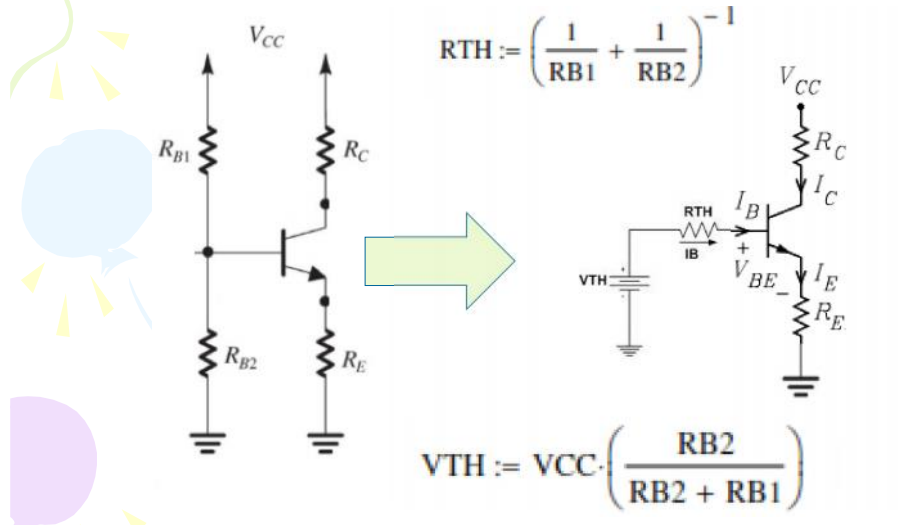

## The common-emitter (CE) amplifier



### DC analysis (Determine Q point)

$$I_B := \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) \cdot R_E}$$

$$I_C := \beta \cdot I_B$$


$$I_E := (\beta + 1) \cdot I_B$$

$$V_E := I_E \cdot R_E$$

$$V_B := V_E + V_{BE}$$

$$V_C := V_{CC} - I_C \cdot R_C$$

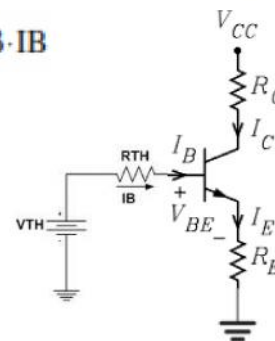DC Quiescent Power  $P_{DQ} = I_{CQ} V_{CEQ}$




Verify that  $V_{CE} > 0$  for the active mode.

$$V_{CE} = V_C - V_B \quad V_{CE} > 0.3 \text{ V}$$

## The common-emitter (CE) amplifier



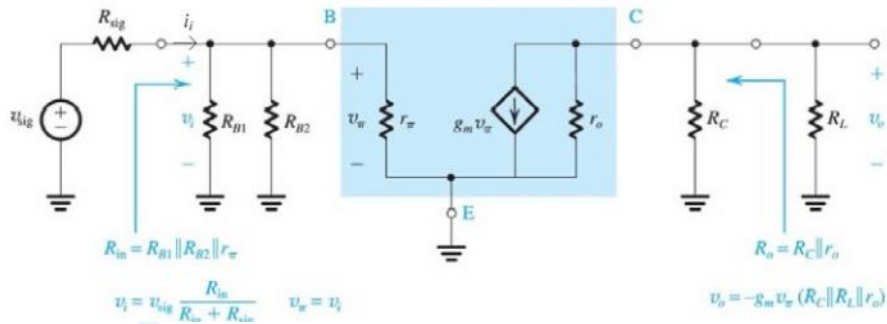
### Common Emitter Small-Signal Amplifier Analysis



the overall voltage gain  $G_v = v_o/v_{sig}$       voltage gain  $A_v = v_o/v_i$ ,

## The common-emitter (CE) amplifier

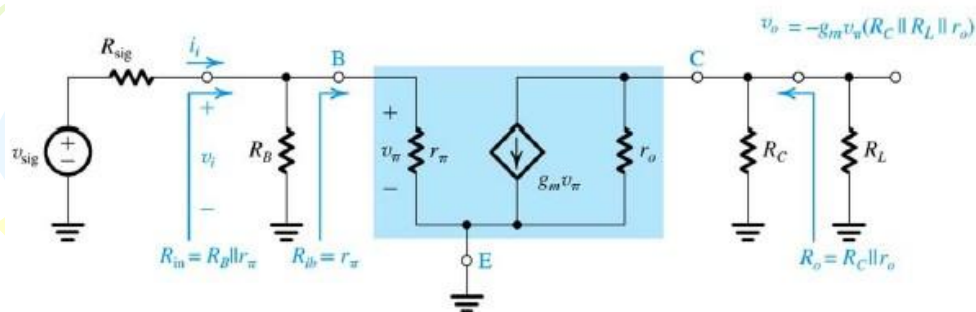

current gain  $A_{is} = i_{os}/i_i$

## The common-emitter (CE) amplifier



- 1 Input resistance,  $R_{in}$ .

$$R_{in} = R_{B1} \parallel R_{B2} \parallel r_{\pi}$$

- 2 small-signal voltage gain,  $A_v$ .

$$A_v \equiv \frac{v_o}{v_i}$$

$$v_i = v_{\pi}$$

$$v_o = -g_m v_{\pi} (r_o \parallel R_C \parallel R_L)$$

$$A_v = -g_m (r_o \parallel R_C \parallel R_L)$$

## The common-emitter (CE) amplifier



- 3 Overall small-signal voltage gain,  $G_v$ .

$$G_v \equiv \frac{v_o}{v_{sig}}$$

$$G_v = \frac{v_o}{v_{sig}} = \frac{-g_m R_{in}}{R_{in} + R_{sig}} (r_o \parallel R_C \parallel R_L)$$

$$v_o = -g_m v_{\pi} (r_o \parallel R_C \parallel R_L)$$

$$v_i = v_{\pi} = \frac{R_{in}}{R_{in} + R_{sig}} v_{sig}$$

$$G_v \approx \frac{-\beta (r_o \parallel R_C \parallel R_L)}{r_{\pi} + R_{sig}}$$

$$r_{\pi} = \beta / g_m$$



## The common-emitter (CE) amplifier



4 Overall small-signal current gain,  $G_i$ .

$$G_i \equiv \frac{i_o}{i_i} \quad v_i = v_\pi$$

$$i_i = \frac{v_i}{R_{in}} \quad \text{and} \quad i_o = \frac{v_o}{R_L} \quad v_o = -g_m v_\pi (r_o \parallel R_C \parallel R_L)$$

$$G_i = \frac{i_o}{i_i} = \frac{R_{in}}{R_L} \frac{v_o}{v_i} = \frac{R_{in}}{R_L} A_v = \frac{r_\pi \parallel R_{B1} \parallel R_{B2}}{R_L} A_v$$

$$G_i = \frac{-g_m (r_\pi \parallel R_{B1} \parallel R_{B2}) (r_o \parallel R_C \parallel R_L)}{R_L}$$

## The common-emitter (CE) amplifier



5 Short circuit small-signal current gain,  $A_{is}$ .

signal current gain of the amplifier but with a short circuited load ( $R_L = 0$ ):

$$A_{is} \equiv \frac{i_{os}}{i_i}$$

$$A_{is} = G_i \Big|_{R_L=0}$$

$$A_{is} = -g_m (r_\pi \parallel R_{B1} \parallel R_{B2})$$

## The common-emitter (CE) amplifier



### 6 Output resistance $R_o$ .

$$R_o = R_C \parallel r_o$$


### 7 Power Gain

$$A_p = \frac{P_L}{P_{in}} \quad A_p = A_v^2 \left( \frac{R_{in}}{R_L} \right)$$

Summary for the common emitter amplifier:


- ✓ Big voltage and current gains are possible.
- ✓ Input resistance is moderately large.
- ✓ Output resistance is fairly large.

## BJT as a Switch

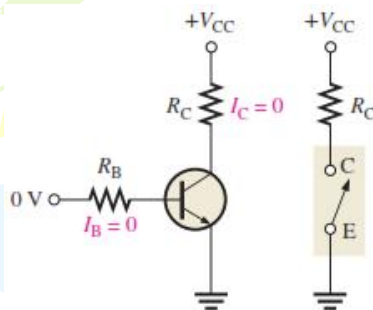

(a) Cutoff — open switch

$$V_{CE(\text{cutoff})} = V_{CC}$$

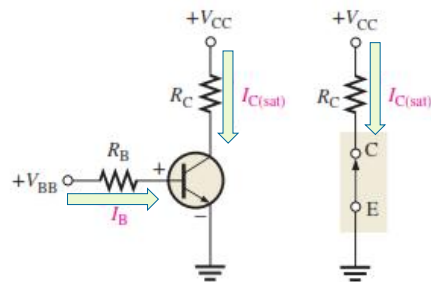

(b) Saturation — closed switch

$$I_{C(\text{sat})} = \frac{V_{CC} - V_{CE(\text{sat})}}{R_C}$$


$V_{CE(\text{sat})}$  is very small compared to  $V_{CC}$ ,

$$I_{B(\text{min})} = \frac{I_{C(\text{sat})}}{\beta_{DC}}$$

## BJT as a Switch



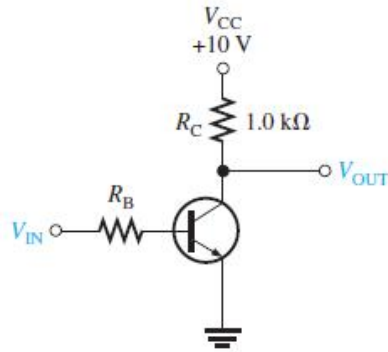- (a) For the transistor circuit in Figure 4–24, what is  $V_{CE}$  when  $V_{IN} = 0$  V?
- (b) What minimum value of  $I_B$  is required to saturate this transistor if  $\beta_{DC}$  is 200? Neglect  $V_{CE(sat)}$ .
- (c) Calculate the maximum value of  $R_B$  when  $V_{IN} = 5$  V.



## BJT as a Switch



- (a) When  $V_{IN} = 0$  V, the transistor is in cutoff (acts like an open switch) and  
 $V_{CE} = V_{CC} = 10$  V

- (b) Since  $V_{CE(sat)}$  is neglected (assumed to be 0 V),

$$I_{C(sat)} = \frac{V_{CC}}{R_C} = \frac{10 \text{ V}}{1.0 \text{ k}\Omega} = 10 \text{ mA}$$

$$I_{B(min)} = \frac{I_{C(sat)}}{\beta_{DC}} = \frac{10 \text{ mA}}{200} = 50 \mu\text{A}$$

This is the value of  $I_B$  necessary to drive the transistor to the point of saturation. Any further increase in  $I_B$  will ensure the transistor remains in saturation but there cannot be any further increase in  $I_C$ .

## BJT as a switch.



(c) When the transistor is on,  $V_{BE} \cong 0.7 \text{ V}$ . The voltage across  $R_B$  is

$$V_{R_B} = V_{IN} - V_{BE} \cong 5 \text{ V} - 0.7 \text{ V} = 4.3 \text{ V}$$

Calculate the maximum value of  $R_B$  needed to allow a minimum  $I_B$  of  $50 \mu\text{A}$  using Ohm's law as follows:


$$R_{B(\text{max})} = \frac{V_{R_B}}{I_{B(\text{min})}} = \frac{4.3 \text{ V}}{50 \mu\text{A}} = 86 \text{ k}\Omega$$

## BJT as a switch.


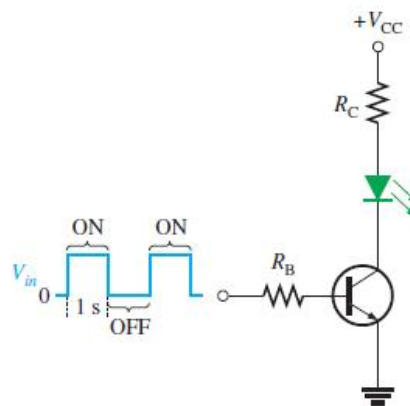
### A Simple Application of a Transistor Switch

A transistor used to switch an LED on and off.




## BJT as a Logic gates (NOT).



### Inverter ( NOT )


NOT Gate

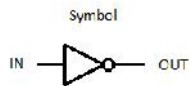



Logic function:  
 IN - A; OUT - Q;  
 $Q = \text{NOT } A$

Table of truth



IN	OUT
0	1
1	0

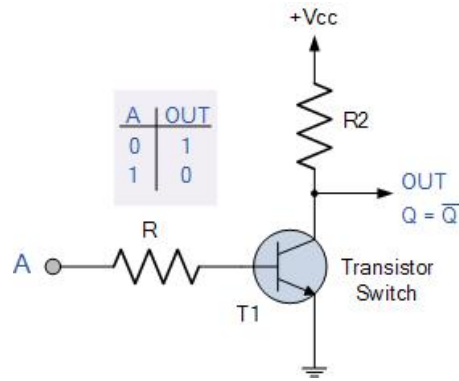

## BJT as a Logic gates (AND).

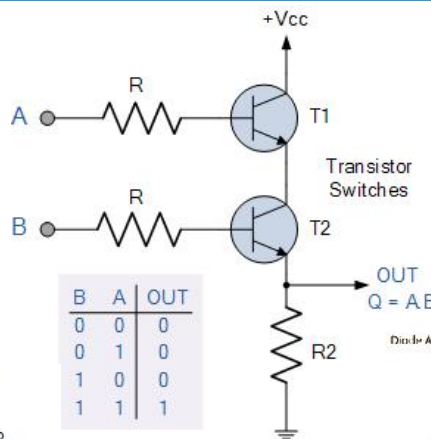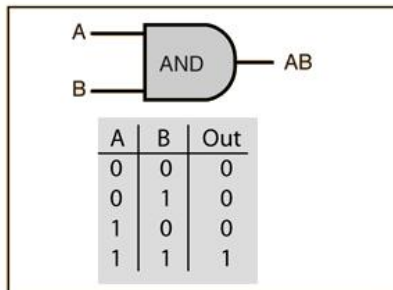

High 5v  
 Low 0v

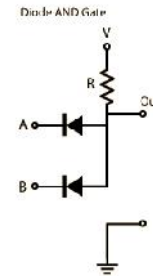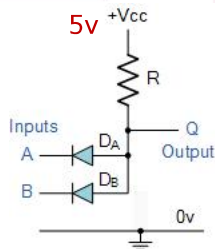

## BJT as a Logic gates (OR).




Symbol




Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Diode OR Gate

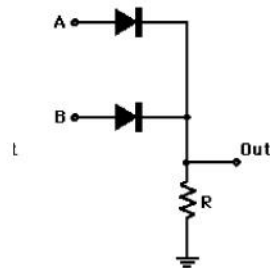


B	A	OUT
0	0	0
0	1	1
1	0	1
1	1	1

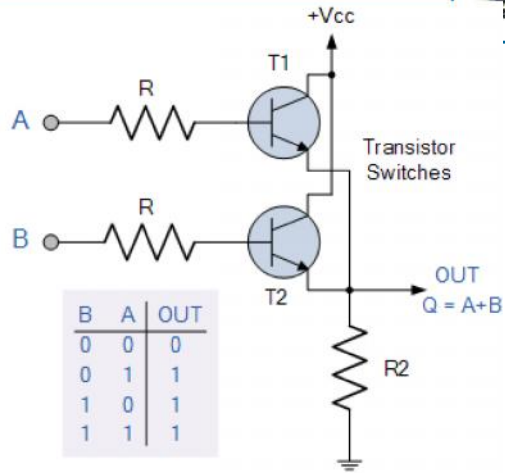

## BJT as a Logic gates (OR).




3 Input OR gate

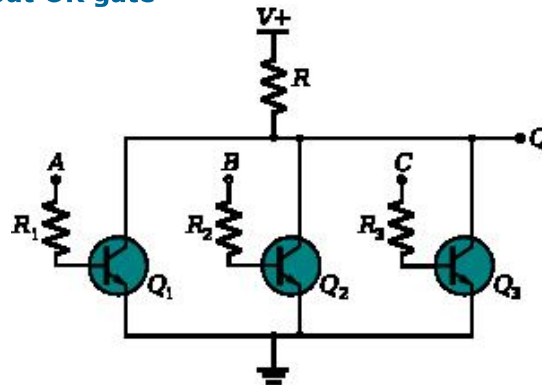


## BJT as a Logic gates (NOR).



Implement the Nor Gate with BJT

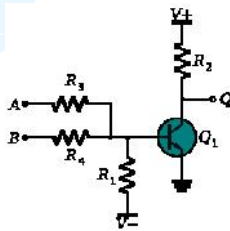


B	A	OUT
0	0	1
0	1	0
1	0	0
1	1	0

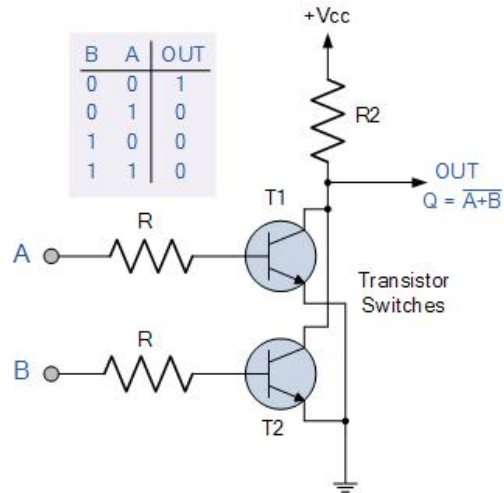


## BJT as a Logic gates (NAND).



Implement the NAND Gate with BJT

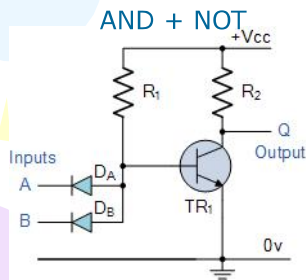

B	A	OUT
0	0	1
0	1	1
1	0	1
1	1	0

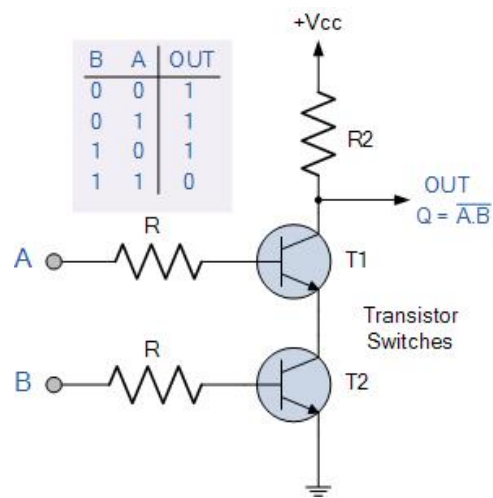



## Field-Effect Transistors (FETs)

## Field-Effect Transistors (FETs)



Few important advantages of FET over conventional Transistors

1. Unipolar device i. e. operation depends on only one type of charge carriers ( $h$  or  $e$ )
2. Voltage controlled Device (gate voltage controls drain current)
3. Very high input impedance ( $\approx 10^9$ - $10^{12} \Omega$ )
4. Source and drain are interchangeable in most Low-frequency applications
5. Low Voltage Low Current Operation is possible (Low-power consumption)
6. Less Noisy as Compared to BJT
7. No minority carrier storage (Turn off is faster)
8. Self limiting device
9. Very small in size, occupies very small space in ICs
10. Low voltage low current operation is possible in MOSFETS
11. Zero temperature drift of out put is possible



## Introduction to FET



- **FET: Field Effect Transistor**
- **There are two types**
  - **MOSFET: metal-oxide-semiconductor FET**
  - **JFET: Junction FET (Field Effect Transistor)**
- **MOSFET is also called the insulated-gate FET or IGFET.**
  - **Quite small**
  - **Simple manufacturing process**
  - **Low power consumption and High Input Resistance**
  - **Widely used in VLSI circuits(>800 million on a single IC chip)**
  - **Disadvantages : low gain ----- narrow bandwidth**



## Classification of FET




- **According to the type of the channel, FETs can be classified as**
  - **MOSFET**
    - **N channel**
    - **P channel**
  - **JFET**
    - **P channel**
    - **N channel**

## Classification of FET



### • Types of FET

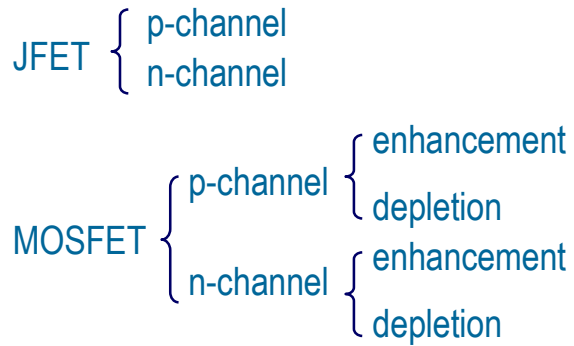

## Field Effect Transistor (FET)



The input-output transfer characteristic of the JFET is not as straight forward as it is for the BJT

In a BJT,  $\beta$  ( $h_{FE}$ ) defined the relationship between  $I_B$  (input current) and  $I_C$  (output current).

In a JFET, the relationship (Shockley's Equation) between  $V_{GS}$  (input voltage) and  $I_D$  (output current) is used to define the transfer characteristics, and a little more complicated (and not linear):

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$



As a result, FET's are often referred to a square law devices
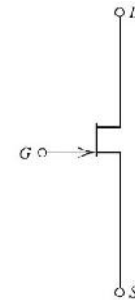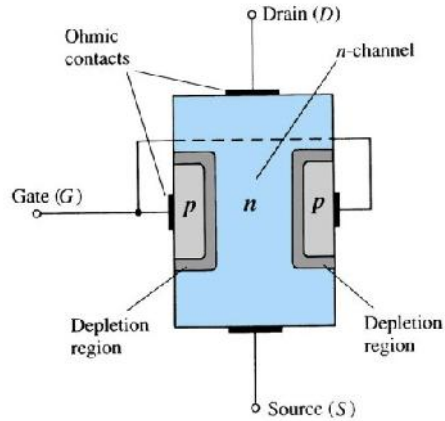
## JFET Construction



There are two types of JFET's: n-channel and p-channel.  
The n-channel is more widely used.


**Voltage  
Controlled  
Current  
Source**



(b) Circuit symbol

There are three terminals: Drain (D) and Source (S) are connected to n-channel  
Gate (G) is connected to the p-type material

## N-Channel JFET Symbol

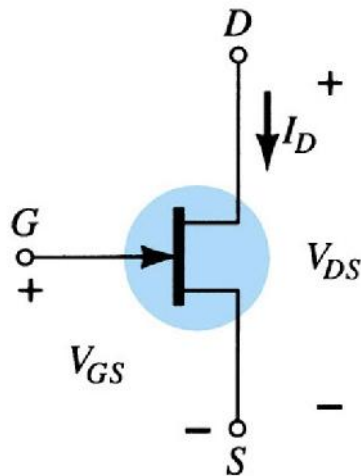


(a)

# Case Construction and Terminal Identification



## 2N2844

CASE 22-03, STYLE 12  
TO-18 (TO-206AA)

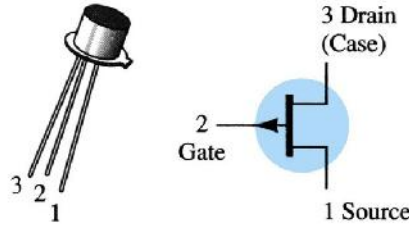

**JFETs**  
**GENERAL PURPOSE**  
**P-CHANNEL**

This information is found on the specification sheet

# Specification Sheet (JFETs)



MAXIMUM RATINGS			
Rating	Symbol	Value	Unit
Drain-Source Voltage	$V_{DS}$	25	Vdc
Drain-Gate Voltage	$V_{DG}$	25	Vdc
Reverse Gate-Source Voltage	$V_{SG}$	-25	Vdc
Gate Current	$I_G$	10	$\mu$ Acd
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Density above $25^\circ\text{C}$	$P_D$	2.0 2.87	mW mW/ $^\circ\text{C}$
Junction Temperature Range	$T_J$	125	$^\circ\text{C}$
Storage Channel Temperature Range	$T_{stg}$	-65 to +150	$^\circ\text{C}$



ELECTRICAL CHARACTERISTICS ( $T_A = 25^\circ\text{C}$ , unless otherwise noted)

Characteristic	Symbol	Min	Typ	Max	Unit
<b>OFF CHARACTERISTICS</b>					
Gate-Source Breakdown Voltage ( $I_D = -10 \mu\text{Acd}$ , $V_{DS} = 0$ )	$V_{DS(BR)}$	-25	-	-	Vdc
Gate Reverse Current ( $V_{DS} = -15 \text{ Vdc}$ , $V_{GS} = 0$ ) ( $V_{DS} = -10 \text{ Vdc}$ , $V_{GS} = 0$ , $T_A = -100^\circ\text{C}$ )	$I_{RSS}$	-	-	-1.0 -200	$\mu$ Acd
Gate Source Cutoff Voltage ( $V_{DS} = 15 \text{ Vdc}$ , $I_D = 10 \mu\text{Acd}$ )	$V_{GS(off)}$	-0.5	-	-6.0	Vdc
Gate Source Voltage ( $V_{DS} = 15 \text{ Vdc}$ , $I_D = 100 \mu\text{Acd}$ )	$V_{GS}$	-	-2.5	-	Vdc
<b>ON CHARACTERISTICS</b>					
Zero-Gate-Voltage Drain Current* ( $V_{DS} = 15 \text{ Vdc}$ , $V_{GS} = 0$ )	$I_{DSS}$	1.0	3.0	5.0	$\mu$ Acd
<b>SMALL-SIGNAL CHARACTERISTICS</b>					
Forward Transfer Admittance Common Source* ( $V_{DS} = 15 \text{ Vdc}$ , $V_{GS} = 0$ , $f = 1.0 \text{ kHz}$ )	$ h_{fs} $	1000	-	5000	$\mu\text{mho}$
Output Admittance Common Source* ( $V_{DS} = 15 \text{ Vdc}$ , $V_{GS} = 0$ , $f = 1.0 \text{ kHz}$ )	$ h_{os} $	-	10	50	$\mu\text{mho}$
Input Capacitance ( $V_{DS} = 15 \text{ Vdc}$ , $V_{GS} = 0$ , $f = 1.0 \text{ MHz}$ )	$C_{iss}$	-	4.5	7.0	pF
Reverse Transfer Capacitance ( $V_{DS} = 15 \text{ Vdc}$ , $V_{GS} = 0$ , $f = 1.0 \text{ MHz}$ )	$C_{rss}$	-	1.5	3.0	pF

## JFET Operating Characteristics



There are three basic operating conditions for a JFET:

**JFET's operate in the depletion mode only**

- $V_{GS} = 0$ ,  $V_{DS}$  is a minimum value depending on  $I_{DSS}$  and the drain and source resistance
- $V_{GS} < 0$ ,  $V_{DS}$  at some positive value and
- Device is operating as a Voltage-Controlled Resistor


For an n channel JFET,  $V_{GS}$  may never be positive\*

For an p channel JFET,  $V_{GS}$  may never be negative\*
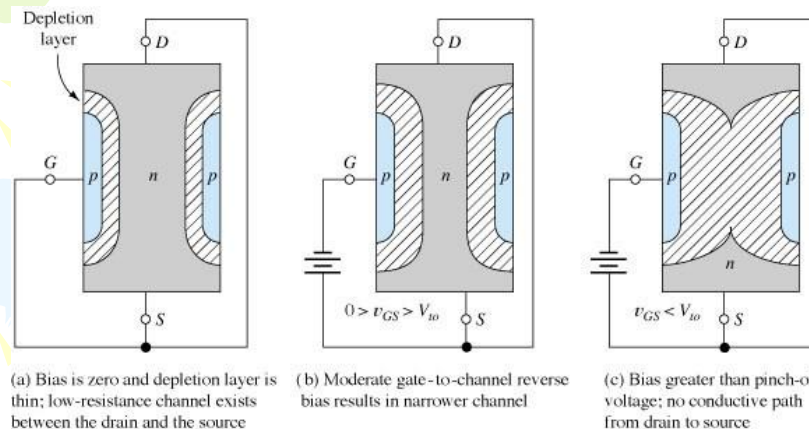
## N-Channel JFET Operation




Operation of JFET at Various Gate Bias Potentials



The nonconductive depletion region becomes thicker with increased reverse bias.  
(Note: The two gate regions of each FET are connected to each other.)

## Field Effect Transistor (FET)

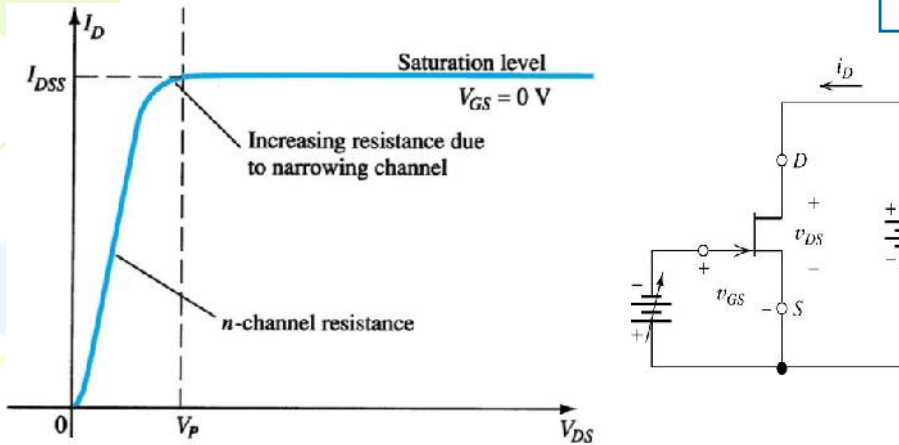

At the pinch-off point:

- any further increase in  $V_{GS}$  does not produce any increase in  $I_D$ .  $V_{GS}$  at pinch-off is denoted as  $V_p$ .
- $I_D$  is at saturation or maximum. It is referred to as  $I_{DSS}$ .
- The ohmic value of the channel is at maximum.

## Transfer (Mutual) Characteristics of n-Channel JFET



n channel JFET:  $i_D$  vs.  $v_{GS}$


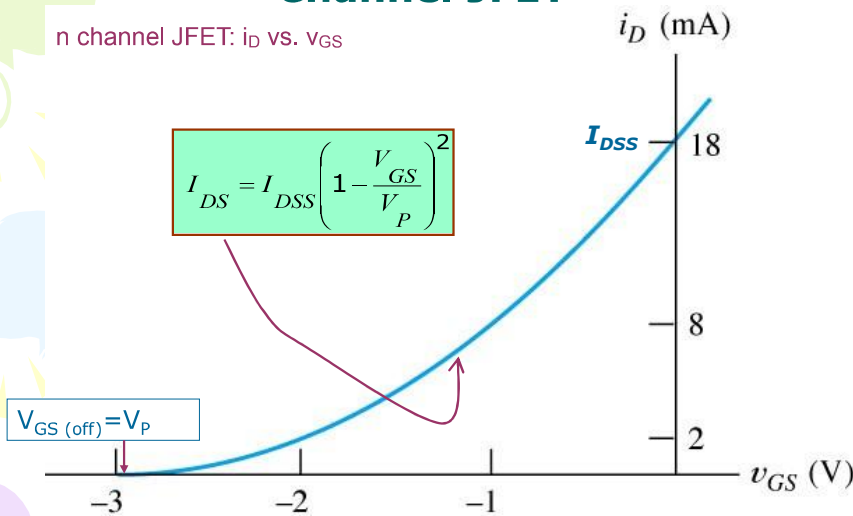


Figure: Transfer (or Mutual) Characteristics of n-Channel JFET

## Transfer (Transconductance) Curve

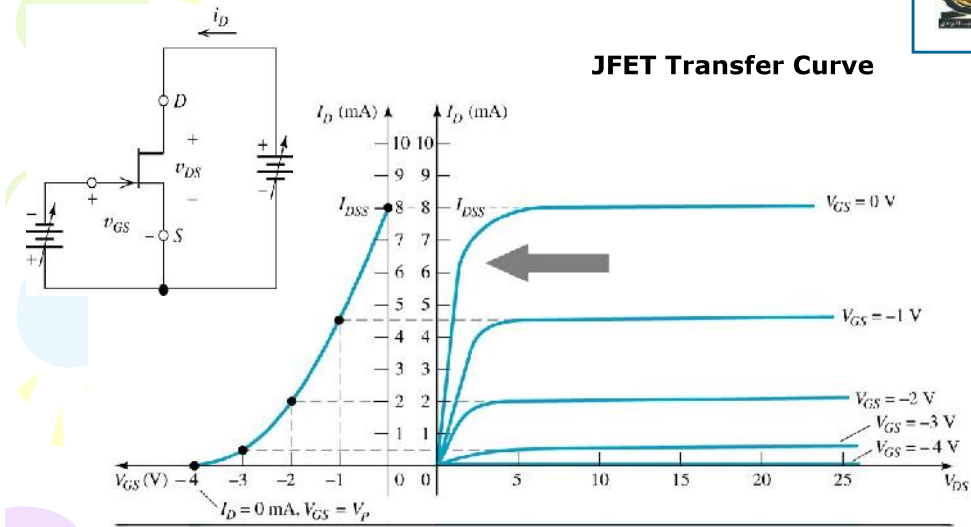

From this graph it is easy to determine the value of  $I_D$  for a given value of  $V_{GS}$ . It is also possible to determine  $I_{DSS}$  and  $V_P$  by looking at the knee where  $V_{GS}$  is 0.

### Plotting the Transconductance Curve



Using  $I_{DSS}$  and  $V_P$  (or  $V_{GS(off)}$ ) values found in a specification sheet, the Family of Curves can be plotted by making a table of data using the following 3 steps:

Step 1:

$$\text{Solve } I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 \quad \text{for } V_{GS} = 0V$$

Step 2

$$\text{Solve } I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 \quad \text{for } V_{GS} = V_P \text{ ( aka } V_{GS(off)} \text{ )}$$

Step 3:

$$\text{Solve } I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 \quad \text{for } 0V \geq V_{GS} \geq V_P \text{ in } 1V \text{ increments for } V_{GS}$$



## Chapter 8

# Sinusoidal Steady-State Analysis



## Chapter 8




- 8.1** Introduction and Motivation.
- 8.2** Sinusoids' features.
- 8.3** Phasors.
- 8.4** Phasor relationships for circuit elements.
- 8.5** Impedance and admittance.


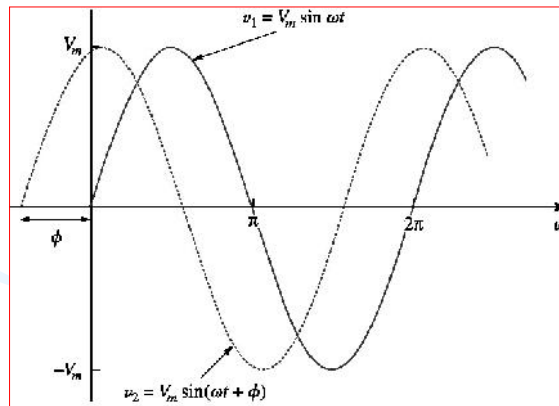
## 8.1 Introduction




A sinusoid is a signal that has the form of the sine or cosine function.




## 8.1 Motivation



How to determine  $v(t)$  and  $i(t)$ ?

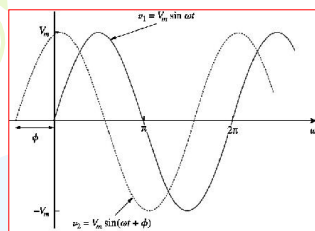

$$v_s = 10 \cos 4t$$

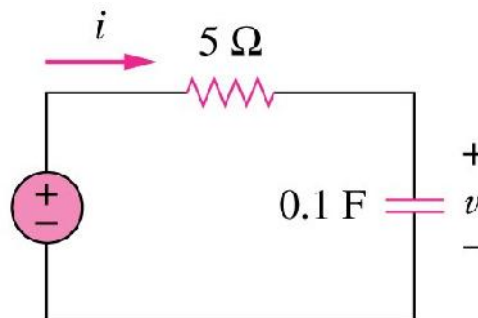


How can we apply what we have learned before to determine  $i(t)$  and  $v(t)$ ?

## 8.2 Sinusoids (1)




- A sinusoid is a signal that has the form of the sine or cosine function.
- A general expression for the sinusoid,

$$v(t) = V_m \sin(\omega t + \phi)$$

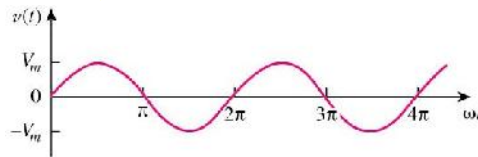

(a)

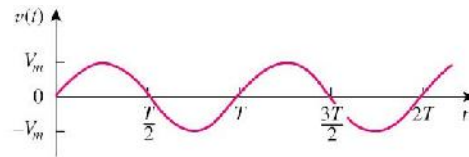

(b)

where

$V_m$  = the **amplitude** of the sinusoid

$\omega$  = the angular frequency in radians/s  
(Radian Frequency =  $2\pi f$ )



$\Phi$  = the phase

$\theta = \omega t$  ----- Angle
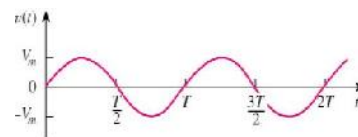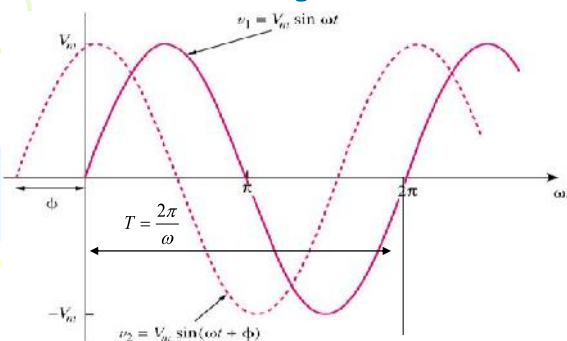
## 8.2 Sinusoids (2)



A **periodic function** is one that satisfies  $v(t) = v(t + nT)$ , for all  $t$  and for all integers  $n$ .




(b)

$$f = \frac{1}{T} \text{ Hz} \quad \omega = 2\pi f$$

- Only two sinusoidal values with the **same frequency** can be compared by their amplitude and phase difference.
- If phase difference is zero, they are in phase; if phase difference is not zero, they are out of phase.

## 8.2 Sinusoids (3)

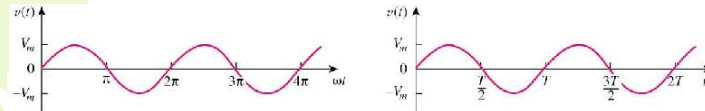


$$v(t) = V_m \sin(\omega t + \phi)$$


$\theta = \omega t$  ----- Angle

completes one cycle every  $2\pi/\omega$

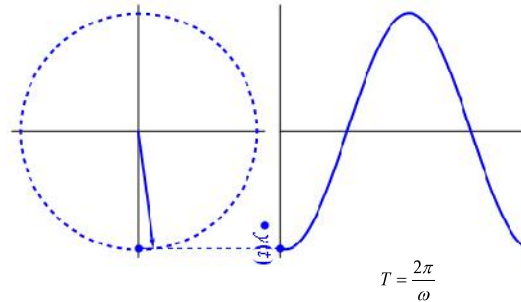$\theta$  is the angle it forms with the real axis at  $t = n \cdot 2\pi/\omega$ , for integer values of  $n$ .



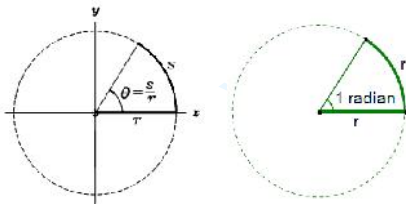- There are  $2\pi$  radians in one circle. ( $2\pi = 360^\circ$ )



## 8.2 Sinusoids (4)



### Converting degrees to radians

$$\text{degrees} \times \frac{\pi}{180} = \text{radians}$$

Example

$$\begin{aligned} 150^\circ \\ 150 \cdot \frac{\pi}{180} \\ \frac{150\pi}{180} \\ \frac{5\pi}{6} \end{aligned}$$

$$150^\circ = \frac{5\pi}{6} \text{ radians}$$

### Converting radians to degrees

$$\text{radians} \times \frac{180}{\pi} = \text{degrees}$$

Example

$$-\frac{3\pi}{4} \text{ radians} = -\frac{3\cancel{\pi}}{4} \times \frac{180^\circ}{\cancel{\pi}} = \left(-\frac{3}{4}\right) \cdot 180^\circ = -135^\circ$$

$$1 \text{ radian} = 1 \times \frac{180^\circ}{\pi} \approx 57.3^\circ$$

## 8.2 Sinusoids (5)



$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$


With these identities, it is easy to show that

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$


$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$
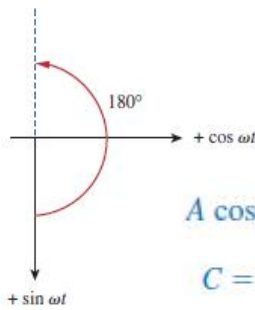
$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$



$$A \cos \omega t + B \sin \omega t = C \cos(\omega t - \theta)$$
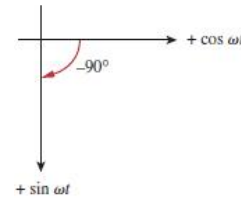
$$C = \sqrt{A^2 + B^2}, \quad \theta = \tan^{-1} \frac{B}{A}$$



## 8.2 Sinusoids (6)



### Example 1

Given a sinusoid,  $5 \sin(4\pi t - 60^\circ)$ , calculate its amplitude, phase, angular frequency, period, and frequency.

### Solution:

$$v(t) = V_m \sin(\omega t + \phi)$$

Amplitude = 5, phase =  $-60^\circ$ , angular frequency =  $4\pi$  rad/s, Period = 0.5 s, frequency = 2 Hz.

$$f = \frac{1}{T} \text{ Hz} \quad \omega = 2\pi f$$

## 8.2 Sinusoids (7)



### Example 2

Find the phase angle between  $i_1 = -4\sin(377t + 25^\circ)$  and  $i_2 = 5\cos(377t - 40^\circ)$ , does  $i_1$  lead or lag  $i_2$ ?

### Solution:

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

Since  $\sin(\omega t + 90^\circ) = \cos \omega t$

$$i_2 = 5\sin(377t - 40^\circ + 90^\circ) = 5\sin(377t + 50^\circ)$$


$$i_1 = -4\sin(377t + 25^\circ) = 4\sin(377t + 180^\circ + 25^\circ) = 4\sin(377t + 205^\circ)$$

therefore,  $i_1$  leads  $i_2$   $155^\circ$ .  $\sin(\omega t \pm 180^\circ) = -\sin \omega t$

## 8.2 Sinusoids (8)



Square wave

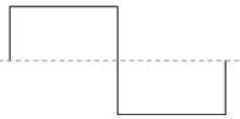



one wave cycle

Triangle wave




one wave cycle

Sawtooth wave

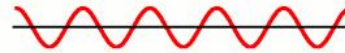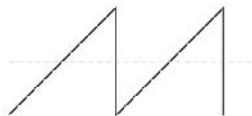

Sine wave

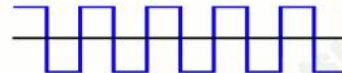

Square wave



Saw-tooth wave




Triangle wave

www.explainthatstuff.com
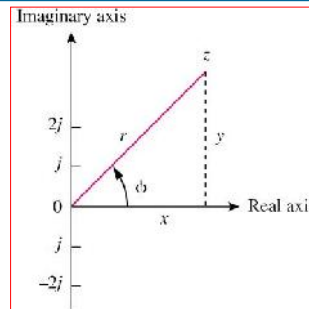
## 8.3 Phasor (1)



- A phasor is a complex number that represents the amplitude and phase of a sinusoid.



- It can be represented in one of the following three forms:

$$x = r \cos \phi, \quad y = r \sin \phi$$

- Rectangular  $z = x + jy = r(\cos \phi + j \sin \phi)$
- Polar  $z = r \angle \phi$
- Exponential  $z = r e^{j\phi}$

where

$$r = \sqrt{x^2 + y^2}$$

$$\phi = \tan^{-1} \frac{y}{x}$$

the imaginary number  $j = \sqrt{-1}$ ;

## 8.3 Phasor (2)



$$z = x + jy = r \angle \phi = r(\cos \phi + j \sin \phi)$$

Mathematic operation of complex number:

- Addition  $z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$

- Subtraction  $z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$

- Multiplication  $z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$

- Division  $\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$

- Reciprocal  $\frac{1}{z} = \frac{1}{r} \angle -\phi$

$$\frac{1}{j} = -j$$

- Square root  $\sqrt{z} = \sqrt{r} \angle \phi/2$

- Complex conjugate  $z^* = x - jy = r \angle -\phi = r e^{-j\phi}$

- Euler's identity  $e^{\pm j\phi} = \cos \phi \pm j \sin \phi$

### 8.3 Phasor (3)



$$z = x + jy = r \angle \phi = r(\cos \phi + j \sin \phi)$$

#### Example 3

- Evaluate the following complex numbers:

a.  $[(5 + j2)(-1 + j4) - 5 \angle 60^\circ]$

b.  $\frac{10 + j5 + 3 \angle 40^\circ}{-3 + j4} + 10 \angle 30^\circ$

#### Solution:

a.  $-15.5 + j13.67$

b.  $8.293 + j2.2$

### 8.3 Phasor (4)



- Transform a sinusoid to and from the time domain to the phasor domain:

$$v(t) = V_m \cos(\omega t + \phi) \longleftrightarrow V = V_m \angle \phi$$

(time domain)

(phasor domain)

- Amplitude** and **phase difference** are two principal concerns in the study of voltage and current sinusoids.
- Phasor will be defined from the **cosine function** in all our proceeding study. If a voltage or current expression is in the form of a sine, it will be changed to a cosine by subtracting from the phase.





## 8.3 Phasor (7)



### Example 5:

Transform the sinusoids corresponding to phasors:

- $\mathbf{V} = -10\angle 30^\circ \text{ V}$
- $\mathbf{I} = j(5 - j12) \text{ A}$

### Solution:

- $v(t) = 10\cos(\omega t + 210^\circ) \text{ V}$
- Since  $\mathbf{I} = 12 + j5 = \sqrt{12^2 + 5^2} \angle \tan^{-1}\left(\frac{5}{12}\right) = 13\angle 22.62^\circ$   
 $i(t) = 13\cos(\omega t + 22.62^\circ) \text{ A}$

## 8.3 Phasor (8)



### The differences between $v(t)$ and $\mathbf{V}$ :

- $v(t)$  is instantaneous or time-domain representation  
 $\mathbf{V}$  is the frequency or phasor-domain representation.
- $v(t)$  is time dependent,  $\mathbf{V}$  is not.
- $v(t)$  is always real with no complex term,  $\mathbf{V}$  is generally complex.

Note: Phasor analysis applies only when frequency is constant; when it is applied to two or more sinusoid signals only if they have the same frequency.

## 8.3 Phasor (9)



Relationship between differential, integral operation in phasor listed as follow:

$$\begin{aligned} v(t) &\longleftrightarrow V = V\angle\phi \\ \frac{dv}{dt} &\longleftrightarrow j\omega V \\ \int v dt &\longleftrightarrow \frac{V}{j\omega} \end{aligned}$$

## 8.3 Phasor (10)



### Example 6

Use phasor approach, determine the current  $i(t)$  in a circuit described by the integro-differential equation.

$$4i + 8\int i dt - 3\frac{di}{dt} = 50\cos(2t + 75^\circ)$$

$$4\mathbf{I} + \frac{8\mathbf{I}}{j\omega} - 3j\omega\mathbf{I} = 50\angle 75^\circ$$

But  $\omega = 2$ , so

$$\mathbf{I}(4 - j4 - j6) = 50\angle 75^\circ$$

$$\mathbf{I} = \frac{50\angle 75^\circ}{4 - j10} = \frac{50\angle 75^\circ}{10.77\angle -68.2^\circ} = 4.642\angle 143.2^\circ \text{ A}$$

Converting this to the time domain,



$$i(t) = 4.642 \cos(2t + 143.2^\circ) \text{ A}$$

**Answer:**  $i(t) = 4.642\cos(2t + 143.2^\circ) \text{ A}$



## 8.4 Phasor Relationships for Circuit Elements (1)





Resistor:

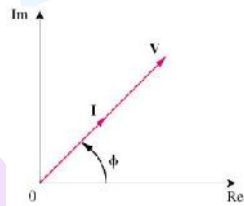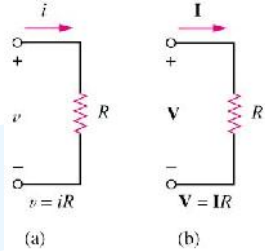

Inductor

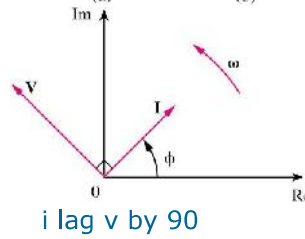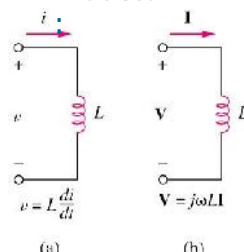

Capacitor:

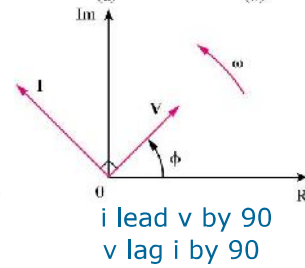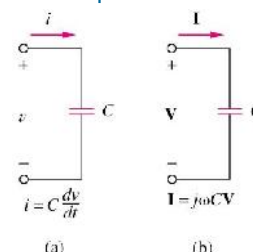

## 8.4 Phasor Relationships for Circuit Elements (2)



### Summary of voltage-current relationship

Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

## 8.4 Phasor Relationships for Circuit Elements (3)



### Example 7

If voltage  $v(t) = 10 \cos(100t + 30^\circ)$  is applied to a  $50 \mu\text{F}$  capacitor, calculate the current,  $i(t)$ , through the capacitor.

$$V = \frac{I}{j\omega C}$$

Since  $j = 1 \angle 90^\circ$ ,

$$i = C \frac{dv}{dt}$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

**Answer:**  $i(t) = 50 \cos(100t + 120^\circ) \text{ mA}$

## 8.5 Impedance and Admittance (1)



- The impedance  $Z$  of a circuit is the ratio of the phasor voltage  $V$  to the phasor current  $I$ , measured in ohms  $\Omega$ .

$$Z = \frac{V}{I} = R + jX$$

where  $R = \text{Re}, Z$  is the resistance and  $X = \text{Im}, Z$  is the reactance. **Positive  $X$**  is for **L** and **negative  $X$**  is for **C**.

- The admittance  $Y$  is the reciprocal of impedance, measured in siemens (S).

$$Y = \frac{1}{Z} = \frac{I}{V}$$


## 8.5 Impedance and Admittance (2)



### Impedances and admittances of passive elements

Element	Impedance	Admittance
<b>R</b>	$Z = R$	$Y = \frac{1}{R}$
<b>L</b>	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
<b>C</b>	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

## 8.5 Impedance and Admittance (3)

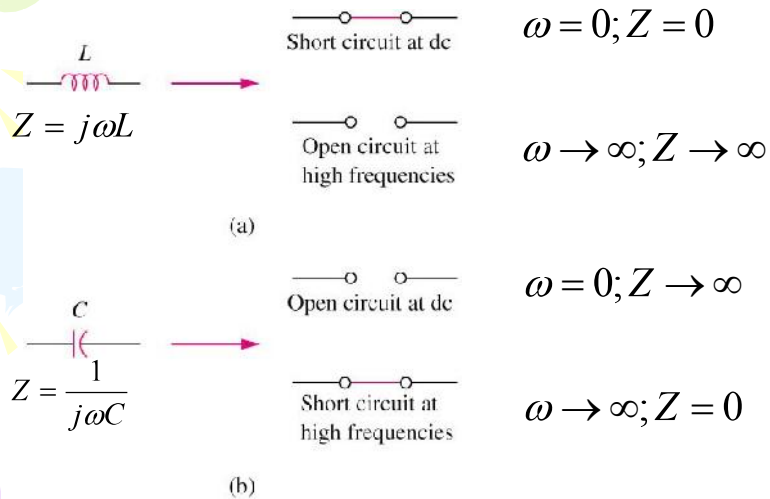

## 8.5 Impedance and Admittance (4)



After we know how to convert RLC components from time to phasor domain, we can **transform** a time domain circuit into a phasor/frequency domain circuit.

Hence, we can apply the KCL laws and other theorems to **directly** set up phasor equations involving our target variable(s) for solving.

## 8.5 Impedance and Admittance (5)




### **Example 8**

Refer to Figure below, determine  $v(t)$  and  $i(t)$ .

From the voltage source  $10 \cos 4t$ ,  $\omega = 4$ ,

$$\mathbf{V}_s = 10 \angle 0^\circ \text{ V}$$

$$v_s = 10 \cos 4t$$

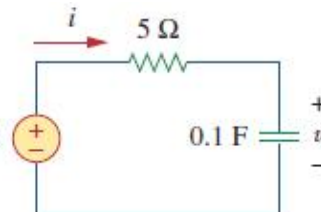

The impedance is

$$\mathbf{Z} = 5 + \frac{1}{j\omega C} = 5 + \frac{1}{j4 \times 0.1} = 5 - j2.5 \Omega$$

$$\begin{aligned} \mathbf{I} &= \frac{\mathbf{V}_s}{\mathbf{Z}} = \frac{10 \angle 0^\circ}{5 - j2.5} = \frac{10(5 + j2.5)}{5^2 + 2.5^2} \\ &= 1.6 + j0.8 = 1.789 \angle 26.57^\circ \text{ A} \end{aligned}$$


## 8.5 Impedance and Admittance (5)



### Example 8

Refer to Figure below, determine  $v(t)$  and  $i(t)$ .

The voltage across the capacitor is

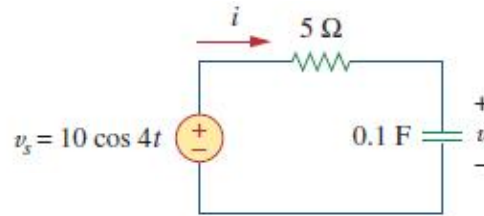

$$\begin{aligned} V &= IZ_C = \frac{I}{j\omega C} = \frac{1.789/26.57^\circ}{j4 \times 0.1} \\ &= \frac{1.789/26.57^\circ}{0.4/90^\circ} = 4.47/-63.43^\circ \text{ V} \end{aligned}$$

Converting  $I$  and  $V$  in Eqs. (9.9.1) and (9.9.2) to the time domain, we get

$$i(t) = 1.789 \cos(4t + 26.57^\circ) \text{ A}$$


$$v(t) = 4.47 \cos(4t - 63.43^\circ) \text{ V}$$

## 8.5 Impedance and Admittance (5)


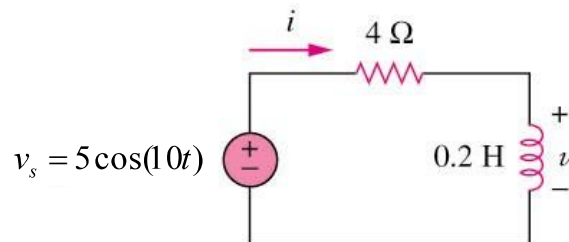
### Example 8

Refer to Figure below, determine  $v(t)$  and  $i(t)$ .



**Answers:**  $i(t) = 1.118 \cos(10t - 26.56^\circ) \text{ A}$ ;  $v(t) = 2.236 \cos(10t + 63.43^\circ) \text{ V}$

## 8.7 Impedance Combinations (1)




- The following principles used for DC circuit analysis all apply to AC circuit.
- For example:
  - a. voltage division
  - b. current division
  - c. circuit reduction
  - d. impedance equivalence
  - e. Y- $\Delta$  transformation

## 8.7 Impedance Combinations (2)


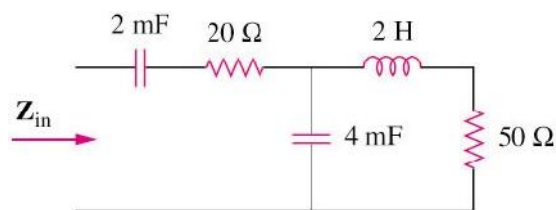
### Example 9

Determine the input impedance of the circuit in figure below at  $\omega = 10$  rad/s.



**Answer:**  $Z_{in} = 32.38 - j73.76$





# Chapter 9

## Diodes and its Applications

### Diodes




- 1** Introduction.
- 2** PN junction.
- 3** IV Ch/s.
- 4** Diode Models.
- 5** Diode Applications.


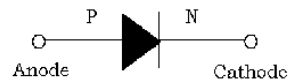
## Introduction



- The diode is the simplest and most fundamental nonlinear circuit element.
- Just like resistor, it has two terminals.
- Unlike resistor, it has a nonlinear current-voltage characteristics.
- Its use in rectifiers is the most common application.





## Types of Diodes

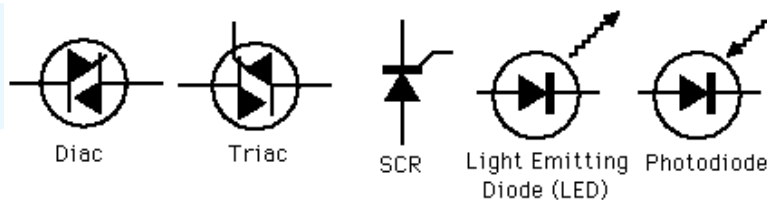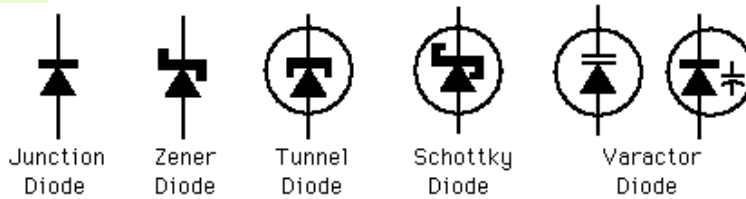

## PN junction

Physical Structure

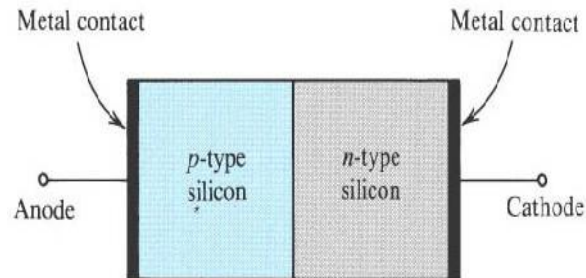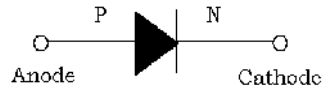

The most important region, which is called *pn* junction, is the boundary between *n*-type and *p*-type semiconductor.

## PN Junction Under Open-Circuit Condition

- Usually the *pn* junction is asymmetric, there are  $p^+n$  and  $pn^+$ .
- The superscript "+" denotes the region is more heavily doped than the other region.

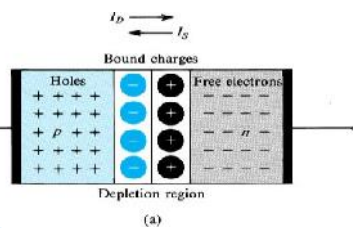


Fig (a) shows the *pn* junction with no applied voltage (open-circuited terminals).


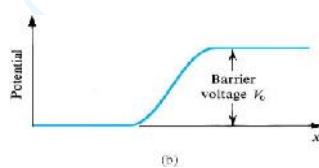


Fig.(b) shows the potential distribution along an axis perpendicular to the junction.

## PN junction under Forward Biasing

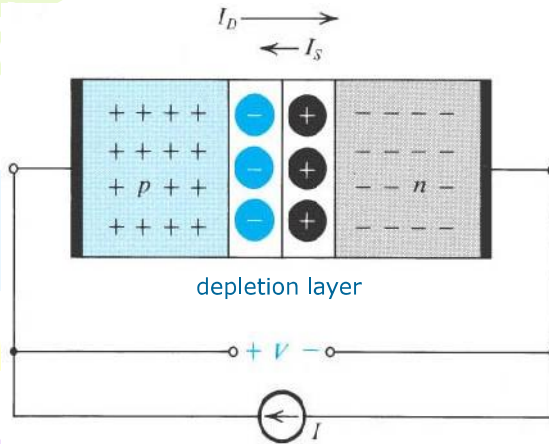

### Physical Structure



➤ The  $pn$  junction excited by a constant-current source supplying a current  $I$  in the forward direction.

➤ The depletion layer narrows and the barrier voltage decreases by  $V$  volts, which appears as an external voltage in the forward direction.

## I-V characteristic equation:



I-V characteristic equation:

$$I_D = I_s (e^{V_D/nV_T} - 1)$$

Exponential relationship, nonlinear.

$I_s$  is called saturation current, strongly depends on temperature.


-  $n$  is emission coefficient in general  $n = 1$

$V_T$  is thermal voltage.  $V_T = 0.025 \text{ V}$

The thermal voltage at  $T = 300\text{K}$  ( $27^\circ\text{C}$ ) is


$$V_T = \frac{kT}{q} = \frac{1.38 \times 10^{-23} \times 300}{1.6 \times 10^{-19}} = 25.88\text{mV}$$

## I-V characteristic

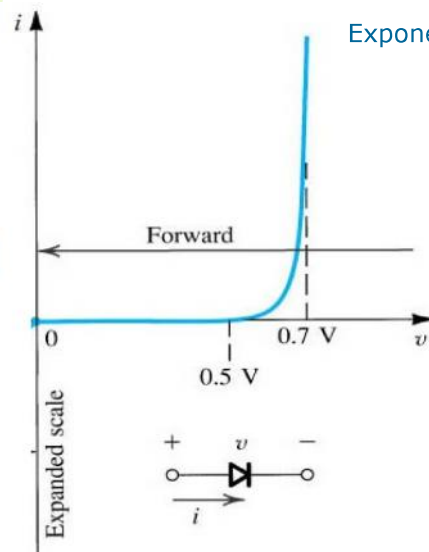

Exponential

$$I_D = I_S ( e^{V_D/nV_T} - 1 )$$

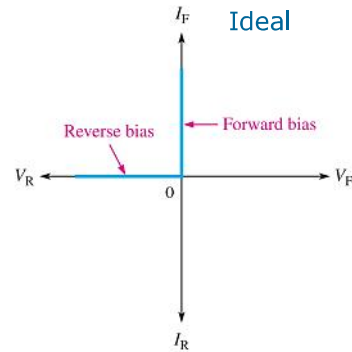

(c) Ideal V-I characteristic curve (blue)

## I-V characteristic equation:



- Turn-on voltage


▶ A conduction diode has approximately a constant voltage drop across it. It's called turn-on voltage.

$$V_{D(on)} = 0.7V \quad \text{For silicon}$$

$$V_{D(on)} = 0.25V \quad \text{For germanium}$$

- Diodes with different current rating will exhibit the turn-on voltage at different currents.
- Negative TC,  $TC = -2mv/^\circ C$
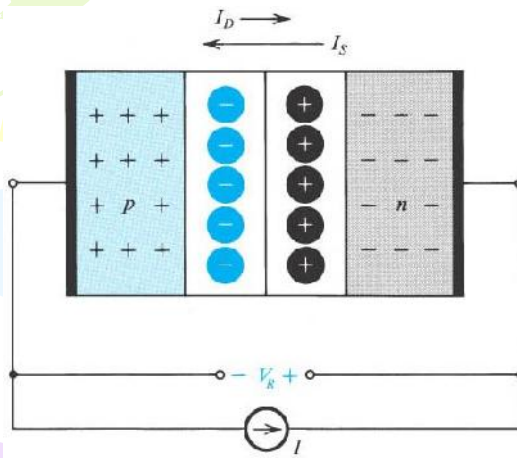
## The pn Junction Under Reverse-Bias Conditions



- > The *pn* junction excited by a constant-current source  $I$  in the reverse direction.
- > To avoid breakdown,  $I$  is kept smaller than  $I_S$ .
- > Note that the depletion layer widens and the barrier voltage increases by  $V_R$  volts, which appears between the terminals as a reverse voltage.

## The pn Junction Under Reverse-Bias Conditions




I-V characteristic equation:


$$i = I_s \quad \text{Independent of voltage}$$

Where  $I_s$  is the saturation current, it is proportional to  $n_i^2$  which is a strong function of temperature.
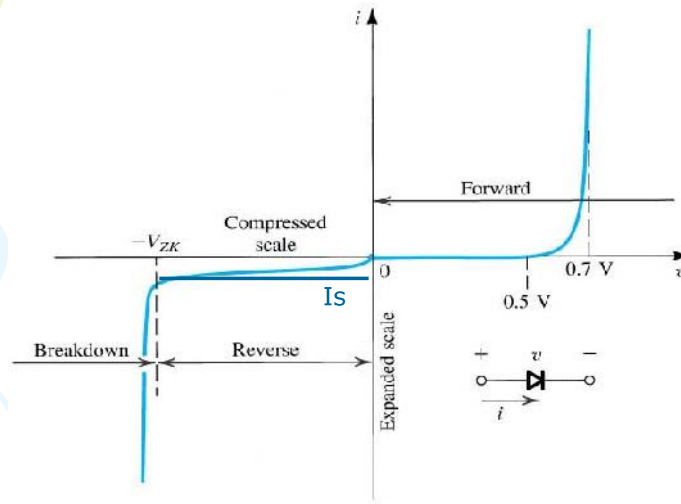
## The pn Junction Under Reverse-Bias Conditions


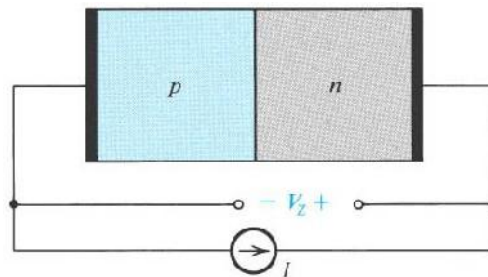
## The pn Junction In the Breakdown Region




The  $pn$  junction excited by a reverse-current source  $I$ , where  $I > I_s$ . The junction breaks down, and a voltage  $V_Z$ , with the polarity indicated, develops across the junction.

## The pn Junction In the Breakdown Region



- Supposing  $I \gg I_s$ , the current source will move holes from p to n through the external circuit.
- The free electrons move through opposite direction.
- This result in the increase of barrier voltage and decrease almost zero of diffusion current.
- To achieved the equilibrium, a new mechanism sets in to supply the charge carriers needed to support the current I.
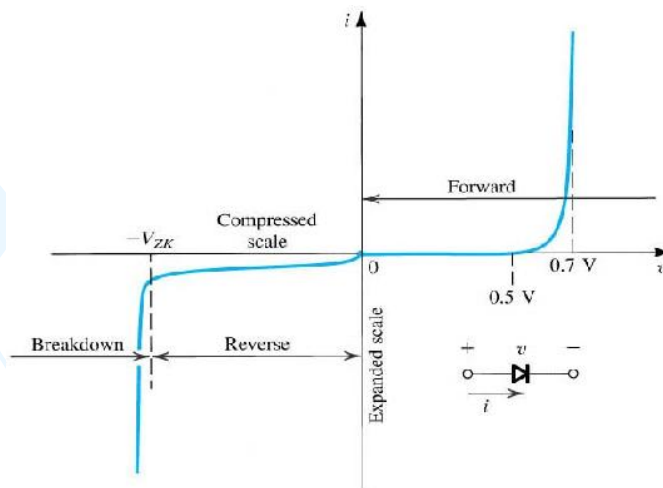
## The pn Junction In the Breakdown Region






## Regions



### Terminal Characteristic of Junction Diodes

- The Forward-Bias Region, determined by  $v > 0$
- The Reverse-Bias Region, determined by  $-V_{ZK} < v < 0$
- The Breakdown Region, determined by  $v < -V_{ZK}$

## Diode Summary

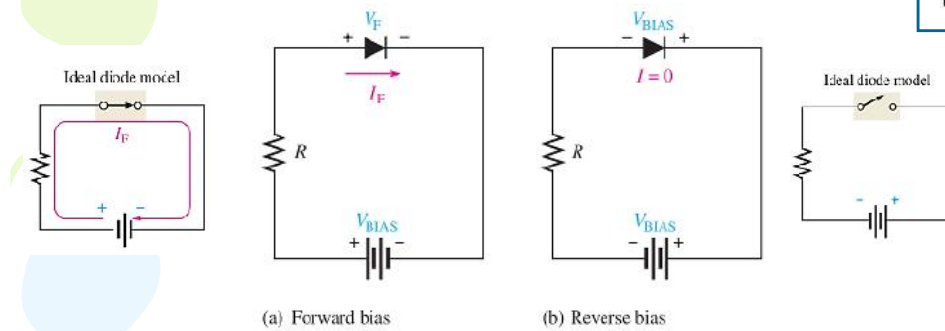

### Ideal

$$V_F = 0 \text{ V} \quad I_F = \frac{V_{BIAS}}{R_{LIMIT}}$$

$$I_R = 0 \text{ A} \quad V_R = V_{BIAS}$$

### Practical

$$I_F = \frac{V_{BIAS} - V_F}{R_{LIMIT}}$$

$$I_R = 0 \text{ A} \\ V_R = V_{BIAS}$$

## Breakdown Mechanisms



- Zener effect

- Occurs in heavily doping semiconductor
- Breakdown voltage is less than 5v.
- Carriers generated by electric field---field ionization.
- TC is negative.



- Avalanche effect.

- Occurs in slightly doping semiconductor
- Breakdown voltage is more than 7v.
- Carriers generated by collision.
- TC is positive.

Remember:

*pn junction breakdown is not a destructive process, provided that the maximum specified power dissipation is not exceeded.*

## Zener Diode

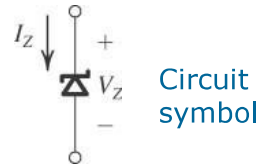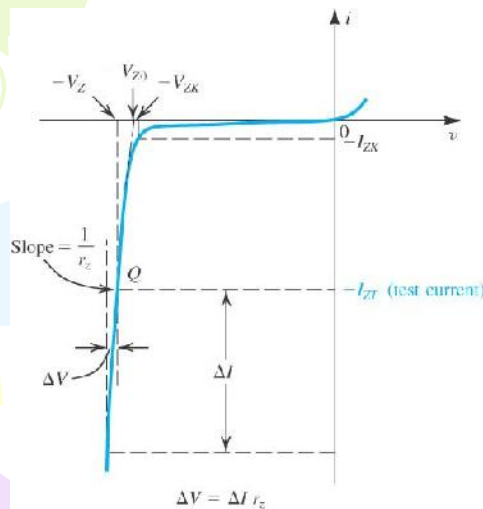

The diode  $i-v$  characteristic with the breakdown region shown in some detail.

## The Diode Models



- Models

- Mathematic model
- Circuit model

### Mathematic Model

$$i = I_s (e^{v/nV_T} - 1)$$

$$\approx \begin{cases} I_s e^{v/nV_T} & \text{Forward biased} \\ -I_s & \text{Reverse biased} \end{cases}$$

The circuit models are derived from approximating the curve into piecewise-line.

## The Diode Models



### Circuit Model


- a) Simplified diode model
- b) The constant-voltage-drop model
- c) Small-signal model
- d) High-frequency model
- e) Zener Diode Model

## Simplified Diode Model




Circuit Model

a) Simplified diode model

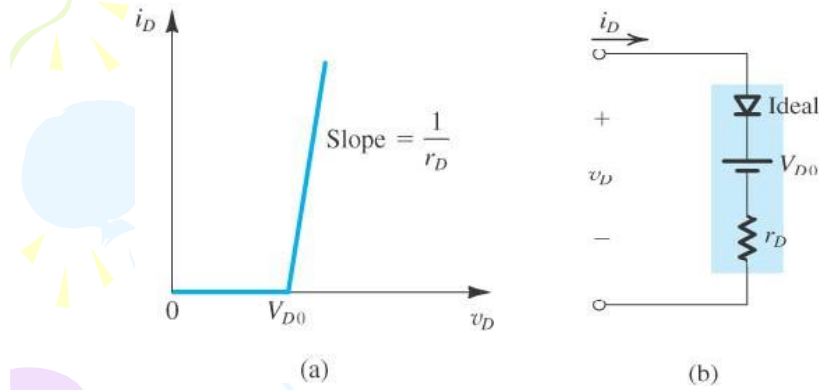

Piecewise-linear model of the diode forward characteristic and its equivalent circuit representation.

## The Constant-Voltage-Drop Model

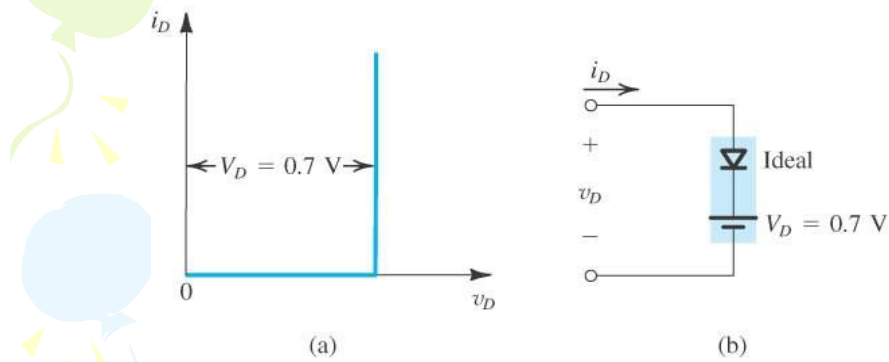


The constant-voltage-drop model of the diode forward characteristics and its equivalent-circuit representation.


## High-Frequency Model



High frequency model

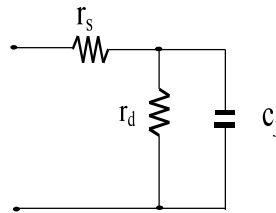

## Zener Diode Model

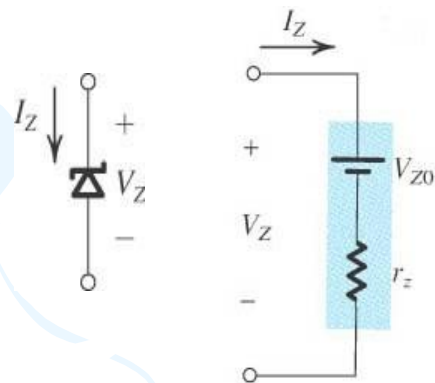


$$V_Z = V_{Z0} + I_Z r_z$$

## Method of Analysis



### Graphical analysis

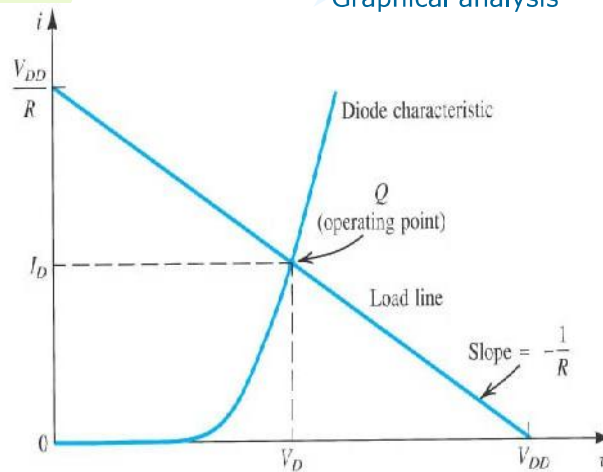


- Load line
- Diode characteristic
- Q is the intersect point
- Visualization

## The Application of Diode Circuits




- Rectifier circuits
  - Half-wave rectifier
  - Full-wave rectifier
    - Transformer with a center-tapped secondary winding
    - Bridge rectifier
  - The peak rectifier
- Voltage regulator
- Limiter

## Half-Wave Rectifier

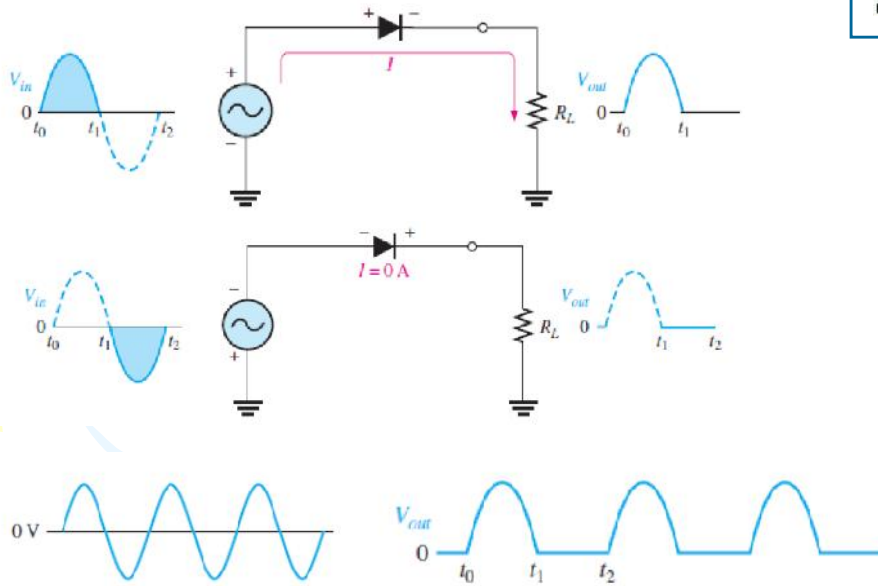


## Half-Wave Rectifier

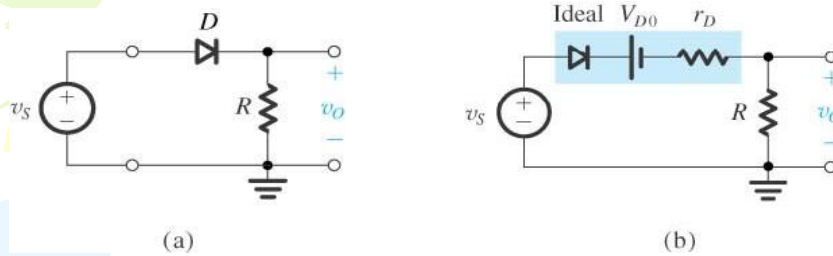


- (a) Half-wave rectifier.
- (b) Equivalent circuit of the half-wave rectifier with the diode replaced with its battery-plus-resistance model.


## Half-Wave Rectifier

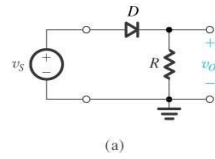

(a)

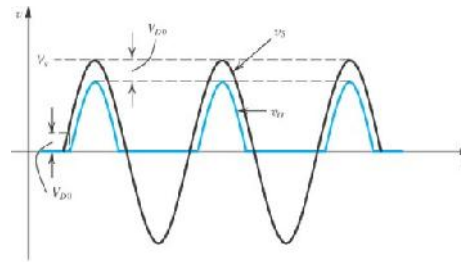

(d)


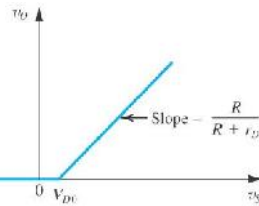


(c)

(c) Transfer characteristic of the rectifier circuit.

(d) Input and output waveforms, assuming that  $r_D \ll R$


## Full-Wave Rectifier

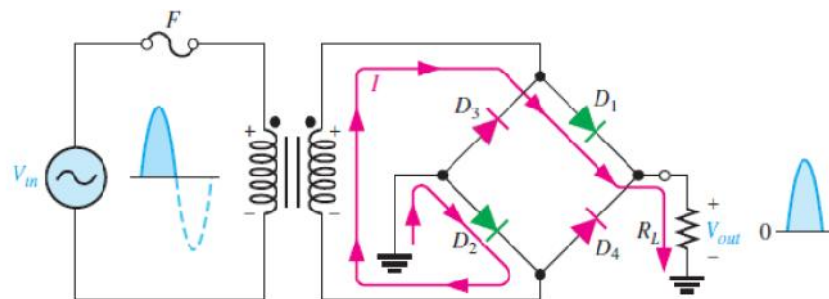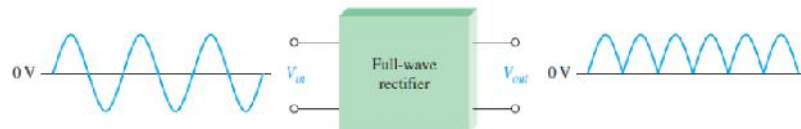

(a) During the positive half-cycle of the input,  $D_1$  and  $D_2$  are forward-biased and conduct current.  $D_3$  and  $D_4$  are reverse-biased.





## Full-Wave Rectifier

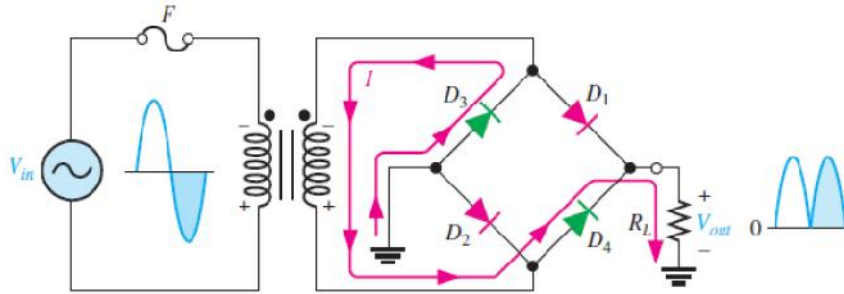

(b) During the negative half-cycle of the input,  $D_3$  and  $D_4$  are forward-biased and conduct current.  $D_1$  and  $D_2$  are reverse-biased.


## Full-Wave Rectifier

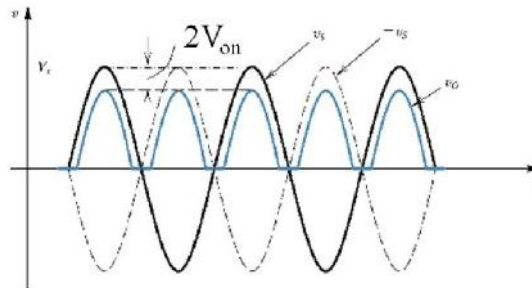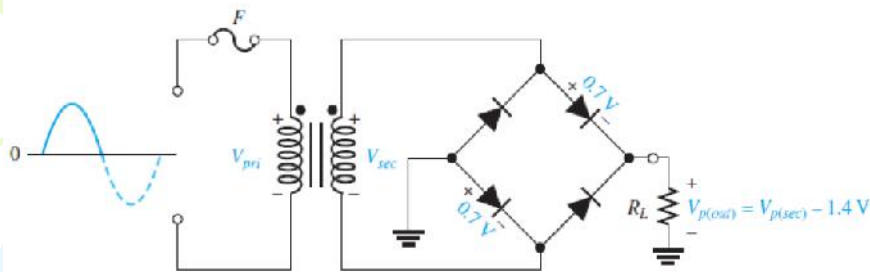

# Full-Wave Rectifier




The Bridge Rectifier

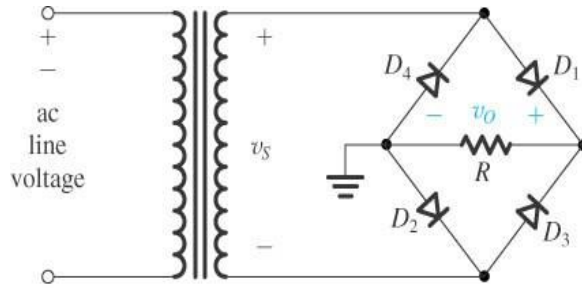

(a)

(a) circuit


# Full-Wave Rectifier

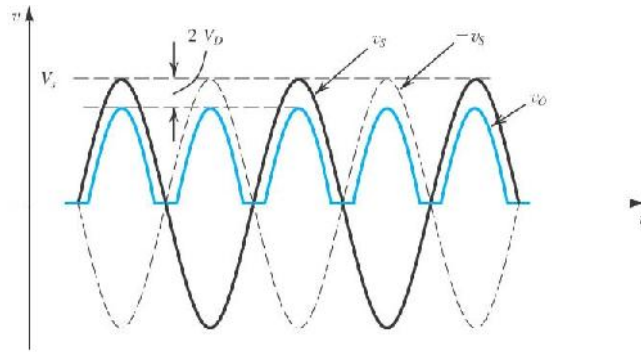


(b)

(b) input and output waveforms



## Diode Limiter

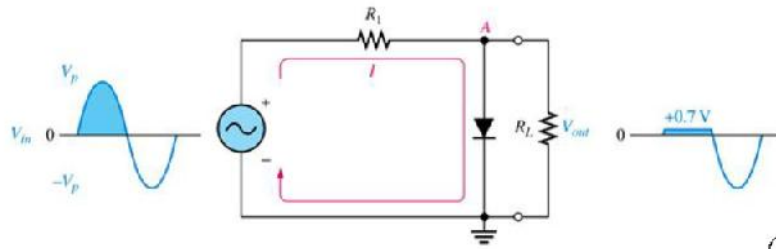

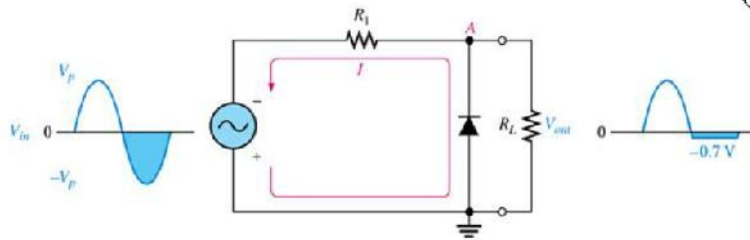
$$V_{out} = \left( \frac{R_L}{R_1 + R_L} \right) V_{in}$$




## Diode Limiter

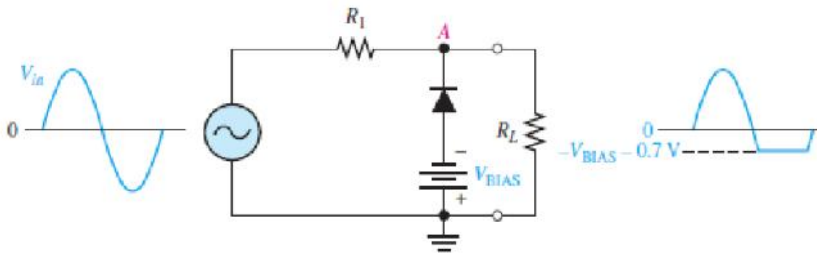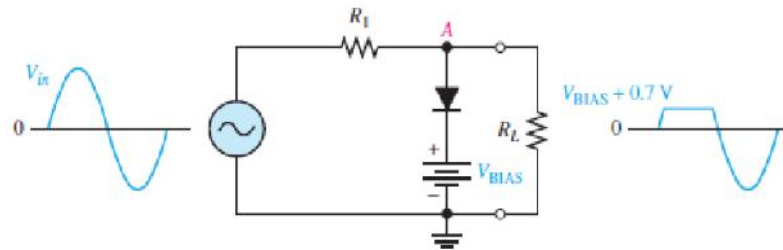


# Diode Limiter

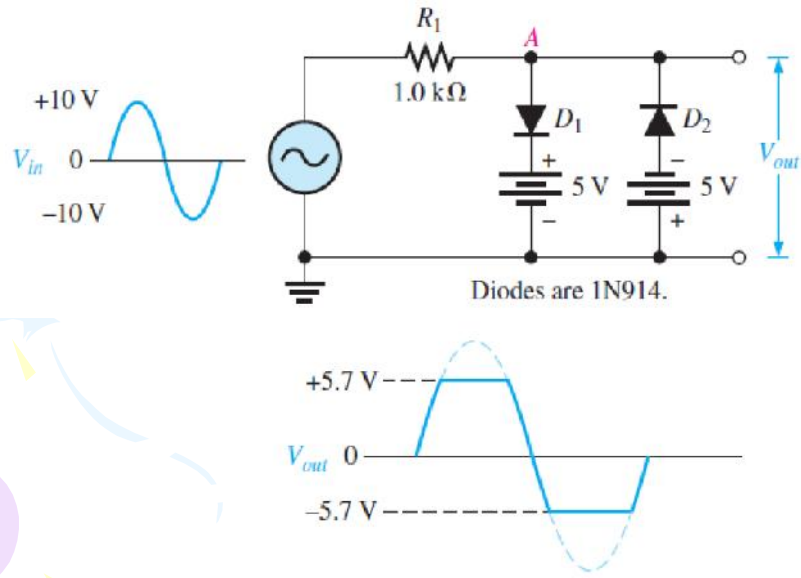

# Diode Limiter

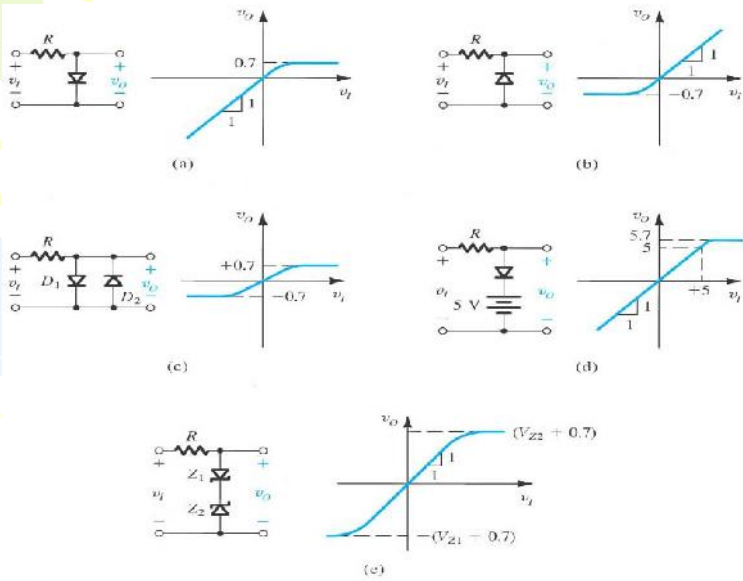


## Diode Limiter

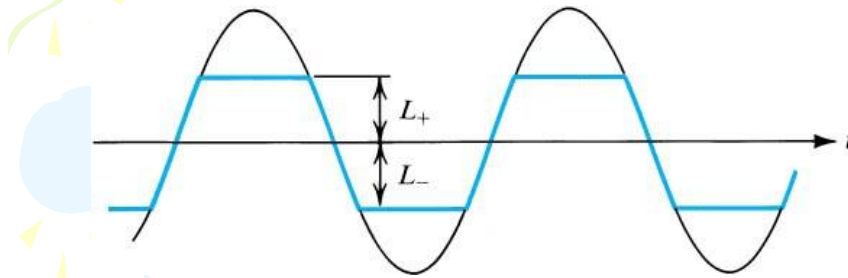

Applying a sine wave to a limiter can result in clipping off its two peaks.

# References

1- Charles K. Alexander and Matthew n. o. Sadiku,  of  
Electric Circuits”, ed. 5<sup>th</sup>, Mc. Graw Hill.

2- Thomas L. Floyd, “ Electronic Devices”, ed. 9<sup>th</sup>